

Solve

BRAC UNIVERSITY

CSE 350

Quiz-3, Section 13

Fall 2024


Marks: 20

Name: _____

ID: _____

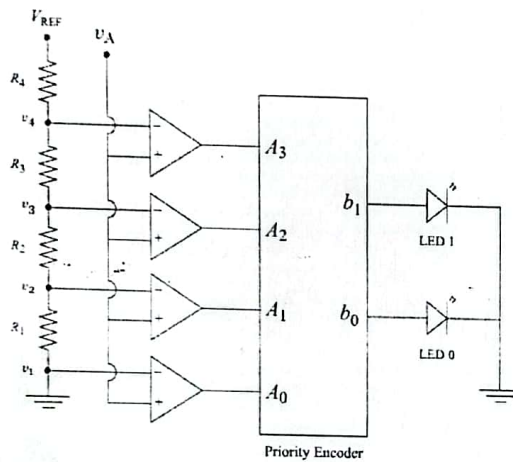1. The figure shows a 2-bit Flash ADC with $V_{REF} = 12V$ and its input ranged from $0V$ to $12V$.

Given: $R_1 = R/2$, $R_2 = 3R/2$, $R_3 = 3R/2$, $R_4 = R/2$. The two outputs of the ADC are connected to two LEDs. This circuit works as Active High Logic.



- Determine the quantization range, corresponding digital output, and the states of the LED for the 2-bit Flash ADC. Make a table with quantization range, corresponding digital output, and the states of the LED. [6]
- Find the truth table of the Encoder and state the priority sequence of the Encoder. [4]

$$1.a) \quad I = \frac{12-0}{4R}$$

$$V_1 = 0$$

$$V_2 = V_1 + I \times \frac{R}{2} = 0 + \frac{12}{4R} \times \frac{R}{2} = 1.5V$$

$$V_3 = V_2 + \frac{12}{4R} \times \frac{3R}{2} = 6V$$

$$V_4 = V_3 + \frac{12}{4R} \times \frac{3R}{2} = 10.5V$$

Range	$b_1 b_0$	LED ₁	LED ₀
0-1.5	00	off	off
1.5-6	01	off	on
6-10.5	10	on	off
10.5-12	11	on	on

1. b)


A_3	A_2	A_1	A_0	b_1	b_0
0	0	0	1	0	0
0	0	1	1	0	1
0	1	1	1	1	0
1	1	1	1	1	1

priority, $A_3 > A_2 > A_1 > A_0$

2. You want to design a 4-bit Flash ADC circuit. You need to use -5V as reference voltage, +20 V as positive power supply and -20 V as negative power supply.

a. Design the circuit to make the maximum output voltage 15 V. [6]

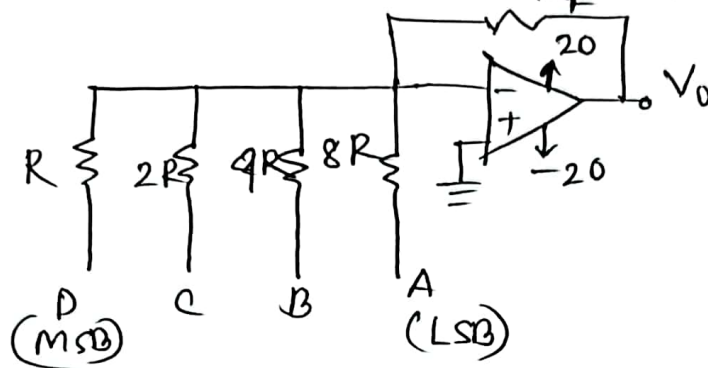b. What will be the step size of the circuit and Output voltage for 0101, 1010. [2+2]



$$2.a) \quad V_O = -\frac{R_F}{R} V_{REF} \left(D + \frac{C}{2} + \frac{B}{4} + \frac{A}{8} \right)$$

$$V_H = 20 \text{ V, and, } V_L = -20 \text{ V}$$

For Max output, Input 1111

$$15 = -\frac{R_F}{R} \times -5 \left(1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right)$$

$$\frac{R_F}{R} = \frac{8}{5}$$

Assume, $R = 20 \mu\Omega$

$$R_F = \frac{8}{5} \times 20 \mu\Omega = 32 \mu\Omega$$

$$2.b) \text{ For, } 0001, \text{ step size } = V_O = -\frac{R_F}{R} \times V_{REF} \left(0 + 0 + 0 + \frac{1}{8} \right)$$

$$= -\frac{32 \times -5}{20} \left(\frac{1}{8} \right) = 1 \text{ V}$$

$$V_O \text{ for } 0101 = -\frac{32}{20} \times -5 \left(0 + \frac{1}{2} + 0 + \frac{1}{8} \right) = 5 \text{ V}$$

$$V_O \text{ for, } 1010 = -\frac{32}{20} \times -5 \left(1 + 0 + \frac{1}{4} + 0 \right) = 10 \text{ V}$$