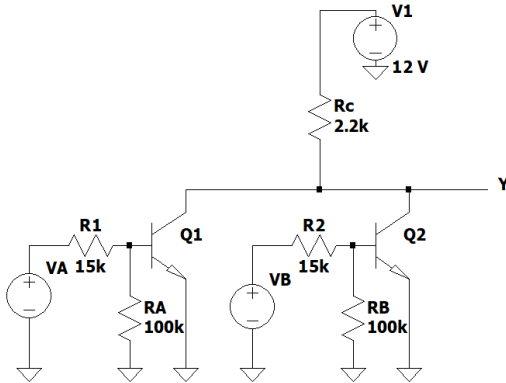


## Basic Operation

### Exercise 1



For the RTL NOR gate-

- Determine the output voltage  $V_Y$  for all logic cases & make a table. Verify your operating mode assumptions.
- What is the high & low threshold for output voltage?
- If  $R_B$  is doubled, find the new base current of  $Q_2$ . Will it still satisfy saturation mode conditions for  $Q_2$  for the cases (1,1) & (0,1)?

[Assume 0.2 V as low input voltage,  $\beta_F = 30$ ]

Ans: a) 12 V, 0.2 V, 0.2 V, 0.2 V  
b) 12 V, 0.2 V  
c) 0.742 mA, Yes


### Practice Problem 1:

For the RTL NOR gate in **Exercise 1**, using the value of  $R_B$  in (d), find the base voltage of  $Q_2$  and verify whether it meets the condition for cutoff for (0,0) & (1,0).

Ans:  $V_B = 0.18 \text{ V} > 0.5 \text{ V}$ , satisfies

## Power Dissipation

### Exercise 2

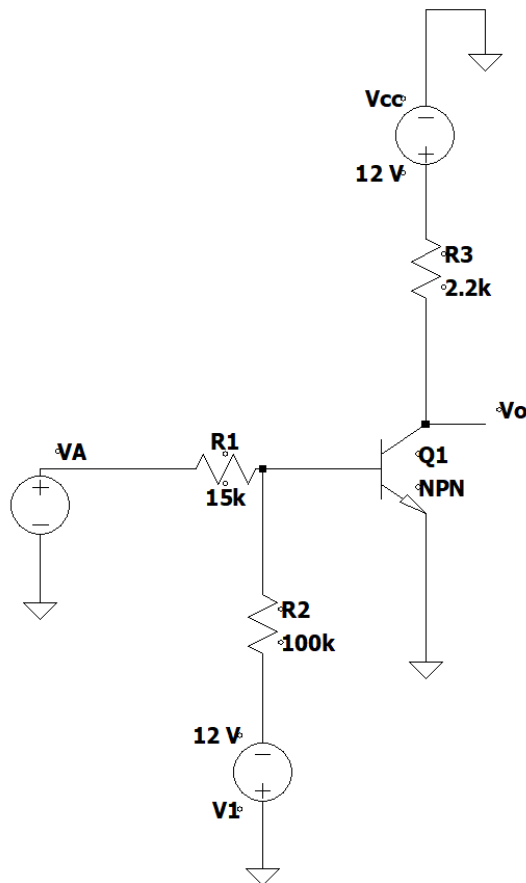

For the RTL inverter, find the maximum & average power dissipation.

[High input = 12 V, Low input = 0.2 V]


Ans: 82.7782 mW, 42.0362 mW

### Practice Problem 2:

For the RTL inverter in **Exercise 2**, find the ratio of maximum & minimum power dissipation, if  $V_1(-12\text{ V})$  was missing.

Ans: 212494.7:1

### Exercise 3

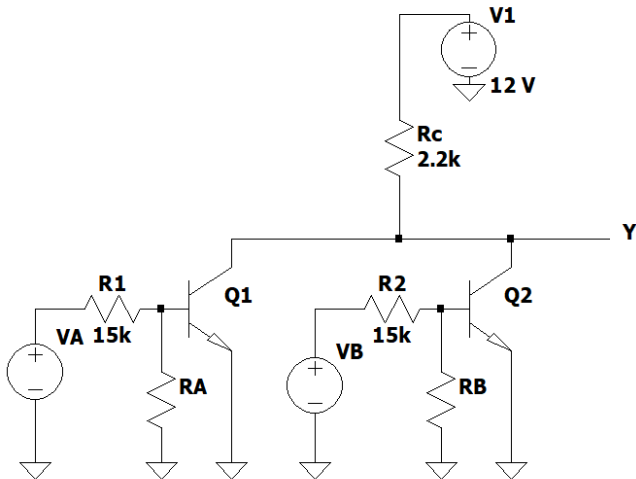

For the RTL NOR gate shown-

- a) If,  $R_A = R_B$ , and the power dissipation for logic case (0,0) is  $0.5 \text{ mW}$ , find the value of the resistances.

$[V_{BE}(\text{saturation}) =$

$0.8 \text{ V}, V_{CE}(\text{saturation}) = 0.2 \text{ V}]$

Assume a low input voltage of  $0.2 \text{ V}$

### Practice Problem 3:


Ans:  $145 \text{ k}\Omega$

In the circuit of Exercise 3, find a new value of  $R_C$  required to double the maximum power dissipation in the circuit.

Ans:  $0.966 \text{ k}\Omega$

## Noise Margin

### Exercise 4

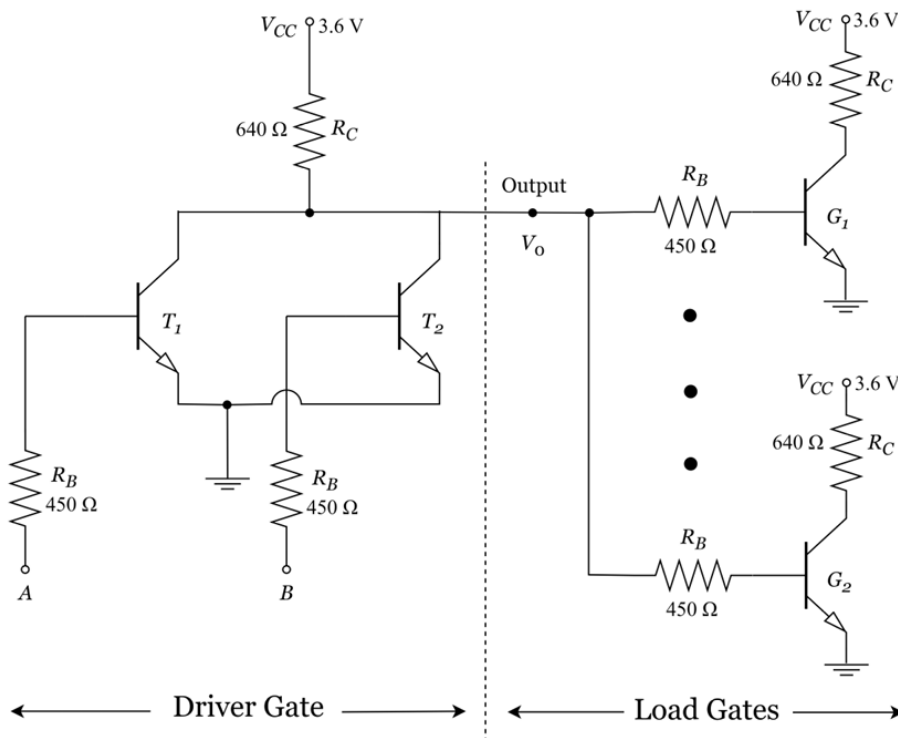

For the RTL NOR driver & RTL NOT loads, find the noise margin.

Assume

$$V_{OH} = 3.5 \text{ V}$$

$$V_{IL} = 0.2 \text{ V}$$

$$\beta_F = 30$$

Ans: 0.3 V

### Practice Problem 4:

In the circuit of **Exercise 4**, what value of  $R_B$  will make  $N_H = N_L$ ?

Ans: 13.55 kΩ

## Fanout

### Exercise 5

For the RTL NOR driver in **Exercise 4** if  $V_{OH} = 1.3 \text{ V}$ -

- Find maximum fanout.
- Find the value of  $V_O$  if fanout (N) = 5, and both inputs are low.
- Find  $(\beta_F)_{min}$  (for the loads) the power dissipation of the loads only for conditions in (b).
- Find the power dissipation in the driver only when both inputs are high.
- If N=1, what logic function does the driver-load combination implement?


## Practice Problem 5:

What value of  $V_{OH}$  would reduce the maximum fanout of the RTL NOR gate to 2 in Exercise 5?

$\text{Ans: } 2.18 \text{ V}$

## Mixed

### Exercise 6

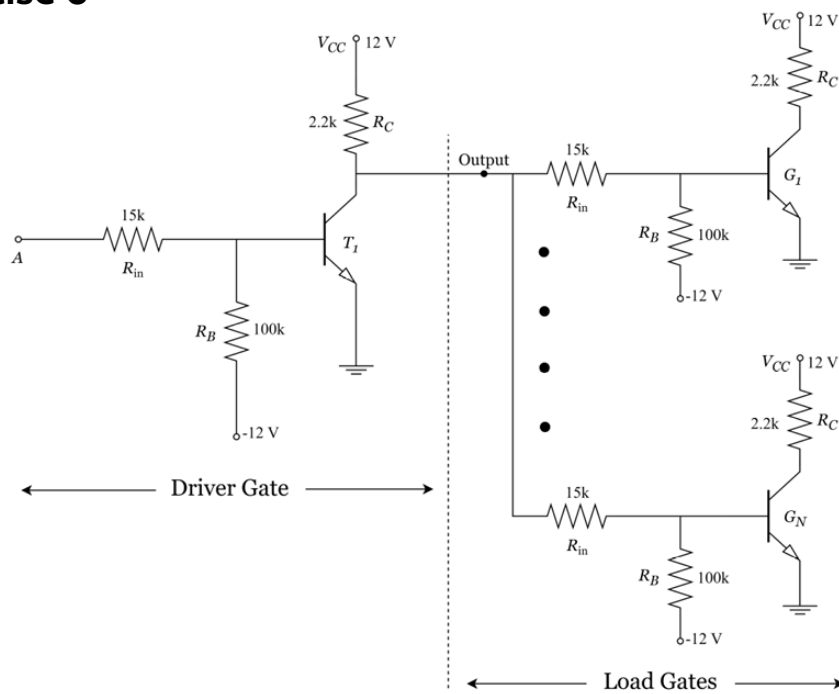

For the given RTL inverters,

$$V_{OH} = 10 \text{ V}, V_{OL} = 0.2 \text{ V}$$

$$\beta_F = 30$$

- Find maximum fanout.
- Find  $V_o$  for  $N=2$  loads, and the input of the driver is low.
- If  $V_{in}$  is high, find the power dissipation of the driver circuit.
- If  $V_{in}$  is low and fanout=2, find the power dissipation of the total circuit (driver + loads).
- Find the noise margin.

$e) 0.375 \text{ W}$


$d) 15.15 \text{ mW}$

$c) 74.86 \text{ mW}$

$b) 9.46 \text{ V}$

$\text{Ans: } a) 1$

## Exercise 7

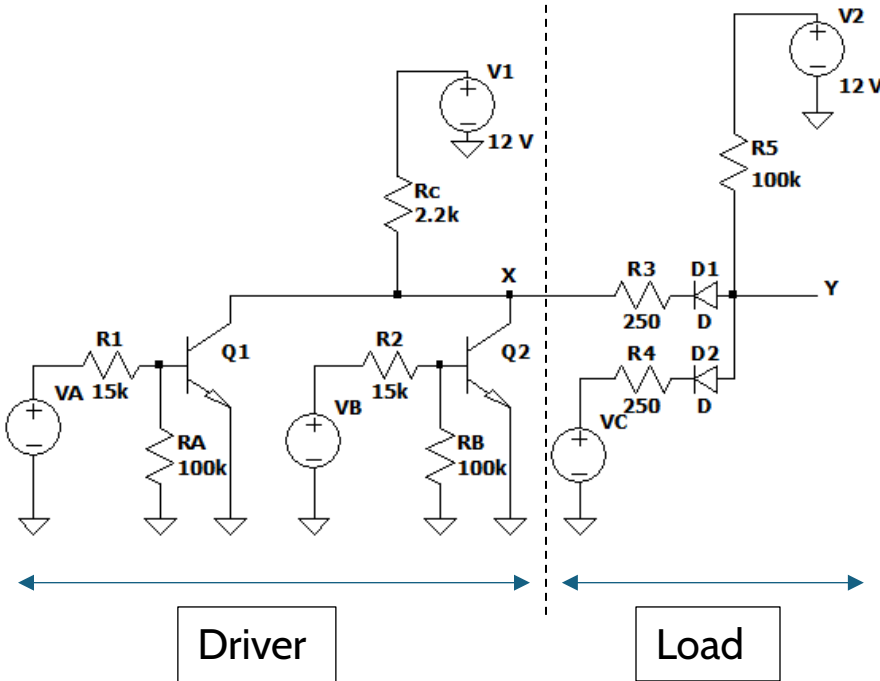

For the circuit given-

- What logic function does it implement?
- Find maximum fanout.
- Find the max power dissipation of the circuit.

Assume

$$V_{OH} = 11.5 \text{ V}$$

$$V_{OL} = 0.2 \text{ V}, \beta_F = 25$$

Ans:


- $Y = A + B.C$
- 13
- 65.7 mW

## Exercise 1

### Solution:

- a) We assume cutoff mode for input logic '0' & saturation mode for input logic '1'.

**Case (0,0):**

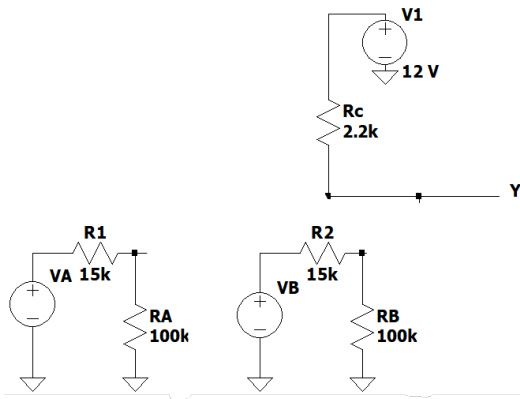

Due to the open circuit, we see,  $V_Y = 12\text{ V}$

Verification:

$$V_{EQ_1} = V_{EQ_2} = 0\text{ V}$$

$$V_A = V_B = 0.2\text{ V}$$

Applying KCL at the base of  $Q_1$ ,


$$\frac{V_A - V_{BQ_1}}{15} = \frac{V_{BQ_1} - 0}{100k} \rightarrow V_{BQ_1} = 0.17\text{ V}$$

$$\therefore V_{BEQ_1} = 0.17 - 0 = 0.17\text{ V} < 0.5\text{ V}$$

Hence  $Q_1$  will be off

Similarly, we can show  $Q_2$  will be off too, as it has the same parameters.

**Case (0,1):**

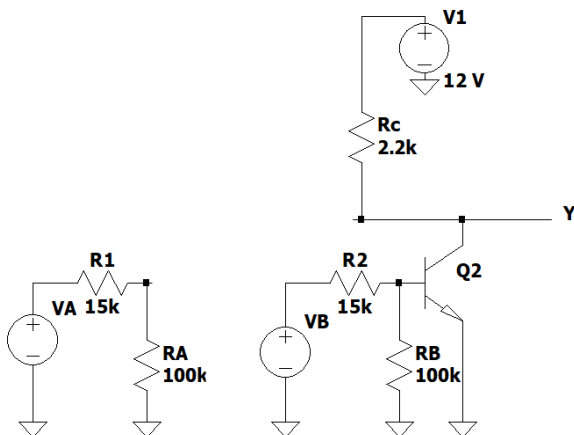

Since  $Q_2$  will be on, we can assume it will be in saturation.

$$\therefore V_{CEQ_2} = 0.2\text{ V}$$

$$\therefore V_Y = V_{CEQ_2} = 0.2\text{ V}$$

Verification:


$$I_{CQ_2} = \frac{12 - V_Y}{2.2} = 5.363\text{ mA}$$

$$I_{BQ_2} = I_{R_2} - I_{R_B} = \frac{12 - V_{BQ_2}}{15} - \frac{V_{BQ_2} - 0}{100} \\ = \frac{12 - 0.8}{15} - \frac{0.8}{100} = 0.738\text{ mA}$$

$$\therefore \beta_{Q_2} = \frac{I_{C_{Q_2}}}{I_{B_{Q_2}}} = \frac{5.363}{0.738} = 7.27 < \beta_F(30)$$

Case (1,0): Same as Case (0,1) since both BJTs' parameters are identical.

Case (1,1):

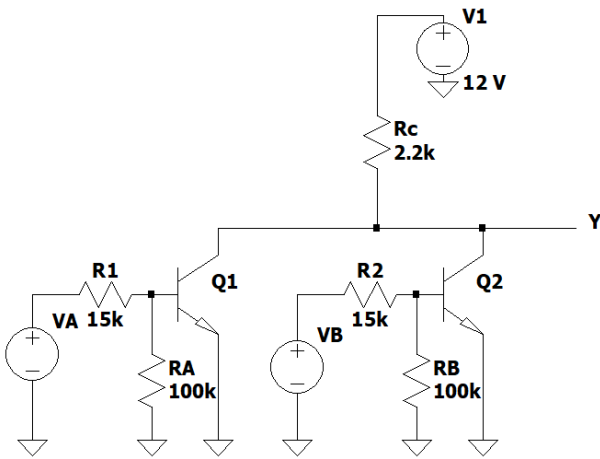

$$V_Y = V_{CE_{Q_1}} = V_{CE_{Q_2}} = 0.2 \text{ V}$$

Verification:

KCL at Y,

$$I_{R_C} = I_{C_{Q_1}} + I_{C_{Q_2}} \rightarrow \frac{12-0.2}{2.2} = 2 \times I_{C_{Q_1}} \rightarrow I_{C_{Q_1}} = 2.681 \text{ mA}$$

$$I_{B_{Q_1}} = I_{B_{Q_2}} = 0.738 \text{ mA [Similarly as in Case (0,1)]}$$

$$\beta_{Q_1} = \beta_{Q_2} = \frac{I_{C_{Q_1}}}{I_{B_{Q_1}}} = 3.63 < \beta_F(30)$$

Case	$V_Y$
0,0	12
0,1	0.2
1,0	0.2
1,1	0.2

b) High threshold = min (12) = 12 V, Low threshold = max (0.2, 0.2, 0.2) = 0.2 V



c) Applying KCL at the base of  $Q_2$ ,  $I_{B_{Q_2}} = I_{R_2} - I_{R_B} = \frac{12-0.8}{15} - \frac{0.8}{2 \times 100} = 0.742 \text{ mA}$

Now,  $\beta_{0,1} = \frac{(I_{C_{Q_2}})_{0,1}}{0.742} = \frac{5.363}{0.742} = 7.23 < \beta_F(30) \text{ \& } \beta_{1,1} = \frac{(I_{C_{Q_2}})_{1,1}}{0.742} = \frac{2.681}{0.742} = 3.61 < \beta_F(30)$

Thus, it will still satisfy saturation mode conditions for (1,1) & (0,1).


## Exercise 2

**Solution:**

**Step 1:**

Case	BJT Q1
0	Cutoff
1	Saturation

**Case 0:**

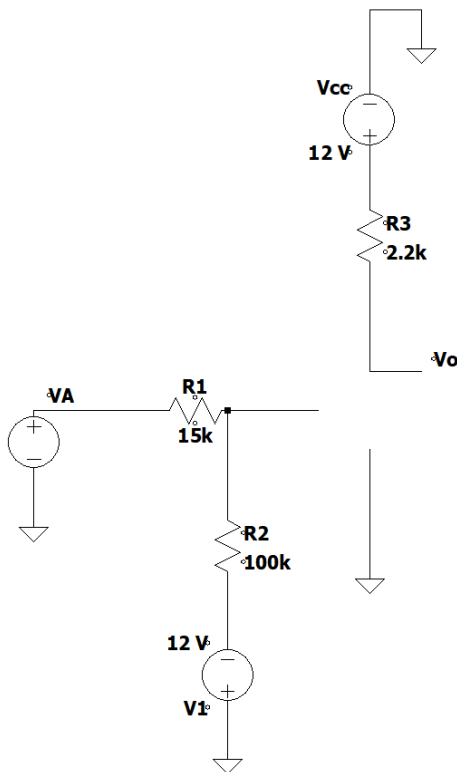

**Step 2:**

$$I_B = I_C = I_E = 0$$

$$V_o = V_{CC} = 12 \text{ V}$$

$$I_{R1} = I_{R2} = \frac{V_A - (-12)}{R_1 + R_2} = \frac{0.2 + 12}{15 + 100} \text{ mA}$$

$$= 0.106 \text{ mA}$$

$$V_A = 0.2 \text{ V}, V_1 = -12 \text{ V}$$

Current flows only through  $R_1$  &  $R_2$


**Step 3:**

$$P_o = (V_A - V_1) \times I_{R1} = (0.2 - (-12)) \times$$

$$0.106 \text{ mW}$$

$$= 1.2932 \text{ mW}$$

## Case 1:

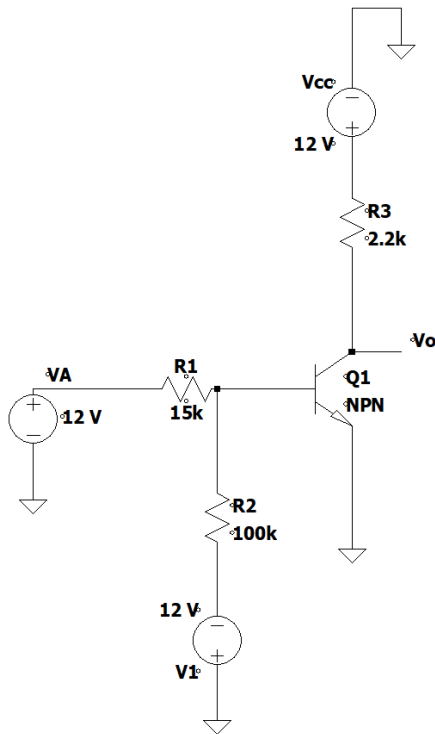

### Step 2:

$$V_O = V_{CE} = 0.2 \text{ V}, V_B = V_{BE} = 0.8 \text{ V}$$

$$I_{R1} = \frac{V_A - V_B}{15} = \frac{12 - 0.8}{15} \text{ mA} = 0.747 \text{ mA}$$

$$I_{R2} = \frac{V_B - (-12)}{100} = \frac{0.8 + 12}{100} \text{ mA} = 0.128 \text{ mA}$$

$$\text{Using KCL, } I_B = I_{R1} - I_{R2} = 0.619 \text{ mA}$$

$$I_C = \frac{V_{CC} - V_O}{2.2} = \frac{12 - 0.2}{2.2} \text{ mA} = 5.363 \text{ mA}$$

$I_{R2}$  flows between  $V_A$  &  $-12 \text{ V}$

$I_B$  flows between  $V_B$  &  $0 \text{ V}$

$I_C$  flows between  $V_{CC}$  &  $0 \text{ V}$

### Step 3:

$$\begin{aligned} \therefore P_1 &= (V_A - (-12)) \times I_{R1} + (V_B - 0) \times I_B + (V_{CC} - 0) \times I_C \\ &= (12 + 12) \times 0.747 + (0.8 - 0) \times 0.619 + (12 - 0) \times 5.363 \\ &= 82.7792 \text{ mW} \end{aligned}$$

$$\therefore \text{Maximum power dissipation} = P_1 = 82.7792 \text{ mW}$$


$$\therefore \text{Average power dissipation} = \frac{P_0 + P_1}{2} = 42.0362 \text{ mW}$$

### Exercise 3

**Solution:**

Both  $Q_1$  &  $Q_2$  will be off for (0,0).

**Step 1:**

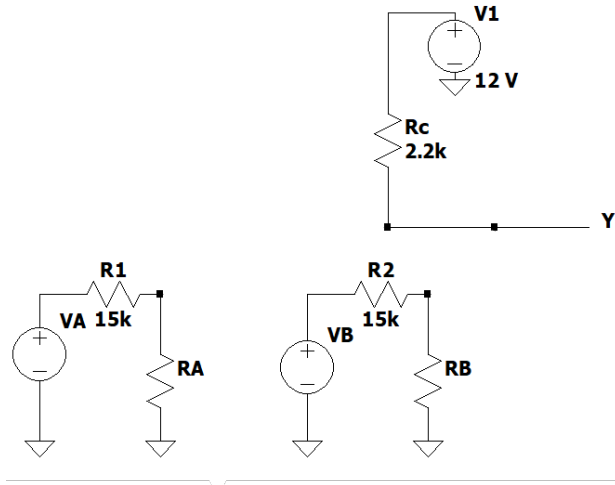

**Step 2:**

$$I_{R_C} = 0 \text{ (open circuit)}$$

$$V_A = V_B = 0.2 \text{ V}$$

**Step 3:**

$$P_{0,0} = 2 \times (V_A - 0) \times I_{R_A} = 2 \times 0.2 \times \frac{0.2 - 0}{15 + R_A}$$

$$\rightarrow 0.5 = 0.4 \times \frac{0.2}{15 + R_A}$$

$$\therefore R_A = R_B = 145 \text{ k}\Omega$$

### Exercise 4

**Solution:**

**Step 1:**

$$V_{OH} = 11.5 \text{ V}, V_{OL} = 0.2 \text{ V}$$

**Step 2:**

Determination of  $V_{IH}$ :

$V_{IH}$  is the lowest input voltage that would drive the RTL Not gate loads to forward active mode from saturation. Thus, the marginal condition here is,

$$\beta_{loads} = \beta_F = 30$$

For saturation mode, we know,  $V_{BE} = 0.8 \text{ V}, V_{CE} = 0.2 \text{ V}$

$$\text{Thus, } I_{B_{loads}} = \frac{V_{IH} - V_B}{0.45} = \frac{V_{IH} - (0.8 - 0)}{0.45} = \frac{V_{IH} - 0.8}{0.45}$$

$$\text{And } I_{C_{loads}} = \frac{V_{CC} - V_{CE}}{0.64} = \frac{3.6 - 0.2}{0.64} = 5.3125 \text{ mA}$$

$$\text{Now, } \beta_{loads} = \frac{I_{C_{loads}}}{I_{B_{loads}}} = 30 \rightarrow \frac{V_{IH} - 0.8}{0.45} = \frac{5.3125}{30} \rightarrow V_{IH} = 0.88 \text{ V}$$

Determination of  $V_{IL}$ :

$V_{IL}$  is the highest input voltage that would turn the RTL Not gates on & violate cutoff condition of  $V_{BE} < 0.5 \text{ V}$  So, the marginal  $V_{BE} = V_B = 0.5 \text{ V}$

Since  $V_E = 0 \text{ V}$ ,

$$V_{BE} = V_B = V_{IL} - I_B \times 0.45 = V_{IL} - 0 \times 0.45 = V_{IL} (\text{In cutoff } I_B = 0)$$

Thus,  $V_{IL} = 0.5 \text{ V}$

**Step 3:**

$$N_H = V_{OH} - V_{IH} = 3.5 - 0.88 = 2.62 \text{ V}$$

$$N_L = V_{IL} - V_{OL} = 0.5 - 0.2 = 0.3 \text{ V}$$

$$\therefore N_M = \min(N_H, N_L) = 0.3 \text{ V}$$

## Exercise 5

**Solution:**

a) **Step 1:**

The current from the driver circuit is going outward to the NOT gate loads. Hence, the condition for maximum fanout is supply & demand current balance.

**Step 2:**

Case (1,1):

Both  $T_1$  &  $T_2$  on, output =  $V_{OL}$

$$\text{Supply current from the driver, } I_{RC} = \frac{V_{CC} - V_{OL}}{R_C} = \frac{3.6 - 0.2}{0.64} = 5.3125 \text{ mA}$$

Loads will be cutoff due to low voltage at the base. Thus, demand current,  $I_L = 0$ .

$$\therefore \text{Fanout} = \infty$$

Case (0,1):

$T_1$  off &  $T_2$  on, output =  $V_{OH}$

Supply current from the driver,  $I_{RC} = \frac{V_{CC} - V_{OH}}{R_C} = \frac{3.6 - 1.3}{0.64} = 3.6 \text{ mA}$

Loads will be in saturation due to high voltage at the base. Thus, demand

current,  $I_L = \frac{V_{OH} - V_B}{R_B}$

$$= \frac{1.3 - 0.8}{0.45} = 1.11 \text{ mA}$$

$$\therefore \text{Fanout} = \text{floor} \left( \frac{I_{RC}}{I_L} \right) = 3$$

Case (1,0): Same as Case (0,1)

Case (1,1): Same as Case (0,1)

**Step 3:**  $\therefore \text{Maximum fanout} = \min(\infty, 3) = 3$

b) Applying KCL at output node,

$$I_{RC} = N \times I_L \rightarrow \frac{V_{CC} - V_o}{R_C} = 5 \times \frac{V_o - V_B}{R_B} \rightarrow \frac{3.6 - V_o}{0.64} = 5 \times \frac{V_o - 0.8}{0.45} \rightarrow V_o = 1.145 \text{ V}$$

c) For  $(\beta_F)_{min}$ ,  $V_{CE} = 0.2 \text{ V}$ ,  $V_{BE} = 0.8 \text{ V}$

$$I_B = \frac{V_o - V_B}{R_B} = \frac{1.145 - 0.8}{0.45} = 0.767 \text{ mA}$$

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{3.6 - 0.2}{0.64} = 5.3125 \text{ mA}$$

$$\therefore (\beta_F)_{min} = \frac{I_C}{I_B} = 6.93$$

$$P_{loads} = 5 \times (V_{CC} - 0) \times I_C = 5 \times 3.6 \times 5.3125 = 95.625 \text{ mW}$$

$$\text{d) } P_{driver} = \Delta V_{(base-ground)_A} \times I_{B_A} + \Delta V_{(base-ground)_B} \times I_{B_B} + \Delta V_{CC-ground} \times I_{RC}$$

$$= (V_A - 0) \times I_{B_A} + (V_B - 0) \times I_{B_B} + (V_{CC} - 0) \times I_{RC}$$


$$= (3.6 - 0) \times \frac{3.6 - 0.8}{0.45} + (3.6 - 0) \times \frac{3.6 - 0.8}{0.45} + (3.6 - 0) \times \frac{3.6 - V_{OL}}{R_C}$$

$$= 2 \times 3.6 \times \frac{2.8}{0.45} + 3.6 \times \frac{3.6 - 0.2}{0.64} = 63.925 \text{ mW}$$

$$\text{e) } Y = \overline{A + B}$$

## Exercise 6

Solution:

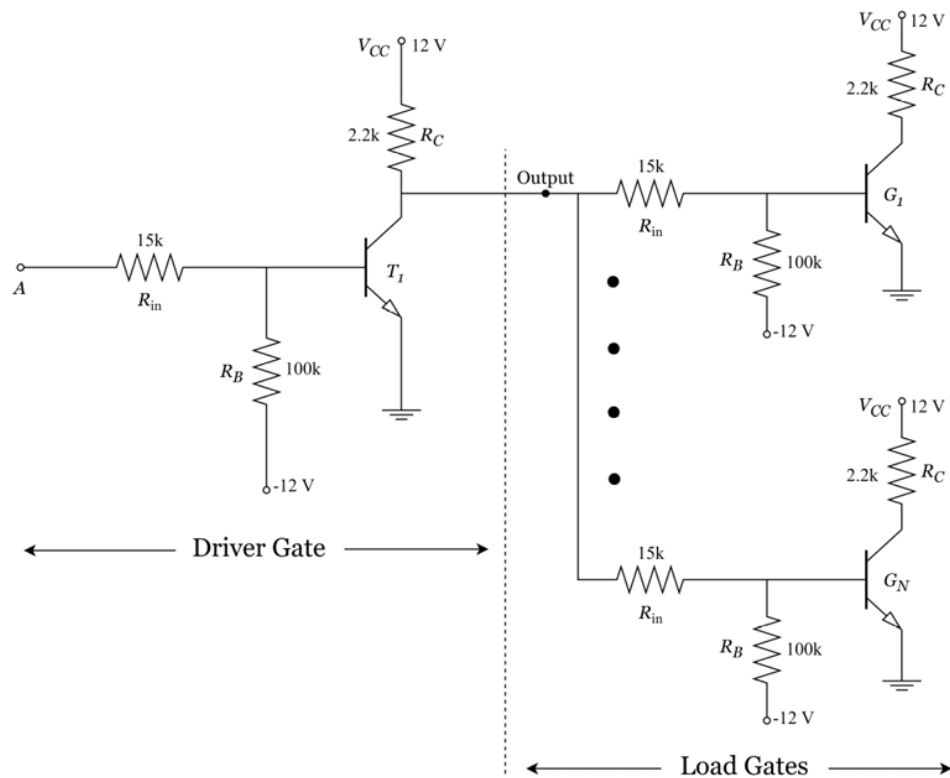

### a) Step 1:

The current from the driver circuit is going outward to the NOT gate loads. Hence, the condition for maximum fanout is supply & demand current balance.

### Step 2:

Case (0):

$T_1$  off, loads on due to high voltage at base.

$$\text{Supply current from driver, } I_{RC} = \frac{12 - V_{OH}}{R_C} = \frac{12 - 10}{2.2} = 0.91 \text{ mA}$$

$$\text{Demand current, } I_L = \frac{V_{OH} - V_B}{R_{in}} = \frac{10 - 0.8}{15} = 0.61 \text{ mA}$$

$$\therefore \text{Fanout} = \text{floor} \left( \frac{0.91}{0.61} \right) = 1$$

Case (1):

$T_1$  on, loads off due to low voltage at base.

$$\text{Supply current from driver, } I_{RC} = \frac{12 - V_{OL}}{2.2} = 5.363 \text{ mA}$$

$$\text{Demand current, } I_L = \frac{V_{OL} - (-12)}{15 + 100} = 0.106 \text{ mA}$$

$$\therefore \text{Fanout} = \text{floor} \left( \frac{5.363}{0.106} \right) = 50$$

**Step 3:**

$$\therefore \text{Maximum fanout} = \min(50, 1) = 1$$

b) KCL at output of driver,

$$I_{R_C} = \frac{12 - V_o}{R_C} = N \times I_L = 2 \times \frac{V_o - V_B}{R_{in}} \rightarrow \frac{12 - V_o}{2.2} = 2 \times \frac{(V_o - 0.8)}{15} \rightarrow V_o = 9.46 \text{ V}$$

c) If the input is high,  $V_{CE} = 0.2 \text{ V}$ . Thus, we have,

$$\begin{aligned} P_{\text{driver}} &= (V_{CC} - 0) \times I_{R_C} + (12 - 0) \times I_B + (12 - (-12)) \times I_{R_B} \\ &= (V_{CC} - 0) \times I_{R_C} + (12 - 0) \times I_B + (12 - (-12)) \times I_{R_B} \\ &= 12 \times \frac{12 - 0.2}{2.2} + 12 \times \left( \frac{12 - 0.8}{15} - \frac{12.8}{100} \right) + 12.8 \times \frac{12.8}{100} \\ &= 74.86 \text{ mW} \end{aligned}$$

$$\begin{aligned} \text{d) } P &= (V_{CC} - 0) \times I_{R_C} + (0.2 - (-12)) \times I_{R_{in}} = (12 - 0) \times \frac{12 - 9.46}{2.2} + \\ &12.2 \times \frac{0.2 - (-12)}{15 + 100} = 15.15 \text{ mW} \end{aligned}$$

e) **Step 1:**

$$V_{OH} = 10 \text{ V}, V_{OL} = 0.2 \text{ V}$$

**Step 2:**

Determination of  $V_{IH}$ :

$V_{IH}$  is the lowest input voltage that would drive the RTL NOT gate loads to forward active mode from saturation. Thus, the marginal condition here is,

$$\beta_{\text{loads}} = \beta_F = 30$$

$$\text{Now, } I_{C_{\text{load}}} = \frac{V_{CC} - V_{OL}}{R_C} = \frac{12 - 0.2}{2.2} = 5.363 \text{ mA}$$

$$I_{B_{\text{load}}} = \frac{V_{IH} - 0.8}{15} - \frac{0.8 - (-12)}{100}$$

$$\therefore \beta_F = 30 \rightarrow \frac{5.363}{\frac{V_{IH} - 0.8}{15} - \frac{12.8}{100}} = 30 \rightarrow V_{IH} = 5.4015 \text{ V}$$

Determination of  $V_{IL}$ :

$V_{IL}$  is the highest input voltage that would turn the RTL NOT gate on & violate cutoff condition of  $V_{BE} < 0.5 V$ . So, the marginal  $V_{BE} = V_B = 0.5 V$   
KCL at base,

$$\frac{V_{IL} - V_B}{15} = \frac{V_B - 0}{100} \rightarrow V_{IL} = \frac{V_B}{100} \times 15 + V_B = 0.575 V$$

**Step 3:**

$$N_H = V_{OH} - V_{IH} = 4.5985 V$$

$$N_L = V_{IL} - V_{OL} = 0.375 V$$

$$N_M = \min(N_H, N_L) = 0.375 V$$

## Exercise 7

Solution:

a)  $Y = \overline{A + B} \cdot C$

b) **Step 1:**

Current from load flows toward driver circuit. Thus, the condition for maximum fanout is determined by driving driver BJTs into forward active mode.

Maximum current from load comes when  $C=0$ . Thus, we will ignore  $C=1$  cases.

**Step 2:**

Case (0,0):

High voltage at the negative terminal of  $D_1$ , thus it remains off.

$$\therefore \text{Fanout} = \infty$$

Case (0,1):

$$V_X = V_{OL} = 0.2 V, D_1 \text{ on}$$

$$\text{Now, } I_{C_{Q2}} = I_{C_{RC}} + N \times I_{D1} = \frac{12-0.2}{2.2} + N \times \frac{12-0.2-0.7}{100+0.25} = 5.363 + 1.11N$$

$$I_{B_{Q2}} = \frac{12-0.8}{15} - \frac{0.8-0}{100} = 0.739 \text{ mA}$$



$$\text{Thus, } \beta_{max} = \frac{I_{CQ2}}{I_{BQ2}} = \beta_F = 25 \rightarrow 5.363 + 1.11N = 25 \times 0.739$$

$$\rightarrow N = \text{floor}(13.112) = 13$$

Case (1,0): Same as Case (0,1)

Case (1,1):

$$V_X = V_{OL} = 0.2 \text{ V}, D_1 \text{ on}$$

$$I_{CQ1} + I_{CQ2} = 2I_{CQ1} = I_{RC} + N \times I_{D1} = \frac{12-0.2}{2.2} + N \times \frac{12-0.2-0.7}{100+0.25}$$

$$= 5.363 + 1.11N$$

$$\therefore I_{CQ1} = \frac{1}{2}(5.363 + 1.11N)$$

$$I_{BQ1} = I_{BQ2} = \frac{12-0.8}{15} - \frac{0.8-0}{100} = 0.739 \text{ mA}$$

$$\text{Thus, } \beta_{max} = \frac{I_{CQ2}}{I_{BQ2}} = \beta_F = 25 \rightarrow \frac{1}{2}(5.363 + 1.11N) = 25 \times 0.739$$

$$\rightarrow N = \text{floor}(31.587) = 31$$

**Step 3:**

$$\therefore \text{Maximum fanout} = \min(\infty, 13, 31) = 13$$

c) Maximum power will be dissipated in the case (1,1,0). This case turns on all the diodes & BJTs.

$$P_{max} = P_{driver} + P_{load} = (12 - 0.2) \times I_{RC} + (12 - 0) \times I_{R5}$$

$$= 12 \times \left[ \frac{12-0.2}{2.2} + \frac{12-V_Y}{100} \right]$$

KCL at Y,

$$\frac{(12-V_Y)}{100} = \frac{V_Y-0.2-0.7}{.25} + \frac{V_Y-0-0.7}{.25} \rightarrow V_Y = 0.81 \text{ V}$$

$$\therefore P_{max} = 65.7 \text{ mW}$$