CSE 350 Digital Electronics and Pulse Techniques

DTL-Noise Margin, Fanout, Power Dissipation



Course Instructor: Shomen Kundu (SDU)

Mail: shomen.kundu@bracu.ac.bd

Desk: 4N166

CSE 350

DTL

 β_{min} = the minimum value of β_F of the switching transistor T, That will keep the circuit operation error free.

case(1), (2) and (3) will not help us to determine the β_{min} because in these case the transistor is turn off.


However for case (4) transistor is on and operates in saturation mode, Therefore, to maintain correct operating we must choose a value of

$$\beta_{min} = \frac{I_C}{I_B} = \frac{2.182}{0.4} = 5.46$$



 NM calculation of DTL is not similar to the RTL circuit.





Example: IF all the inputs are high, what is the magnitude of noise voltage which will cause the gate to malfunction?

correct operating condition when all inputs are high.

Case (4). D1, D2 off.

D3 and D4 ON


Sat

Inspiring Excellence

The circuit will malfunction if it starts operating in case (1) conditions.

D1, D2 on, D3, D4, T off.

 If D1 and D2 starts conducting, they will have precedence over D3, D4 and T because of Ower resistance at that direction.




So the circuit will malfunction when the voltage difference VA and VP is equal to cut in voltage of diode.

If VA = 1.6V, then anode voltage of D1 will have enough voltage to start conducting. Hence circuit will malfunction.

$$V_N + 5 = 1.6 \Rightarrow V_N = -3.4 V$$

  $V_N = 3.4 \ (taking magnitude)$
 $V_{NM} = 3.4 V$





$$V_A = 1.6 \text{ V}$$
 $V_P = 2.2 \text{ V}$ $V_P = 0.6 \text{ V}$


Q. If one of the inputs is low and others are high, then what magnitude of noise voltage at low input terminal will cause the transistor to malfunction?

valid operation: case (2) D1 on, D2, D3, D4, T off.

The circuit will malfunction if D3, D4 and T start conducting or turned on.

As long as D1 is on any increment in noise voltage at node A will also increase the voltage at Vp. Because, the difference between anode and cathode terminal should be 0.7 V for conducting diode D1.

Inspiring Excellence

 

DTL NAND Gate


If we increase Vp upto 1.7 V for conducting, then D3, D4 and T will turn on.

$$V_P + V_N = 1.7$$


 $\Rightarrow V_N = 1.7 - 0.9 = 0.8 V$

Low noise margin = 0.8 V


Finally, total noise margin, NM

 

Inspiring Excellence

 

Different from RTL

 




Case 1: Output voltage of driver is high (5V).

If $V_o = 5 V$, then the demand current of the load circuit is zero.

Therefore, we can connect as many load circuit as we wish for this case.

Max Fanout = ∝

 



...............

Case 2: Output voltage of driver is low.(0.2 V)


Individual load circuit delivers IL current

IL = standard load $I'_{C} = No \ load \ collector \ current$ $I_{C} = Total \ collector \ current$

If the number of fanout = N,

Inspiring Excellence

 
Total collector current, $I_C = I'_C + N * I_L$



Constraint: Since the transistor T in driver circuit in saturation mode, the collector current cannot cross a certain value. That will push the transistor T from saturation to forward active mode.

$$eta_{forced} > eta_{F}(Not \ in \ saturation)$$
 $eta_{forced} pprox eta_{F} \ (Edge \ of \ sat. \ and \ F > A]$
 $I_{Cmax}, = eta_{F} * I_{B}$
 $= 30 * 0.4$
 $= 12 \ mA$



 



CSE 350

$$I_{Cmax} = I'_{C} + N * I_{L}$$
, $Floor(N)$
will be the max f anout

Standard load ,
$$I_L=rac{5-0.9}{5k}=0.82~mA$$

No load collector current,

$$I_C' = \frac{5 - 0.2}{2.2k} = 2.182 \, mA$$



Now,
$$12 = 2.182 + N * 0.82$$

 $\Rightarrow N = 11.97 \approx 11 (Floor)$

We cannot choose 12, because in that case collector current will overflow and make transistor T to operate in Forward Active.


Fanout =
$$Min(\infty, 11) = 11$$



Power dissipation for DTL circuit.

Case 1:
$$V_o = 0.2 V$$

  $V_1 = V_2 = 5 V$
 $D_1, D_2, \rightarrow OFF$
 $D_3, D_4, T \rightarrow ON$
 $\frac{5 - 2.2}{1} = 0.56 mA$
 $I_c = \frac{5 - 0.2}{2.2k} = 2.182 mA$






Power

$$P_1 = (5 - 0) * 0.56 mA = 2.8 mW$$

  $P_2 = (5 - 0) * 2.182 mA = 10.91 mW$
 $P = P_1 + P_2 = 13.71 mW$






Power dissipation for DTL circuit.

Case 2:
$$V_o = 5 V$$

  $V_1 = V_2 = 0.2 V$
 $D_1, D_2, \rightarrow ON$
 $D_3, D_4, T \rightarrow OFF$
 $\frac{5 - 0.9}{5k} = 0.82 mA$
 $I_{D1} = I_{D2} = \frac{I_1}{2} = 0.41 mA$






Power dissipation for DTL circuit.

$$P1 = (5 - 0.2) * 0.41 mA = 1.968 mW$$

 $P2 = (5 - 0.2) * 0.41 mA = 1.968 mW$

$$P = P1 + P2 = 3.936 \text{ m W}$$

 



Case 3:
$$V_o = 5 V$$

 $V_1 = 0.2 V, V_2 = 5 V$

Case 4:
$$V_o = 5 V$$

 $V_1 = 5V, V_2 = 0.2 V$

Try yourself. Both will give the same result as the case 2.



CSE 350