

CSE 350

Digital Electronics and Pulse Techniques

Diode Logic


Course Instructor: Shomen Kundu (SDU)

Mail: shomen.kundu@bracu.ac.bd
Desk: 4N166



Inspiring Excellence


Abstract of Logic Gate:

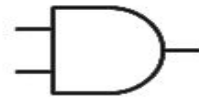

AND




NAND

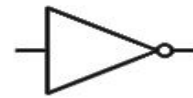

NOT



OR

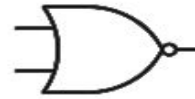

NOR






XOR




XNOR

This gates are abstract, because they just represent logical operations.

Logic families

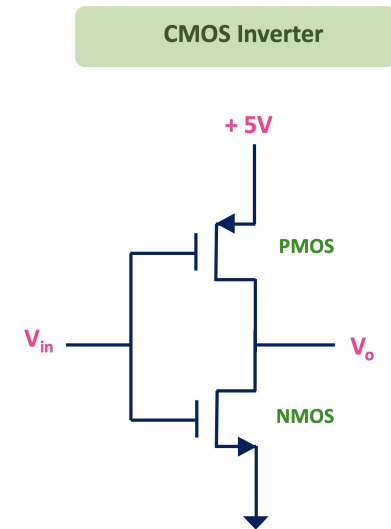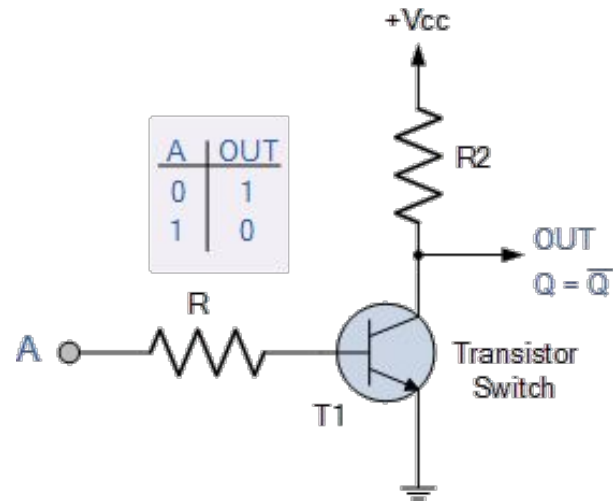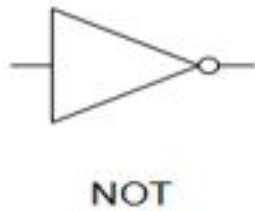

Logic families

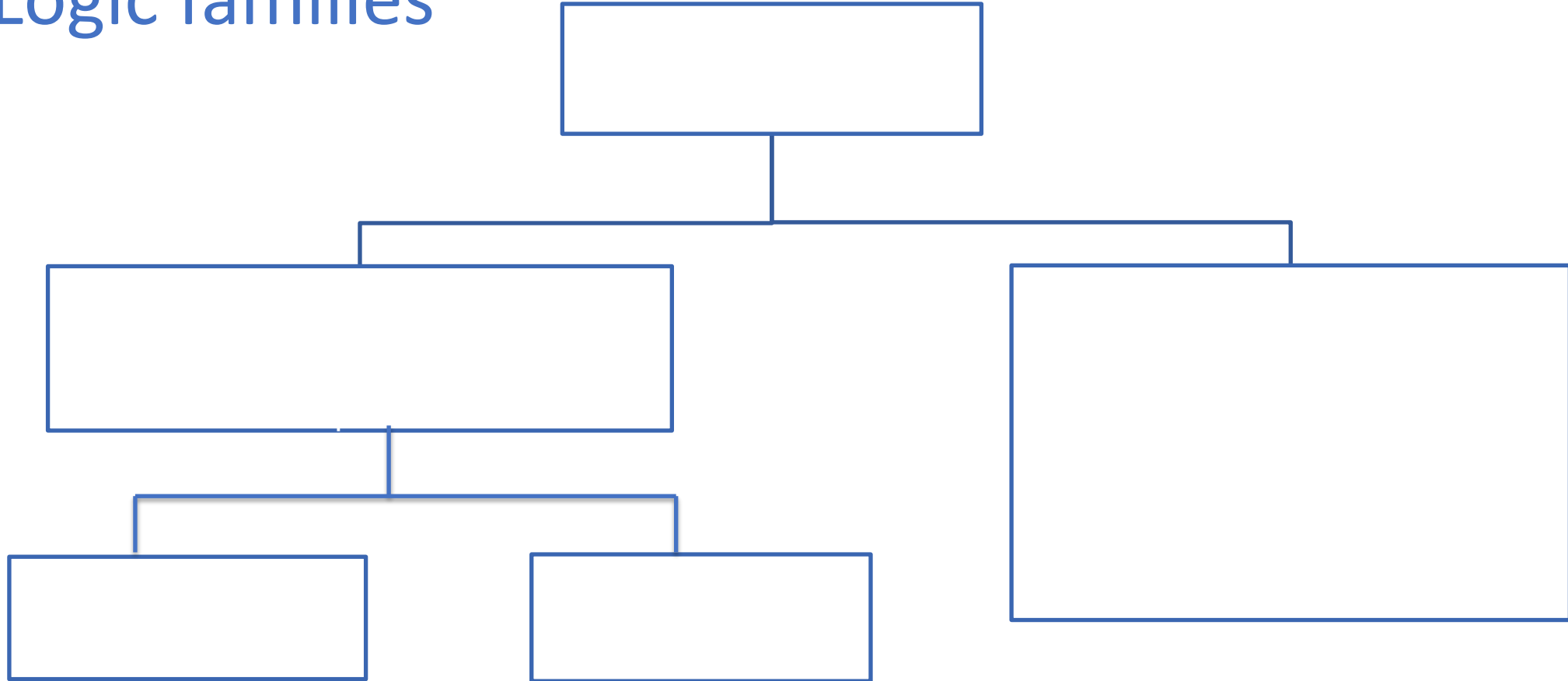

Logic families

Saturated Logic Family: Uses Saturation & Cutoff region of a BJT for implementation of logic states.

- ❑ Resistor Transistor Logic (RTL)
- ❑ Diode Transistor Logic (DTL)
- ❑ Direct Coupled Transistor Logic (DCTL)
- ❑ Integrated Injection Logic (IIL)
- ❑ High Threshold Logic (HTL)
- ❑ Transistor-Transistor Logic (TTL)

Unsaturated Logic Family: Uses Active & Cutoff region of a BJT for implementation of logic states.

- ❑ Schottky TTL
- ❑ Emitter Coupled Logic (ECL)



Logic families

Unipolar Logic Family: JFET, MOSFET etc. single charge carrier-based transistor logic families.

- PMOS Logic Family
- NMOS Logic Family
- CMOS Logic Family



Diode logic

OR gate and AND gate Design Techniques,

- For each input we need a **series resistance** and a **diode**
- Output will be connected with GND or VDD
- For OR gate output will be connected to the GND via **pull down** resistance
- For AND gate output will be connected to the VDD via **pull up** resistance.
- Series resistance will be small.
- Pull up / Pull down resistance will be large.


Diode logic

OR Gate

Series and pull down resistance can be chosen as


$$R_s = 1\text{ k}\Omega$$

$$R_{pd} = 100\text{ k}\Omega$$

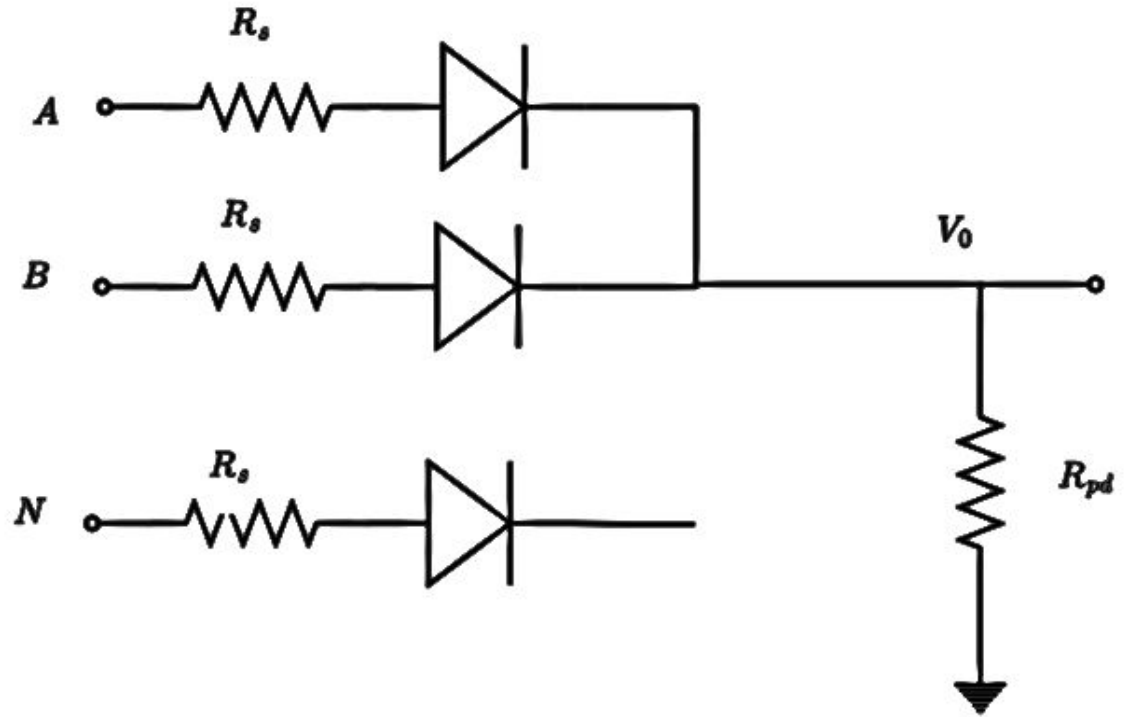

Diode logic

Two input OR Gate

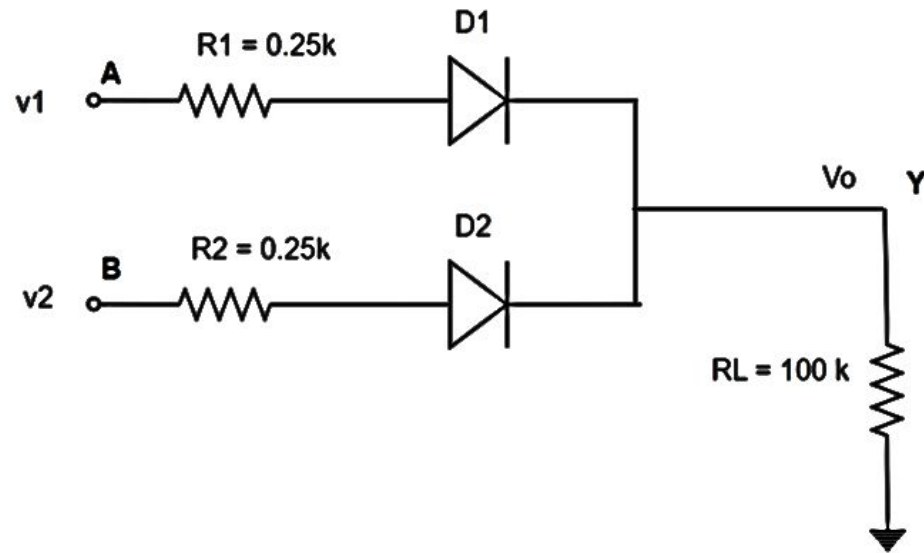

A	B	V1	V2	V _o	Y
0	0	0V	0V		
0	1	0V	5V		
1	0	5V	0V		
1	1	5V	5V		

Assume: Logic 1 means 5 V on input side. Logic 0 means 0 voltage/GND

Diode logic

Case 1: $A = 0, B = 0$



First thing to check whether diodes are on or off.

FACT: We need at least 0.7 V to turn on any diode.

Conclusion: D1 and D2 are OFF.

$$\frac{V_o - 0}{R_L} = i = 0 \Rightarrow V_o = 0 V$$

$$Y = 0 \text{ (logic)}$$

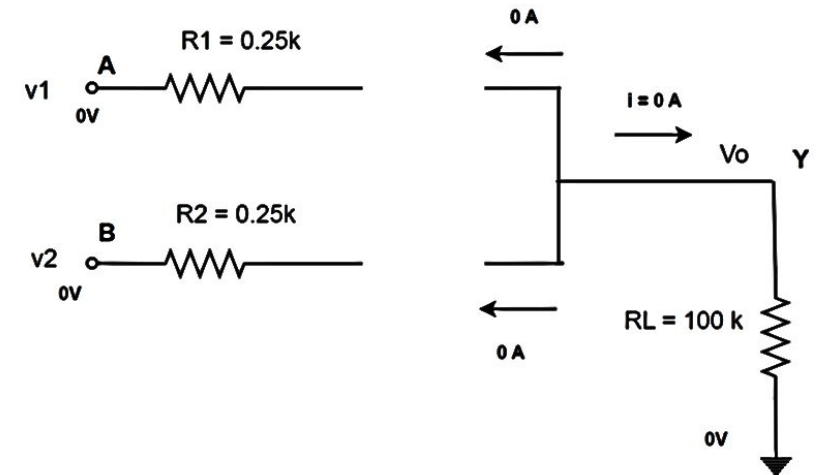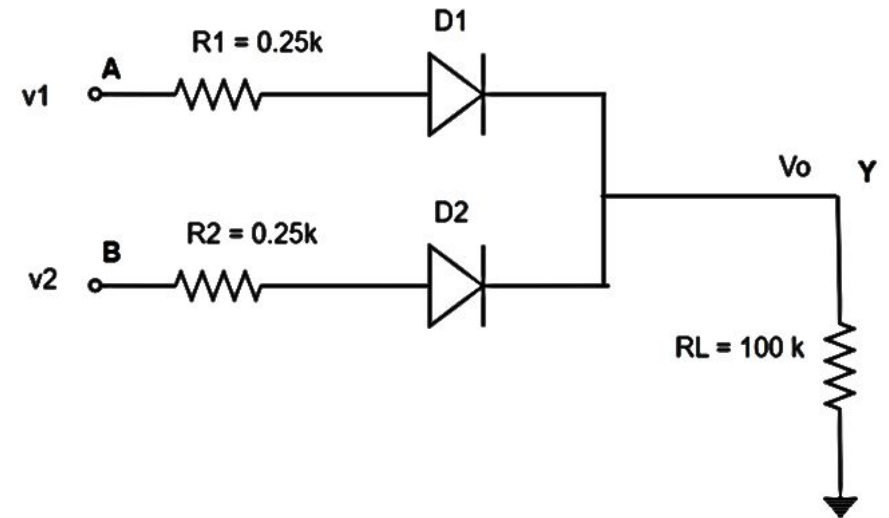

Diode logic


Case 2: $A = 0, B = 1$

First thing to check whether diodes are on or off.

Here: D1 will be OFF and D2 will be ON

$$\frac{V_o - 0}{100k} + \frac{(V_o + 0.7) - 5}{0.25k} = 0 \Rightarrow V_o = 4.2893V$$

$$Y = 1 (\text{logic})$$

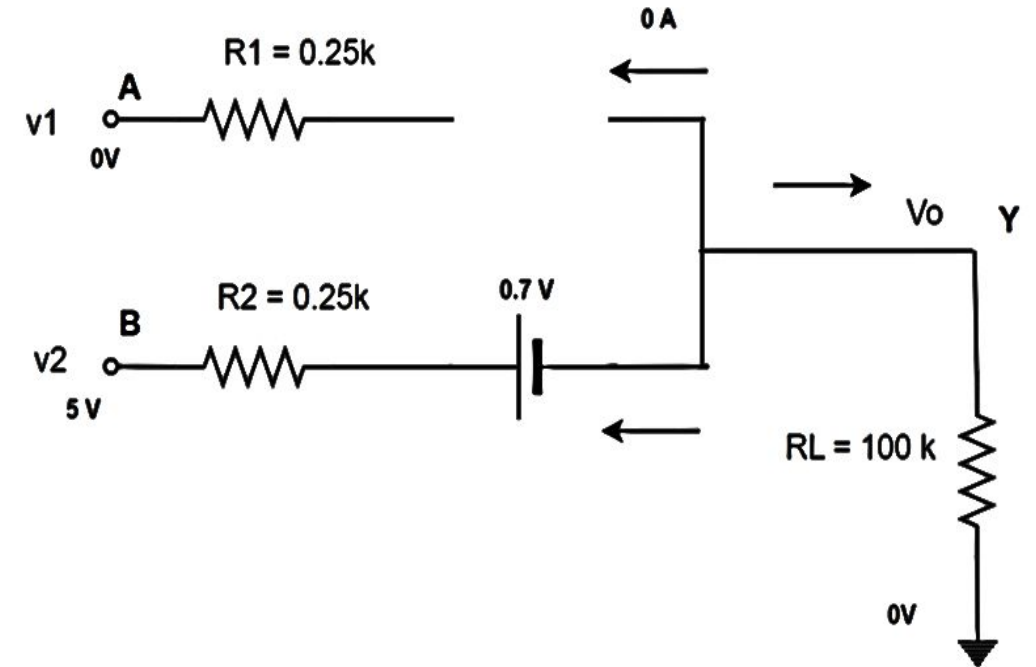

Diode logic


Case 3: $A = 1, B = 0$ (symmetrical to case 1)

First thing to check whether diodes are on or off.

Here: D1 will be ON and D2 will be OFF

$$\frac{V_o - 0}{100\text{ k}} + \frac{(V_o + 0.7) - 5}{0.25\text{ k}} = 0 \Rightarrow V_o = 4.2893\text{ V}$$

$Y = 1$ (*logic*)

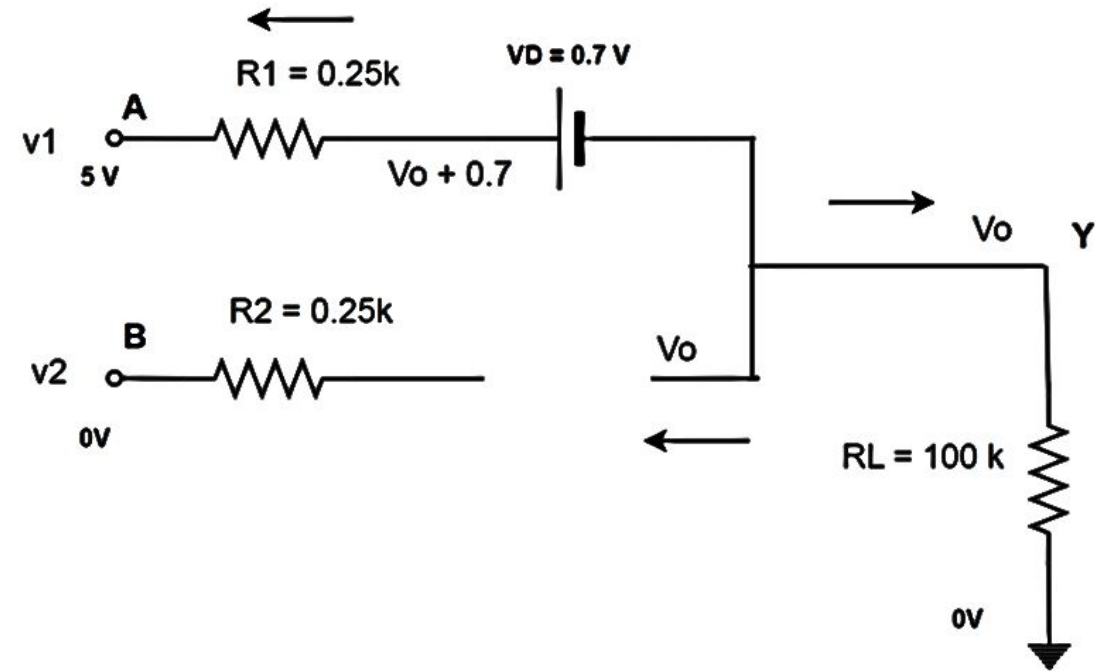

Diode logic


Case 4: $A = 1, B = 1$

First thing to check whether diodes are on or off.

Here: D1 will be ON and D2 will be ON

$$\frac{V_o - 0}{100\text{ k}} + \frac{(V_o + 0.7) - 5}{0.25\text{ k}} + \frac{(V_o + 0.7) - 5}{0.25\text{ k}} = 0$$
$$\Rightarrow V_o = 4.2946\text{ V}$$

$Y = 1$ (logic)

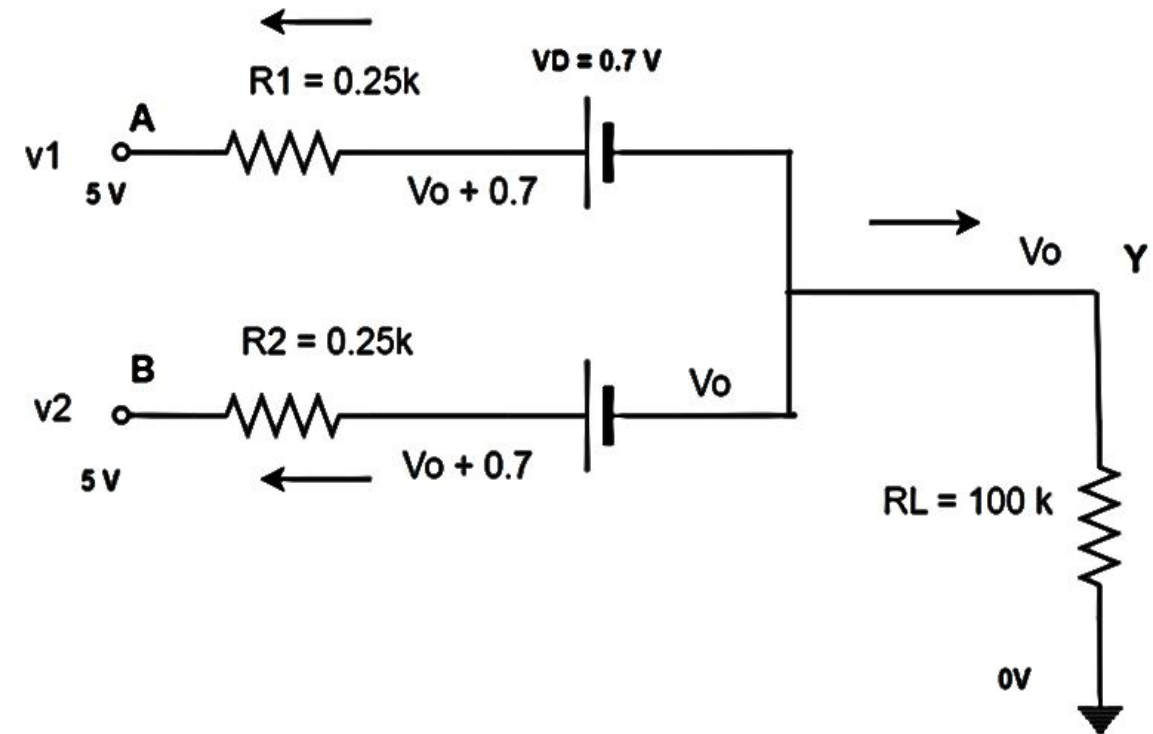

Diode logic

Two input OR Gate Findings

#4.28 V , 4.29 V

logical High and Low can be
Different at input and output side

$V_{OH} = 4.28 \text{ V}$


(lowest of the outputs values
that can be considered as logic 1)

A	B	V1	V2	V _o	Y
0	0	0V	0V	0 V	0
0	1	0V	5V	4.2893V	1
1	0	5V	0V	4.2893V	1
1	1	5V	5V	4.2946 V	1




Power Dissipation Calculation

Theory:

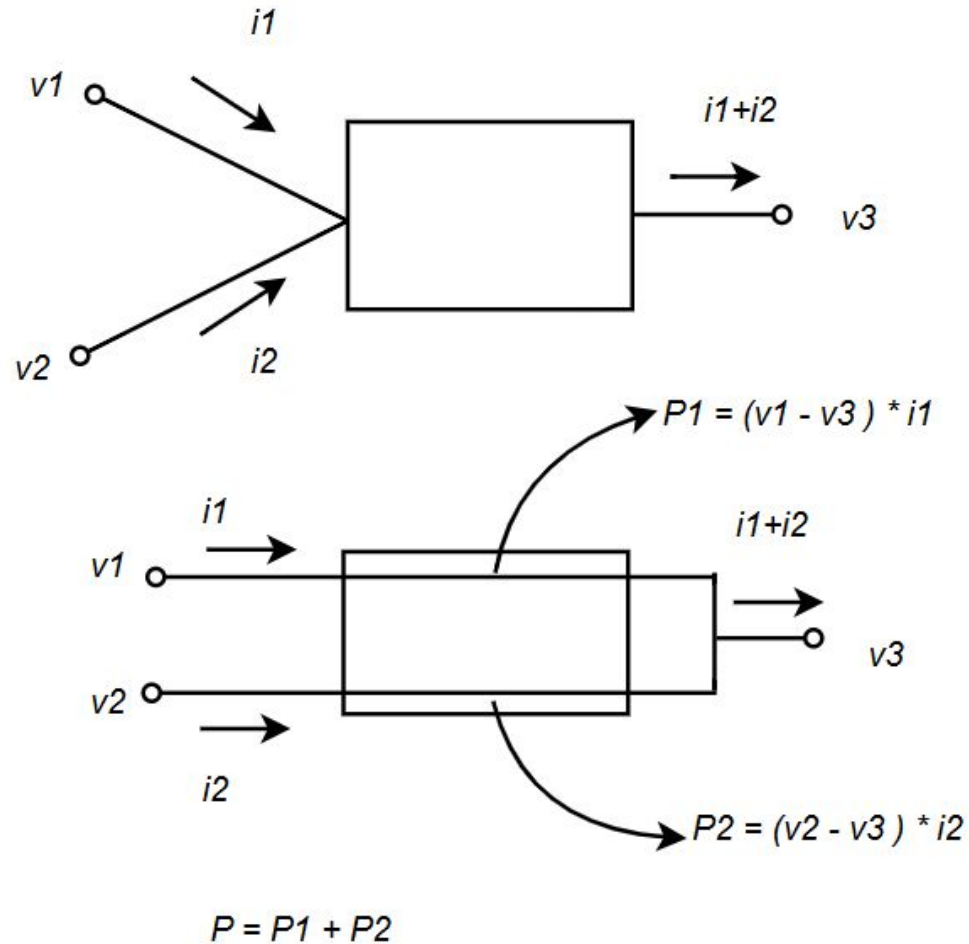

Max Power Dissipation

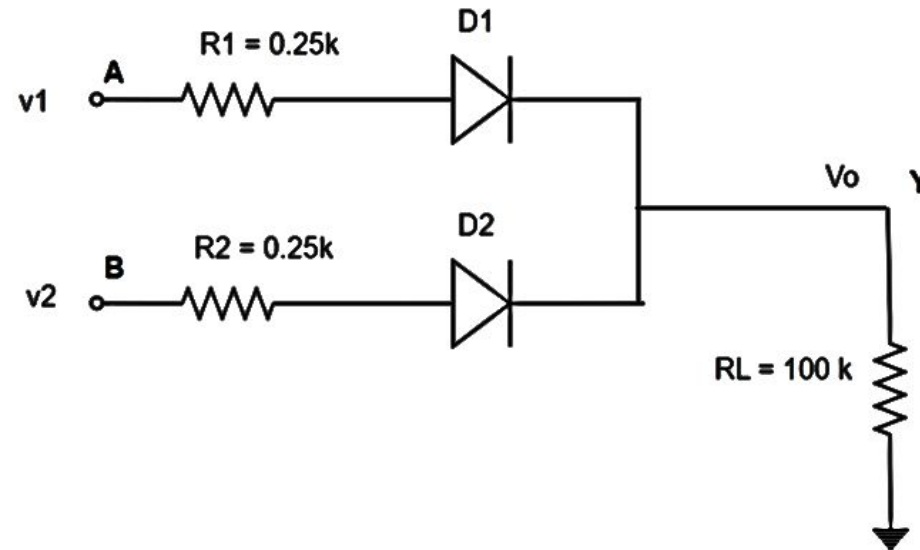Example: Find the max power dissipation of the given circuit.



Max Power Dissipation

Max power dissipation will be in the case 4

$$V_0 = 4.2946 \text{ V}$$


$$i_1 = \frac{5 - (V_0 + 0.7)}{0.25 \text{ k}} = 0.0216 \text{ mA}$$

$$i_2 = i_1$$

$$i_3 = \frac{V_0 - 0}{100 \text{ k}} = 0.042946 \text{ mA}$$


$$P = (5 - 0) * i_1 + (5 - 0) * i_2 = 0.216 \text{ mW}$$
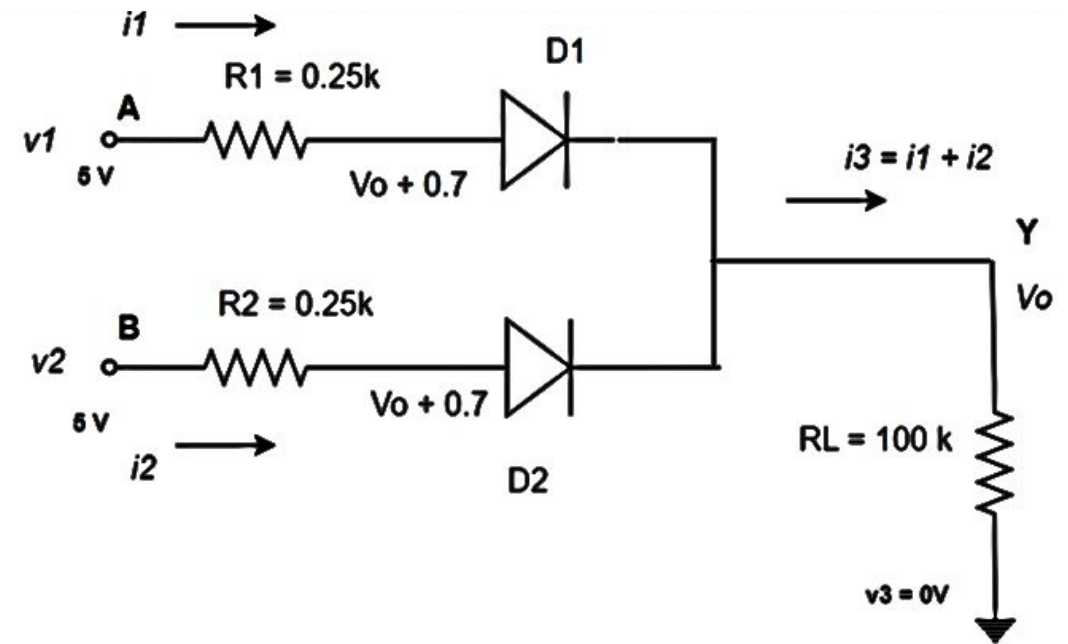
$$\text{Or } P = (5 - 0) * i_3 = 0.216 \text{ mW}$$



Diode logic


AND gate:

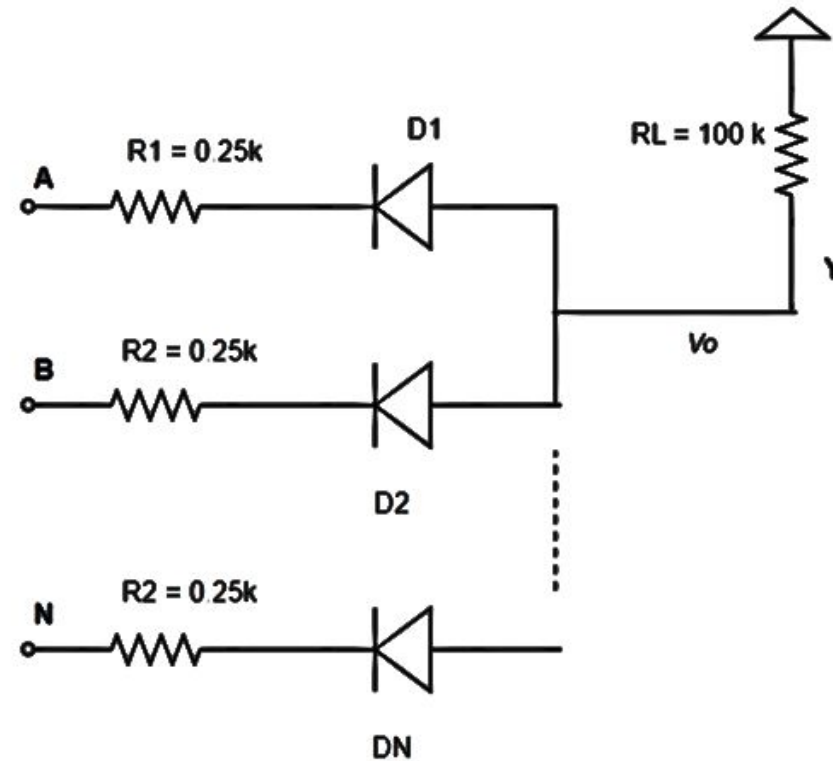

Diode logic

Exercise: Analysis the four possible input and fill the table. Also find the V_{OL} for this circuit.

A	B	V1	V2	Vo	Y
0	0	0V	0V		
0	1	0V	5V		
1	0	5V	0V		
1	1	5V	5V		

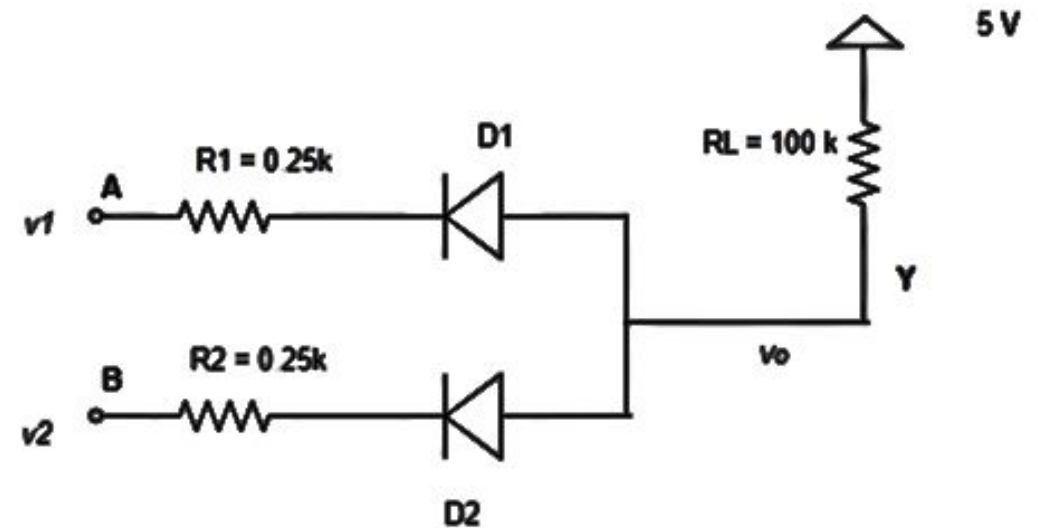

Hints: Logical low voltage at the output side --□ Highest voltage for which the output is considered to be 0 or logic low.

Diode logic

Try yourself,

1. Design a logic circuit, $Y = A(B + C)$ using diode logic.
2. For the given circuit find the maximum power and average power.

