

Solve

BRAC UNIVERSITY

CSE 350

Quiz-4, Section 8

Fall 2024

Marks: 20

Name: _____

ID: _____

1. Design an inverting Schmitt trigger circuit having a center voltage of 4V and Hysteresis width of 1 V. Assume $V_H = +10V$ and $V_L = -10V$. Draw the circuit and transfer curve with proper labeling. [10]

Here, $V_H = +10V$, $V_L = -10V$,

$$V_S = 4V, V_{HW} = 1V$$

$$V_{TH} = V_S + \frac{V_{HW}}{2} = 4 + \frac{1}{2} = 4.5V$$

$$V_{TL} = V_S - \frac{V_{HW}}{2} = 4 - \frac{1}{2} = 3.5V$$

We know,

$$V_S = V_{REF} \frac{R_2}{R_1 + R_2}, V_{HW} = 2V_H \frac{R_1}{R_1 + R_2} \quad \text{--- (i)}$$

From (ii),

$$1 = 2 \times 10 \times \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow \frac{R_1}{R_1 + R_2} = \frac{1}{20}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{1}{19}$$



$$\text{if, } R_2 = 38k\Omega,$$

$$\frac{R_1}{38k} = \frac{1}{19} \Rightarrow R_1 = 2k\Omega$$

From (i),

$$4 = V_{REF} \times \frac{38}{38 + 1}$$

$$\therefore V_{REF} = 4.1V$$

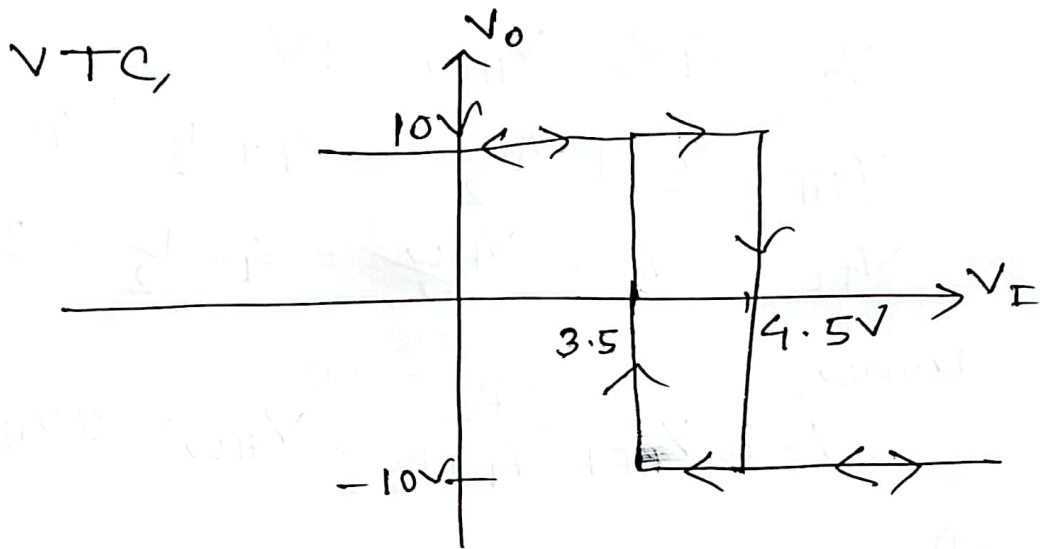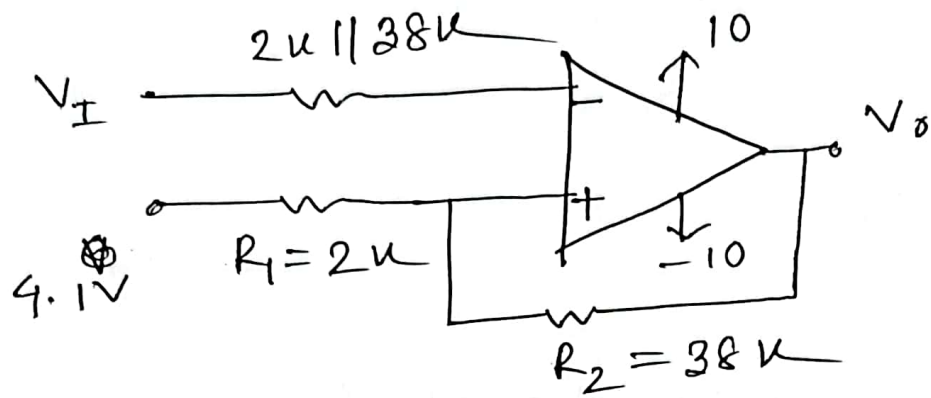


2.a) For the given circuit, determine the duty cycle.

b) Plot the voltage of capacitor (V_x) and output voltage with respect to time on the same graph with proper labeling.

(Given: $R_x = 1 \text{ k}\Omega$ and $C_x = 10 \mu\text{F}$)

[4]

[6]

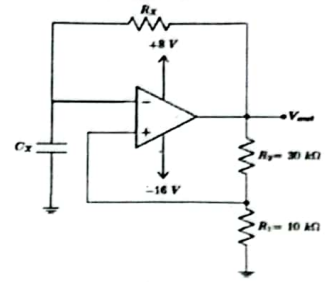

$$2.a) R_1 = 10 \mu, R_2 = 30 \mu,$$

$$V_H = 8 \text{ V}, V_L = -16 \text{ V},$$

$$V_{TH} = 8 \times \frac{10}{10 + 30} = 2 \text{ V},$$

$$V_{TL} = -16 \times \frac{10}{10 + 30} = -4 \text{ V}$$

$$T_1 = R_x C_x \ln \frac{V_H - V_{TL}}{V_H - V_{TH}}$$

$$= R_x C_x \ln \frac{8 + 4}{8 - 2} = R_x C_x \ln 2$$

$$T_2 = R_x C_x \ln \frac{V_L - V_{TH}}{V_L - V_{TL}}$$

$$= R_x C_x \ln \frac{-16 - 2}{-16 + 4} = R_x C_x \ln 1.5$$

$$DC = \frac{T_1}{T_1 + T_2} \times 100\% = \frac{R_x C_x \ln 2}{R_x C_x \ln 2 + R_x C_x \ln 1.5} \times 100\%$$

$$= 0.63 \times 100\% = 63.09\%$$

$$2.b) R_x C_x = 1 \mu \times 10 \mu = 10 \text{ ms}$$

$$T_1 = 10 \text{ ms} \ln 2 = 6.93 \text{ ms}$$

$$T_2 = 10 \text{ ms} \ln 1.5 = 4.05 \text{ ms}$$

