

## BRAC UNIVERSITY

CSE 350

Quiz-3, Section 8

Fall 2024

Marks: 20


Name: \_\_\_\_\_

ID: \_\_\_\_\_

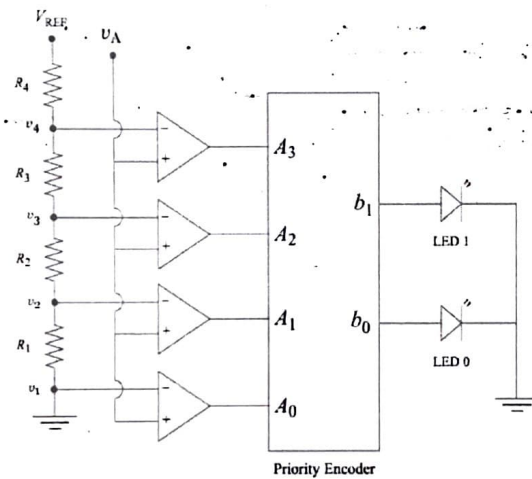1. The figure shows a 2-bit Flash ADC with  $V_{REF} = 12V$  and its input ranged from  $0V$  to  $12V$ .

Given:  $R_1 = 5k\Omega$ ,  $R_2 = 10k\Omega$ ,  $R_3 = 10k\Omega$ ,  $R_4 = 15k\Omega$ . The two outputs of the ADC are connected to two LEDs.

This circuit works as Active High Logic. ( High Voltage Output  $\rightarrow$  '1' and Low Voltage Output  $\rightarrow$  '0')



- Determine the quantization range, corresponding digital output, and the states of the LED for the 2-bit Flash ADC. Make a table with quantization range, corresponding digital output, and the states of the LED. [6]
- Find the truth table of the Encoder and state the priority sequence of the Encoder. [4]

a)

Here,  $V_1 = 0V$

$$I = \frac{12-0}{40k} = \frac{12}{40k}$$

$$\frac{V_2-0}{5k} = \frac{12}{40k}$$

$$\Rightarrow V_2 = 1.5V$$

$$V_3 = V_2 + \frac{12}{40k} \times 10k = 4.5V$$

$$V_4 = V_3 + \frac{12}{40k} \times 10k = 7.5V$$

Q. Range	$b_1$ $b_0$	LED <sub>1</sub> LED <sub>0</sub>
0 - 1.5	00	off off
1.5 - 4.5	01	off on
4.5 - 7.5	10	on off
7.5 - 12	11	on on


b) Truth table,

$A_3$	$A_2$	$A_1$	$A_0$	$b_1$	$b_0$
0	0	0	1	0	0
0	0	1	1	0	1
0	1	1	1	1	0
1	1	1	1	1	1

Priority,  $A_3 > A_2 > A_1 > A_0$

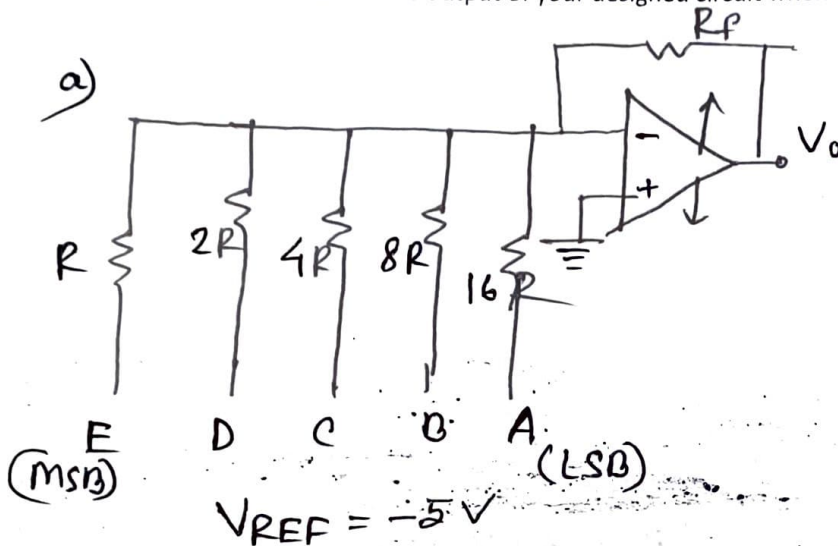2. You want to design a 5-bit binary weighted DAC circuit. You need to use -5V as reference voltage, +15 V as positive power supply and -15 V as negative power supply.

- Design the circuit to make the step size 0.25 V. [4]
- Draw the output voltage vs input plot with proper labeling. [3]
- For  $4R_F$  what will be the output of your designed circuit when all the inputs are high. [3]



For, 00001,  $V_o = 0.25V$

$$0.25 = -\frac{R_F}{R} V_{REF} \left( E + \frac{D}{2} + \frac{C}{4} + \frac{B}{8} + \frac{A}{16} \right)$$

$$\Rightarrow 0.25 = -\frac{R_F}{R} \times -5 \times \left( 0 + 0 + 0 + 0 + \frac{1}{16} \right)$$



$$\Rightarrow \frac{4}{5} = \frac{R_F}{R}$$

Assuming,  $R = 10K$ ,

$$\frac{4}{5} = \frac{R_F}{10K}$$

$$\therefore R_F = 8K$$

$$V_H = +15V, V_L = -15V$$

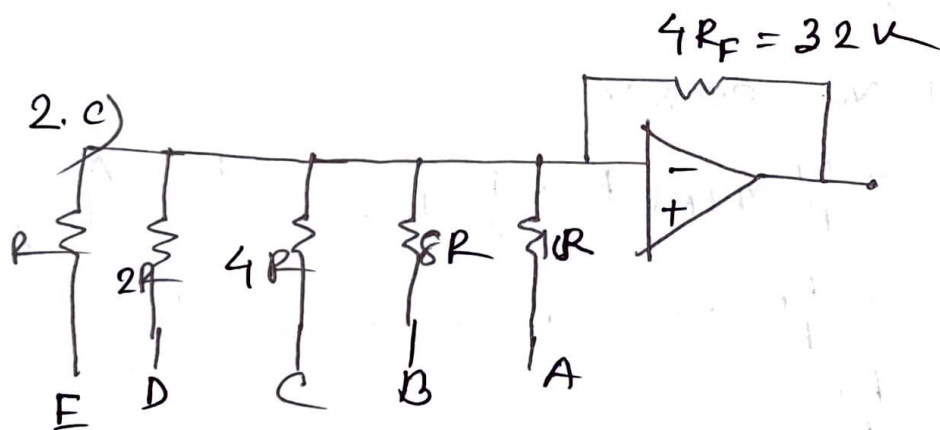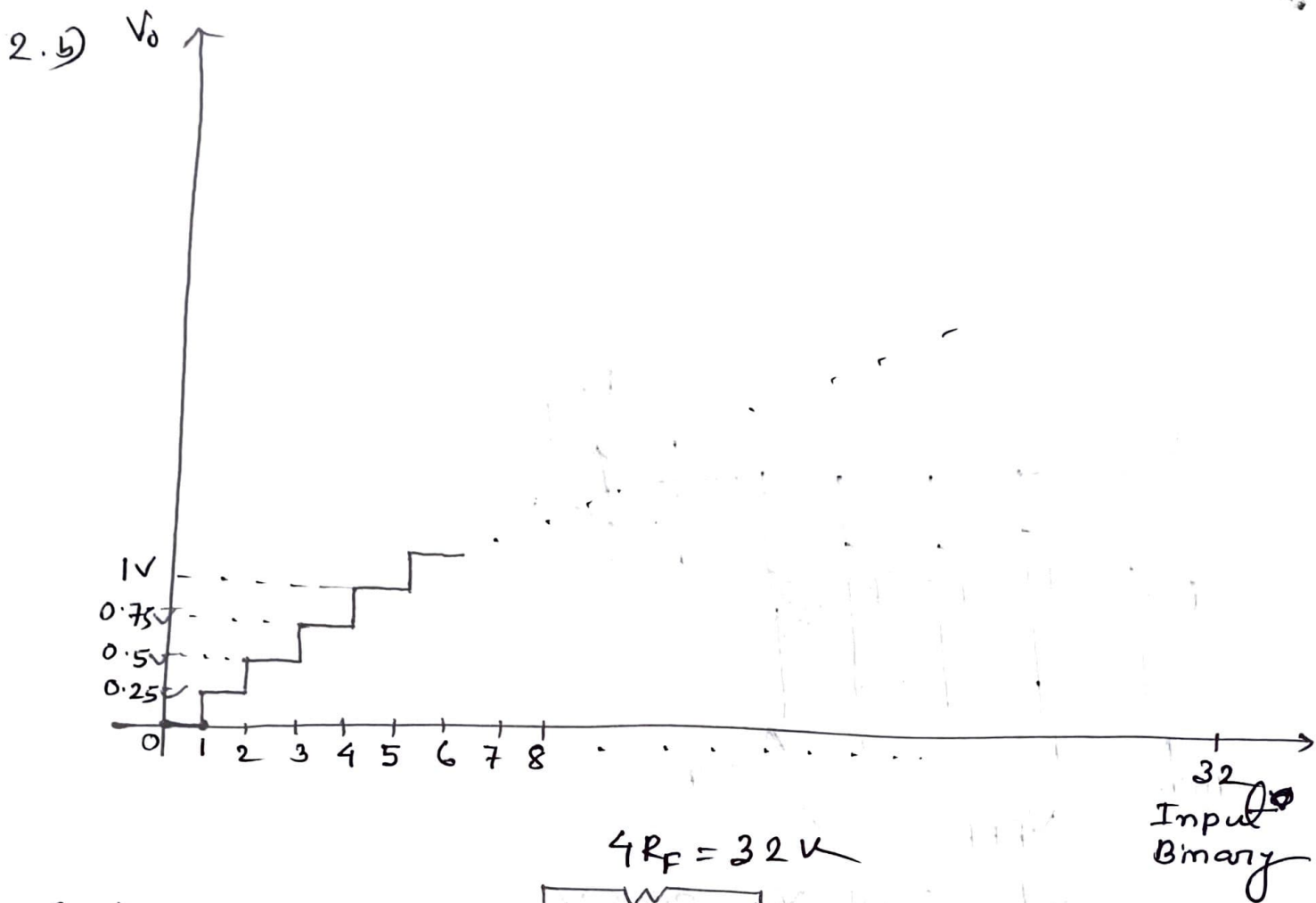

$$\begin{aligned}
 V_o &= -\frac{R_F}{R} V_{REF} \left( E + \frac{D}{2} + \frac{C}{4} + \frac{B}{8} + \frac{A}{16} \right) \\
 V_o &= -\frac{32}{10} \times 5 \left( 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right) \\
 &= \frac{1}{2} \times (32 + 16 + 8 + 4 + 2) \\
 &= (16 + 8 + 4 + 2 + 1) \\
 &= 31V \\
 \text{but this is not possible,} \\
 V_o &= 15V
 \end{aligned}$$