

# CSE 350

## Digital Electronics and Pulse Techniques

### Analog to Digital Converter (ADC)

**Course Instructor:** Shomen Kundu (SDU)

Mail: [shomen.kundu@bracu.ac.bd](mailto:shomen.kundu@bracu.ac.bd)  
Desk: 4N166



# Analog to Digital Converter (ADC)

Signal can be classified into two broad categories.

- i. Analog Signal
- ii. Digital Signal

*Analog Signal*



*Digital Signal*




# Analog to Digital Converter (ADC)


Physical world's information are mostly analog. Analog means data could take any real value at each instant of time.

In order to store/process we use digital data in our computers and microprocessor


 
Digital data means binary bit of strings.



# A/D conversion process

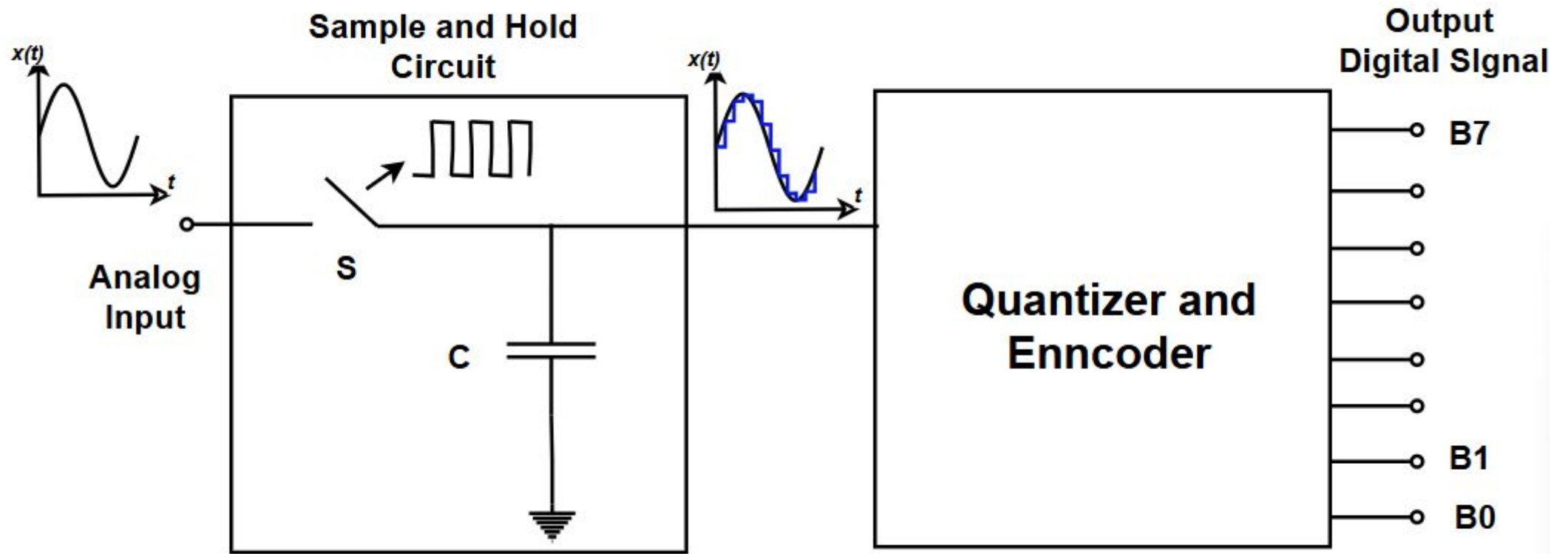

# Sample and Hold Circuit

  

Inspiring Excellence

# Quantization:

Quantization is a process by which we assign sampled and hold signal data to some fixed preassigned values.

- i. Midrise Quantization
- ii. Midtread Quantization


$N = \text{Number of bits}$

$2^N = \text{Number of levels}$

$$\Delta = \text{resolution} = \frac{V_{\max} - V_{\min}}{2^N}$$




# Midrise Quantization:

 

Quantization Range	Quantization Level
 
# Mid tread Quantization ( Not symmetrical and Equally Spaced)



Quantization Range	Quantization Level



# Encoding

We can choose binary values for each of the level.

$$\text{Number of bits} = \text{Ceil}(\log_2(\text{Number of levels}))$$



Assign lower Q level to 0

Then increase one for each next level



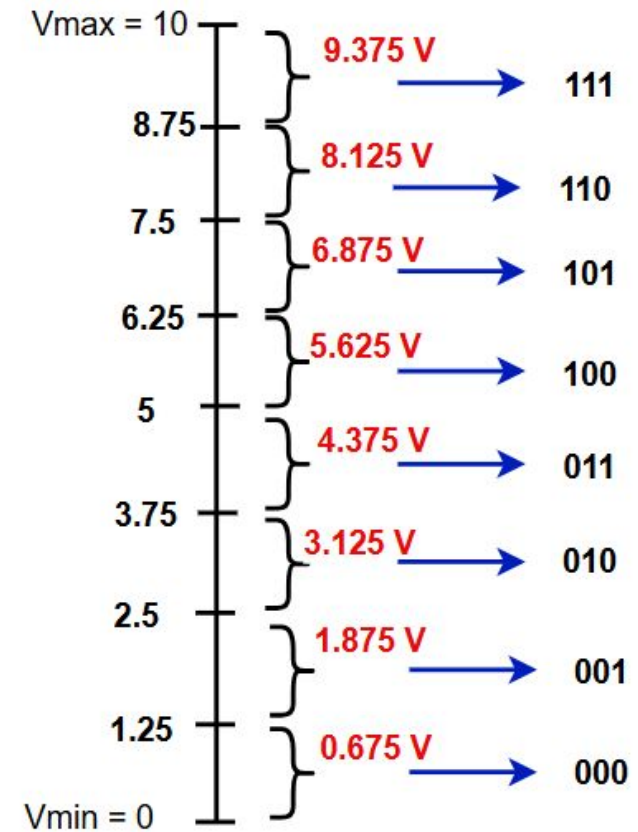 
# Quantization Range, Level, code

Ex: Identify which one is Mid rise and Mid tread.



# Quantization Range, Level, code

 

Here,


$$\frac{V_{max} + V_{min}}{2} = \frac{8 + 0}{2} = 4 V$$

As 4 V is a Quantization level. So, it is a mid tread quantization


 
# Quantization Range, Level, code

Ex: Identify which one is Mid rise and Mid tread.



Here,

$$\frac{V_{max} + V_{min}}{2} = \frac{10 + 0}{2} = 5 V$$

As 5 V is not a Quantization level. So, it is a mid rise quantization



# Flash A/D converter

## Features of the Flash A/D converter


- ✓ This converter is very fast.
- ✓ It requires one clock cycle to convert the analog to digital data.
- ✓ It requires a lot components.

# Op-Amp

For open loop configuration

*If  $V_+ > V_-$ ,  $V_{out} = \text{High (logic 1)}$*

 *If  $V_+ < V_-$ ,  $V_{out} = \text{Low (logic 0)}$*



# Flash ADC design

Suppose you have a signal with  $V_{\max} = 10\text{ V}$  and  $V_{\min} = 0\text{ V}$ . Design a simple flash ADC converter. Use 3 bits for designing.

# Flash ADC design

Suppose you have a signal with  $V_{max} = 10\text{ V}$  and  $V_{min} = 0\text{ V}$ . Design a simple flash ADC converter. Use 3 bits for designing. Provide your encoder truth table.

Design:

Here,

$$N = 3$$

$$\text{\#Number of registor} = 2^3 = 8$$

$$\text{\#Number of comparator} = 2^3 - 1 = 7$$

$$V_{+ref} = V_{max} = 10\text{ V}$$

$$V_{-ref} = V_{min} = 0\text{ V}$$






# Circuit

The following is the Circuit of a 3 bits Flash ADC,

 **$V_+$  of the comparator is connected to the input.**



# Circuit Analysis

The following is the Circuit of a 3 bits Flash ADC,

$$I = \frac{10 - 0}{8R} = \frac{10}{8R}$$


$$I = \frac{V1 - V_{-ref}}{R}$$

$$V1 = V_{-ref} + IR = 0 + \frac{10}{8R} * R = 1.25 V$$

$$\text{Similarly, } I = \frac{V2 - V1}{R} \Rightarrow V2 = V1 + IR$$

$$\Rightarrow V2 = 1.25 + \frac{10}{8R} * R = 2.5 V$$


You can find other voltage in this way.

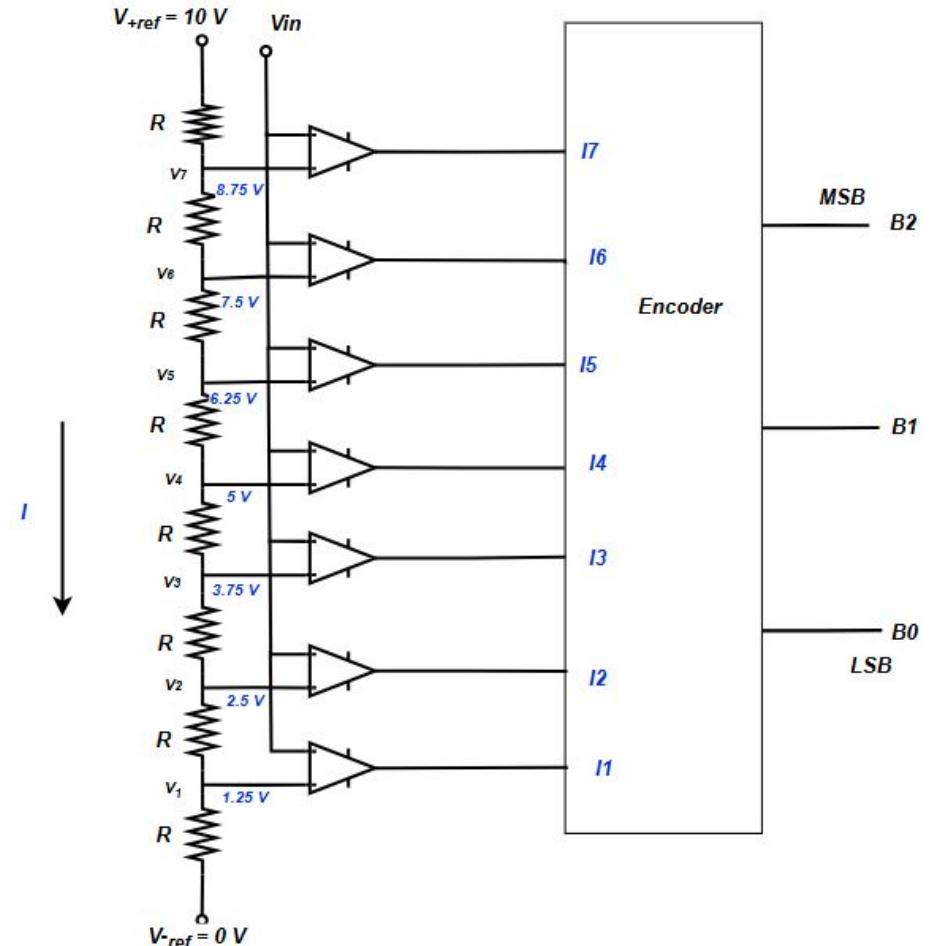

# Circuit Analysis

Summary table:

Q Range	Q level	I7I6I5I4I3I2I1	Binary (B2B1B0)
0 - 1.25	0.675	000 000 0	
1.25 - 2.5	1.875	000 000 1	
2.5 - 3.75	3.125	000 001 1	
3.75 - 5	4.375	000 011 1	
5 - 6.25	5.625	000 111 1	
6.25 - 7.5	6.875	001 111 1	
7.5 - 8.75	8.125	011 111 1	
8.75 - 10	9.375	111 111 1	

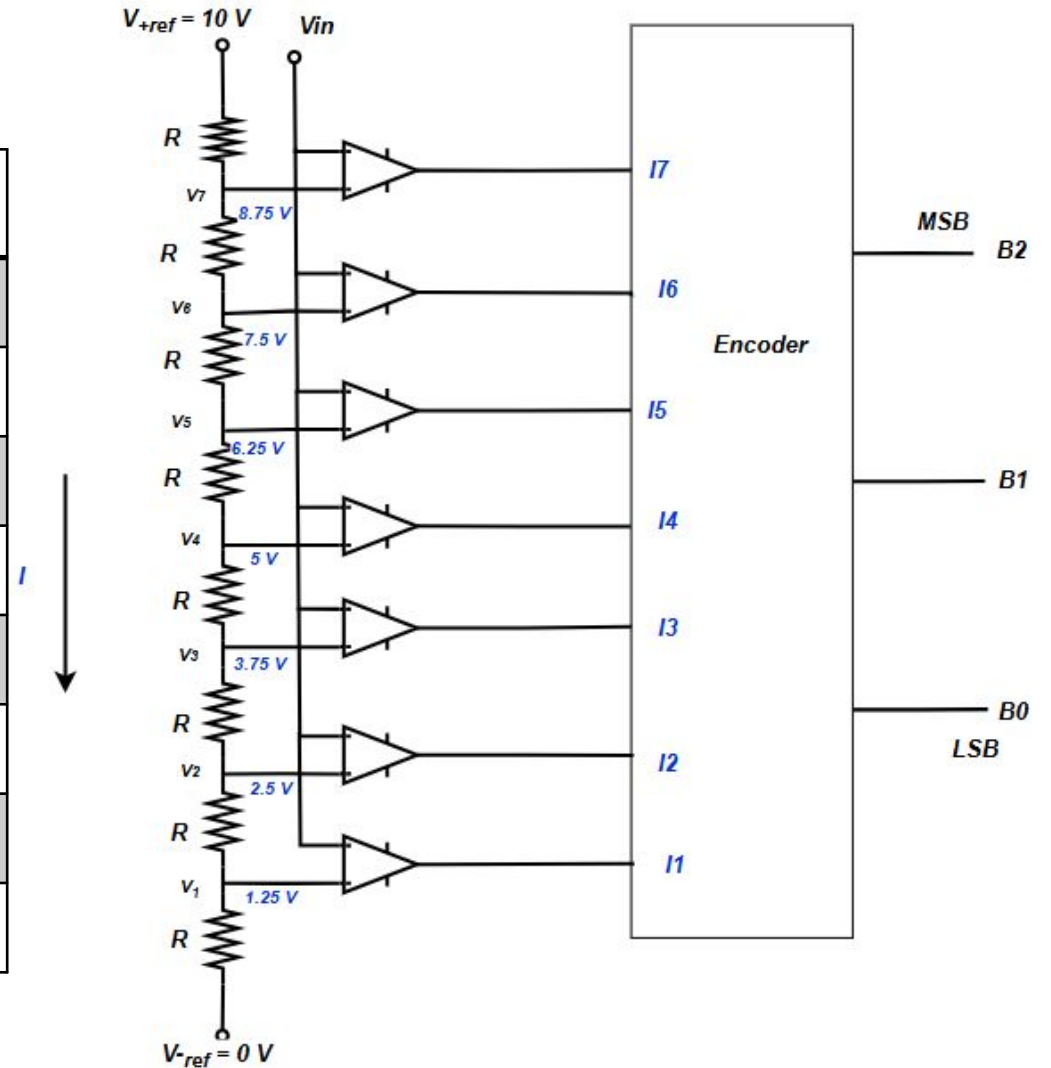

# Circuit Analysis

## Encoder Truth Table:

( **V+ of the comparator is connected to the Input** )

Encoder can be implemented using the combinational network.

I7I6I5I4I3I2I1	Binary (B2B1B0)
000 000 0	000
000 000 1	001
000 001 1	010
000 011 1	011
000 111 1	100
001 111 1	101
011 111 1	110
111 111 1	111



# Circuit Analysis

## Encoder Truth Table:

( V- of the comparator is connected to the Input )

Encoder can be implemented using the combinational network.

I7I6I5I4I3I2I1	Binary (B2B1B0)
111 111 1	000
111 111 0	001
111 110 0	010
111 100 0	011
111 000 0	100
110 000 0	101
1 000 000	110
000 000 0	111



# Problem:

Make a table with Quantization Range, Quantization Level and Binary values for the given ADC circuit.

What will be the final output if the input voltage  $V_A = 2.125 \text{ V}$ .

[  $V_{REF} = 12 \text{ V}$  ]

