

# CSE 350

## Digital Electronics and Pulse Techniques

### RTL circuits


**Course Instructor:** Shomen Kundu (SDU)

Mail: [shomen.kundu@bracu.ac.bd](mailto:shomen.kundu@bracu.ac.bd)  
Desk: 4N166



# Resistor Transistor Logic (RTL)

## Not gate

 


# Resistor Transistor Logic (RTL)

**Case 1:**  $A = 0$  ,  $v_i = 0$  V

# input low, output  
expected to be high.  
We need to prove it.

**Assumption:** Cutoff mode

 

# Resistor Transistor Logic (RTL)

## Verification


$$\frac{V_b - 0}{15\text{ k}} + \frac{V_b - (-12)}{100\text{ k}} = 0 \Rightarrow V_B = -1.565\text{ V},$$

Here,  $V_E = 0$

As  $V_{BE} = -1.565\text{ V} < 0.7\text{ V}$ , | Assumption is correct

For cutoff mode:  $I_B = I_C = I_E = 0$
 
$$I_C = 0 = \frac{12 - V_C}{2.2\text{ k}}, \quad V_C = 12\text{ V}$$



# Resistor Transistor Logic (RTL)

**Case 2:**  $A = 1, V_i = 12\text{ V}$

# input high, output


expected to be low.

$V_{CE} = 0.2\text{ V}$

We can expect this BJT

to be operating in saturation mode.

**Assumption:** Saturation mode

 

# Resistor Transistor Logic (RTL)

$$I_C = \frac{12 - 0.2}{2.2 \text{ k}} = 5.36 \text{ mA}$$

**T** → **Saturation**,  $V_{BE} = 0.8 \text{ V}$  and  $V_{CE} = 0.2 \text{ V}$

$$I_1 = \frac{12 - 0.8}{15 \text{ k}} = 0.746 \text{ mA}$$


$$I_2 = \frac{0.8 - (-12)}{100 \text{ k}} = 0.128 \text{ mA}$$

$$I_B + I_2 - I_1 = 0$$

$$I_B = I_1 - I_2 = 0.619 \text{ mA}$$

$$\text{Here, } \beta_{\text{forced}} = \frac{I_C}{I_B} = 8.659 < \beta_F$$


**( Saturation assumption is correct )**

 

# Power dissipation for RTL inverters:

## Case 01: T --> Cutoff mode

$$I_B = I_C = I_E = 0$$


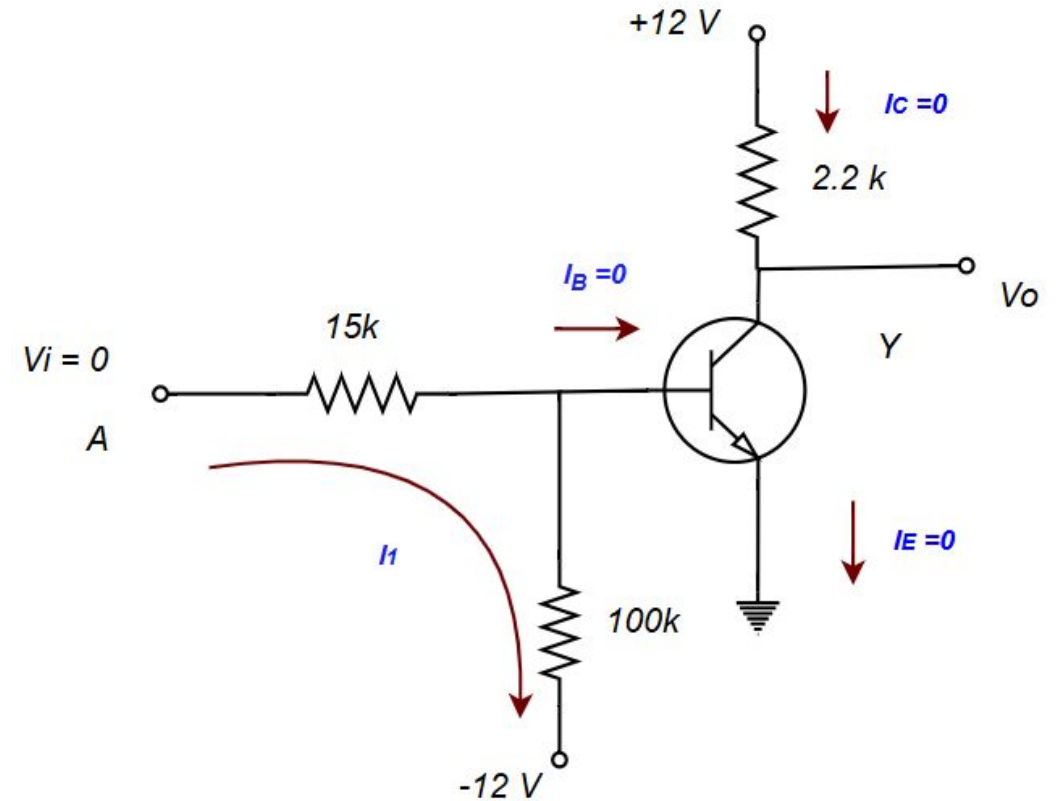


# Power dissipation for RTL inverter

$$I_1 = \frac{0 - (-12)}{(100 + 15) k} = 0.104 \text{ mA}$$

  **Power dissipation,**

$$P = (0 - (-12)) * 0.104 = 1.2521 \text{ mW}$$





# Power dissipation for RTL inverter

**Case 2:**  $A = 1, V_i = 12\text{ V}$

# input high, output


expected to be low.

$V_{CE} = 0.2\text{ V}, V_{BE} = 0.8\text{ V}$

We can expect this BJT

to be operating in saturation mode.

**Assumption:** Saturation mode

 

# Power dissipation for RTL inverter

$$I_C = \frac{12 - 0.2}{2.2 \text{ k}} = 5.36 \text{ mA}$$

***T → Saturation,***

$$V_{BE} = 0.8 \text{ V and } V_{CE} = 0.2 \text{ V}$$

$$I_1 = \frac{12 - 0.8}{15 \text{ k}} = 0.746 \text{ mA}$$


$$I_2 = \frac{0.8 - (-12)}{100 \text{ k}} = 0.128 \text{ mA}$$

$$I_B + I_2 - I_1 = 0$$


$$I_B = I_1 - I_2 = 0.619 \text{ mA}$$

$$\beta_{forced} = \frac{I_C}{I_B} = 8.659 < \beta_F$$

***(Saturation assumption is correct)***

 

# Power dissipation for RTL inverter

 

# Power dissipation for RTL inverter

$$P1 = (12 - (-12))V * 0.128 \text{ mA} = 3.072 \text{ mW}$$

$$P2 = (12 - 0)V * 0.6186 \text{ mA} = 7.4323 \text{ mW}$$

$$P3 = (12 - 0) V * 5.3632 \text{ mW} = 64.3632 \text{ mW}$$


$$\text{Total Power, } P = P1 + P2 + P3 = 74.8584 \text{ mW}$$


 
# Noise Margin

Output from one inverter is received as input to the next inverter.

External interference, noise can hamper the signal transmission



# Noise Margin

**Noise Margin:** The maximum amount of noise voltage can be tolerated by a circuit while completing a successful transmission from output to input.

**High state noise margin:**


$$V_{NH} = V_{OH} - V_{IH}$$

**Low state noise margin:**

$$V_{NL} = V_{IL} - V_{OL}$$



# Noise Margin

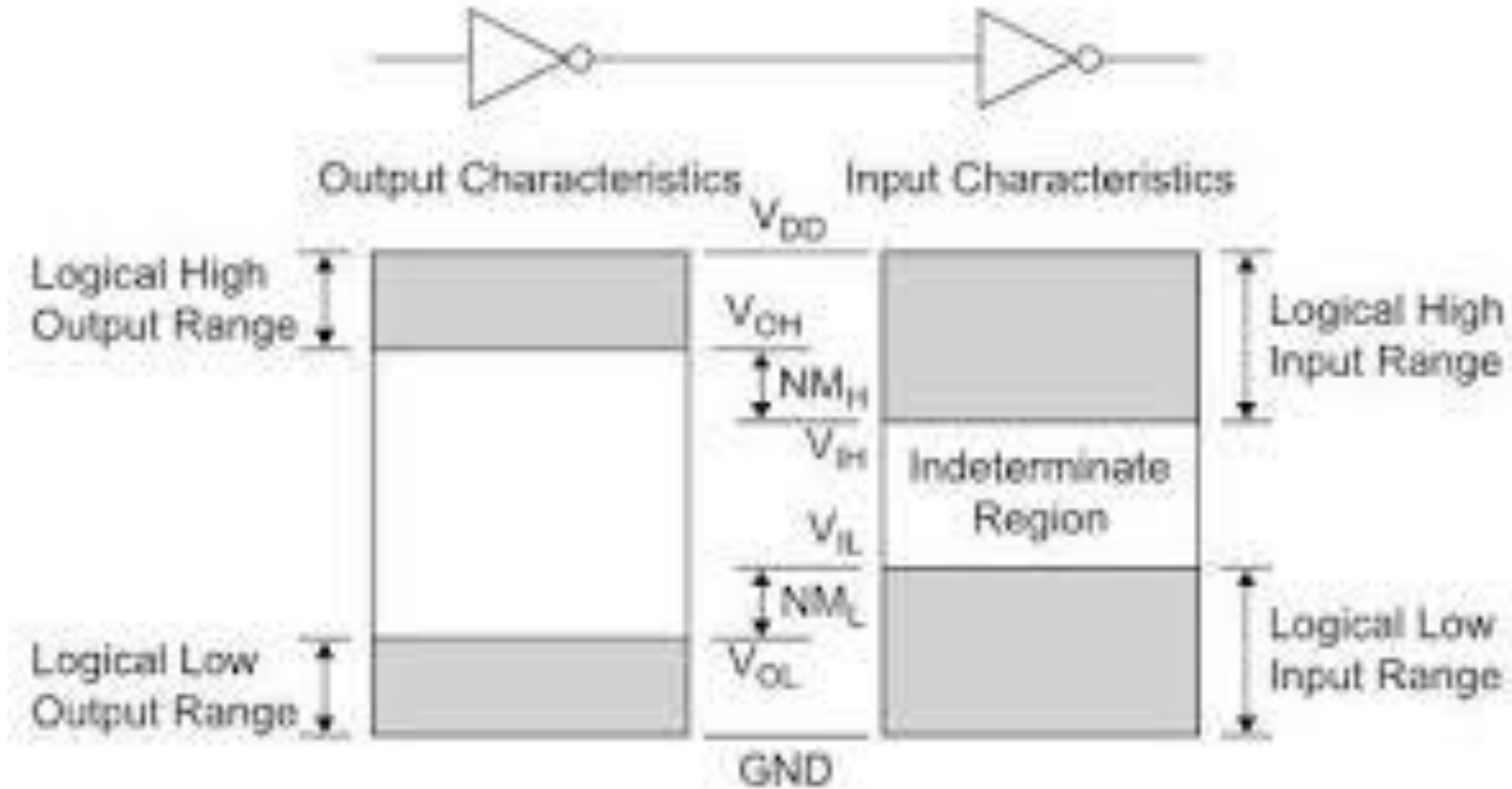

# Noise Margin

$V_{OH}$  □ The minimum voltage level at an output in logical '1' state under defined load condition

$V_{IH}$  □ The minimum voltage level at an input in logical '1' state under defined load condition

$V_{OL}$  □ The maximum voltage level at an output in the logical '0' state under defined load condition.

$V_{IL}$  □ The maximum voltage level at an input in the logical '0' state under defined load condition.





# Example:

The output voltage might drop 0.5V from the maximum voltage. Find out the Noise Margin of the circuit. Given  $\beta_F = 30$ .

## $V_{OL}$ Calculation:

When input is high output should be low and BJT will remain at the saturation mode.


Max  $V_o$  for saturation mode will be 0.2 V

$$V_{OL} = 0.2 \text{ V (saturated)}$$

## $V_{OH}$ Calculation:

Maximum output voltage = 12V ,

$$V_{OH} = 12 - 0.5 = 11.5 \text{ V}$$

 

# Noise Margin

$V_{IL}$  calculation :

The maximum voltage we might apply so that the transistor is still turn off.

$V_{BE} = 0.5 \text{ V}$ , we are on the verge of turning on the transistor T.

→ T : cutoff ,  $I_B = 0$  ,  $I_1 = I_2$


We need to find out for  $V_{BE} = 0.5 \text{ V}$  , what should be the input voltage.

$$I_2 = \frac{0.5 - (-12)}{100k} = 0.125 \text{ mA}$$

$$\Rightarrow V_i = 0.5 + 15 * 0.125 = 2.375 \text{ V}$$

This voltage is maximum that we can apply to the inverter without turning on the transistor.

$$V_{IL} = 2.375 \text{ V}$$

 

# Noise Margin

**$V_{IH}$  calculation :**

**T  $\rightarrow$  Saturation**

The minimum high voltage that we can apply to the input so that the transistor is still operating in saturation mode.  $\beta_F = 30$


We need to apply such input voltage that transistor T is operating on the verge of going to saturation from forward active mode.

on ,  $V_{BE} = 0.8 V$  ,  $V_{CE} = 0.2 V$

$$I_C = \frac{12 - 0.2}{2.2k} = 5.3636 \text{ mA}$$

$$\beta_{forced} = \frac{I_C}{I_B} \approx \beta_F$$

 (This will occur on the average of going from  
sat. to forward active mode)



# Noise Margin


$$I_B = \frac{I_C}{\beta_F} = 0.1788 \text{ mA},$$

$$I_2 = \frac{0.8 - (-12)}{100k} = 0.128 \text{ mA}$$

$$I_1 = I_2 + I_B = 0.3068 \text{ mA}$$

$$\frac{V_i - 0.8}{15k} = I_1 = 0.3068$$
 
$$V_i = 0.8 + 0.3068 * 15 = 5.4018 \text{ V}$$



# Noise Margin

$$V_{NH} = 11.5 - 5.4018 = 6.0982 \text{ V} < -\text{High noise margin}$$

$$V_{NL} = 2.375 - 0.2 = 2.175 \text{ V} < -\text{Low noise margin}$$

$$\text{Noise Margin} = \min(V_{NH}, V_{NL}) = 2.175 \text{ V}$$

This noise voltage can be tolerated for both input and output voltages.



# Fanout



## **Fanout:**

The maximum number of logic inputs ( of the same logic family ) that an output can drive reliably is called maximum fanout.

- ✓ **calculate fanout  $\square$  maximum fanout**
- ✓ **fanout given in question may not be maximum**




# Fanout

  

Here output is connected with two other gate input. Fanout = 2

# Fanout

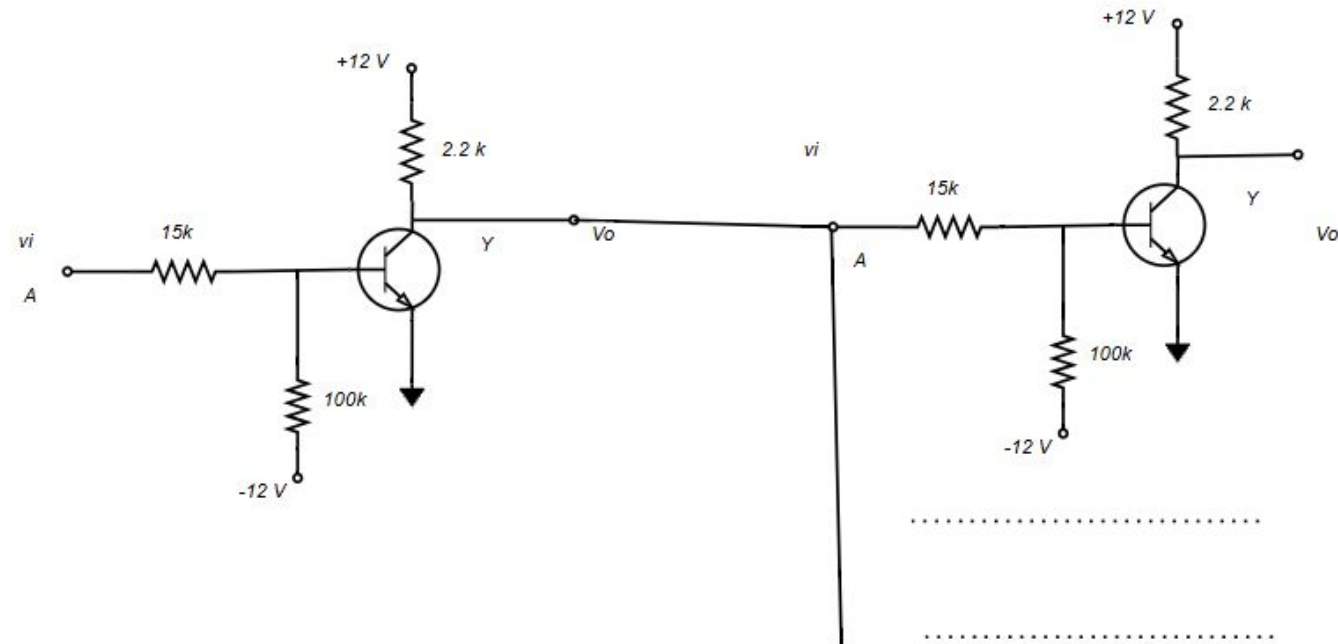**Example:** Calculate the fanout of the RTL circuit. Assume  $V_{OH} = 10V$ .





# Fanout

**Driver gate** □ **Supply current**

**Load gate** □ **Consume current**

**Two case:**

Case 1: Driver output Low,


Case 2: Driver output high

**Calculate:**

1. Individual demand current for each load circuit/ gate
2. The maximum current that can be supplied from driver circuit



# Fanout

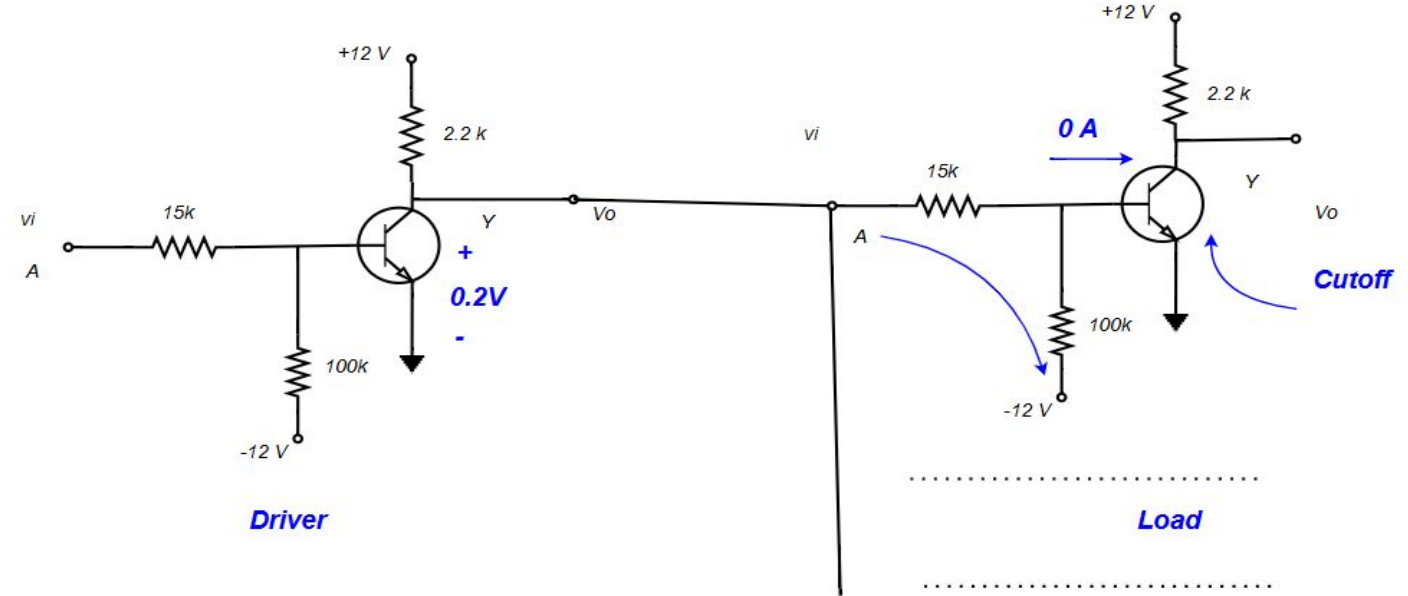

**Case 1.** When output voltage at the driver is low.

$$V_{OL} = 0.2 \text{ V}$$

$$\text{Maximum total supply} = \frac{12 - 0.2}{2.2k} = 5.3636 \text{ mA}$$

$$\text{Individual load current demand} = \frac{0.2 - (-12)}{115k} = 0.106 \text{ mA}$$


( in this case load circuits transistors are in cutoff mode )

Maximum number of load circuits that we can afford ,

$$\text{Fanout} = \frac{5.3636 \text{ mA}}{0.106 \text{ mA}} = \lfloor 50.6 \rfloor = 50 \text{ (Floor)}$$



# Fanout

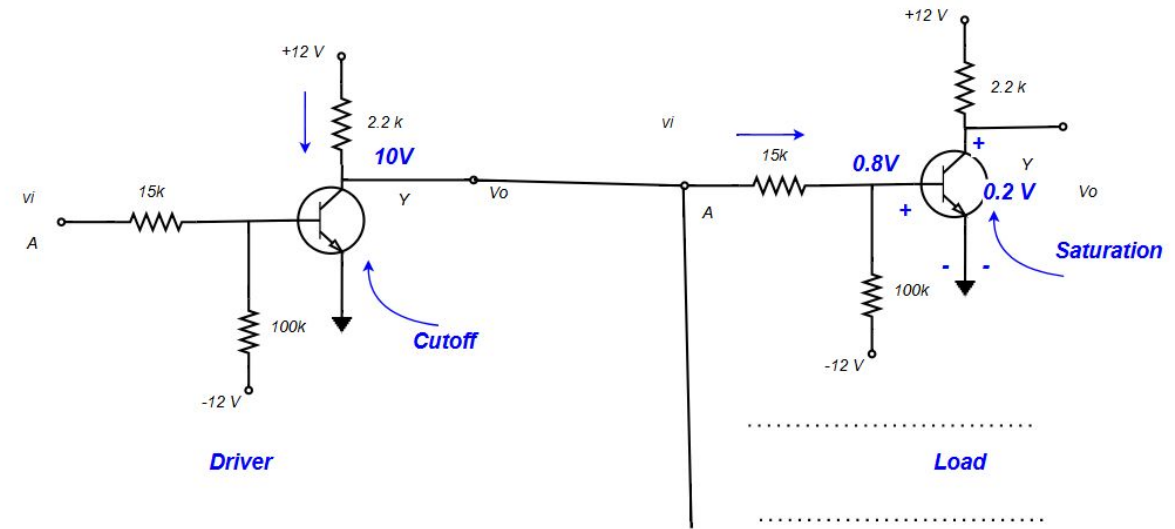

**Case 2: When output voltage driver circuit is high.  $V_{OH}$ .**

Driver transistor is in cutoff and load transistor is in saturation

$$\text{Maximum supply current} = \frac{12-10}{2.2k} = 0.909 \text{ mA}$$

$$\text{Individual load current} = I_L = \frac{10-0.8}{15k} = 0.6133 \text{ mA}$$

$$\text{Maximum fanout for this} = \left\lfloor \frac{0.909}{0.6133} \right\rfloor = 1$$



# Fanout

Overall maximum fanout must be calculated by considering worst case scenario.

To prevent malfunction of driver circuit , we need to take the minimum of the two cases.

$$\text{Max Fanout} = \text{Min} ( 50, 1 ) = 1$$