

# CSE 350

## Digital Electronics and Pulse Techniques

### DTL - NAND Gate

**Course Instructor:** Shomen Kundu (SDU)

Mail: [shomen.kundu@bracu.ac.bd](mailto:shomen.kundu@bracu.ac.bd)  
Desk: 4N166



Inspiring Excellence

# DTL

**DTL** : Diode Transistor Logic

**Bipolar** :

Saturated ( Switching transistor will be operating in cutoff or saturation mode)


Input terminals connect through a diode to a transistor's base terminal.

# DTL NAND Gate

## Basic Operation:

DTL NAND Gate

2 input AND gate + Inverter

 


# DTL NAND Gate

## Basic Operation:


DTL NAND Gate

2 input AND gate + Inverter

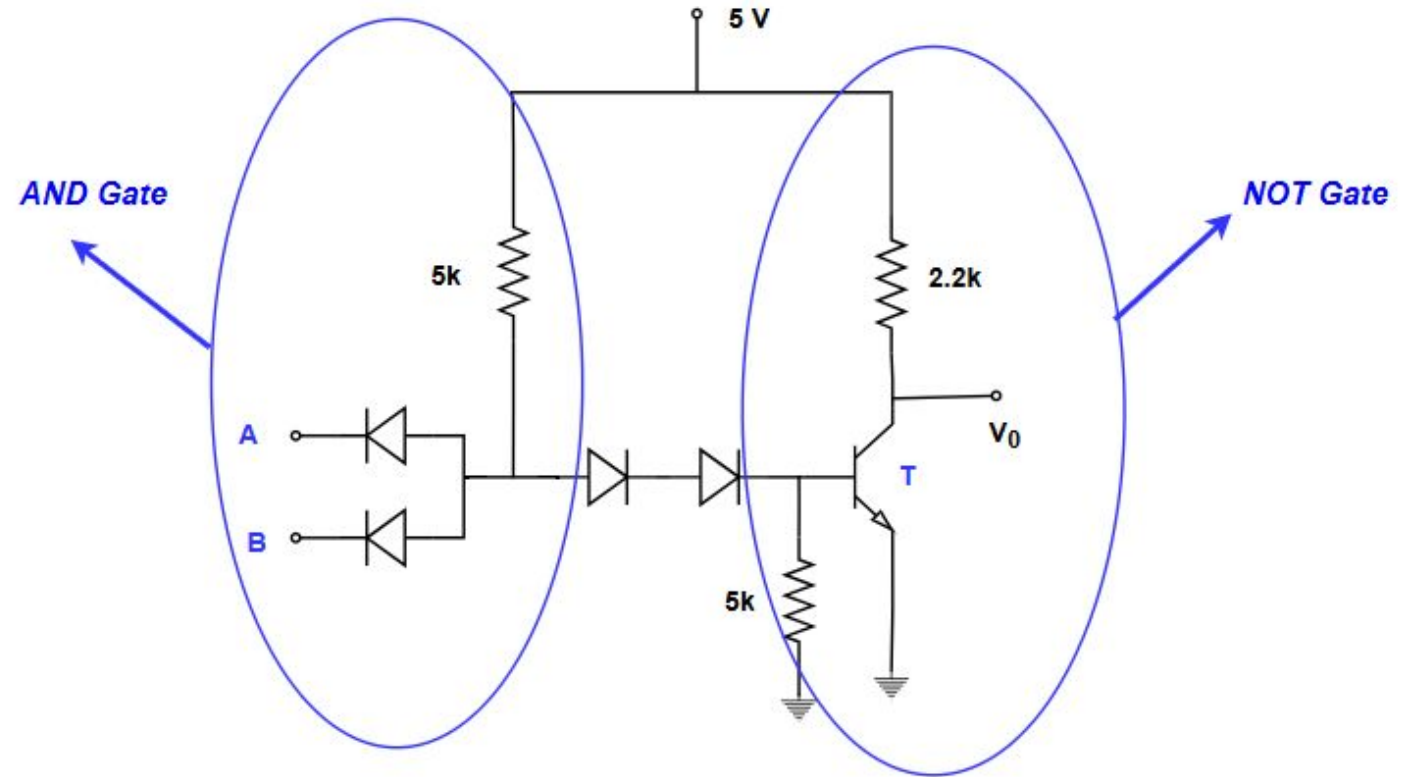

# DTL NAND Gate

 **Example:** Calculate the currents and node voltages for the following DTL gate. Verify it is a NAND gate. Input of the DTL NAND gate might be connected to the output of other DTL NAND gate.



# DTL NAND Gate

$V_A$	$V_B$	$V_o$
0.2	0.2	
0.2	5	
5	0.2	
5	5	



# DTL NAND Gate

Case 01:

$$V_A = low = 0.2 V$$

$$V_B = low = 0.2 V$$

Assume ,

The anode voltage  $V_P$  might be higher than the cathode voltages of D1 and 2 diode.

D1 and D2 are conducting , Thus  $V_{D1} = 0.7 V, V_{D2} = 0.7 V$

According to the assumption,  $V_P = 0.2 + 0.7 = 0.9 V$



# DTL NAND Gate


# In order for T transistor to turn on we need to have  $V_{BE} = 0.5$  ( cut in voltage of transistors ) , we also need to have  $VD3 = VD4 = 0.6$  V ( Cut in voltage for diode )

As a total we require,

$VD3 + VD4 + V_{BE} = 0.6 + 0.6 + 0.5 = 1.7$  V at p node to turn on the right side of the circuits.

Necessary condition to turn the transistor T.

 If  $V_p = 0.9$  V, then T can not turn on. This justifies our assumption.





# DTL NAND Gate

Now we can calculate the current and voltages.

T → cutoff

D1, D2 → conducting

D3, D4 → off,


$V_p = 0.9 \text{ V}$ ,  $I_C = I_B = 0$ ,  $V_o = 5 \text{ V}$

$I_3 = 0$ ,  $I_2 = 0$

$$I_1 = \frac{5 - 0.9}{5k} = 0.82 \text{ mA}$$

$I_{D1} = I_{D2}$  because both of the branches are identical
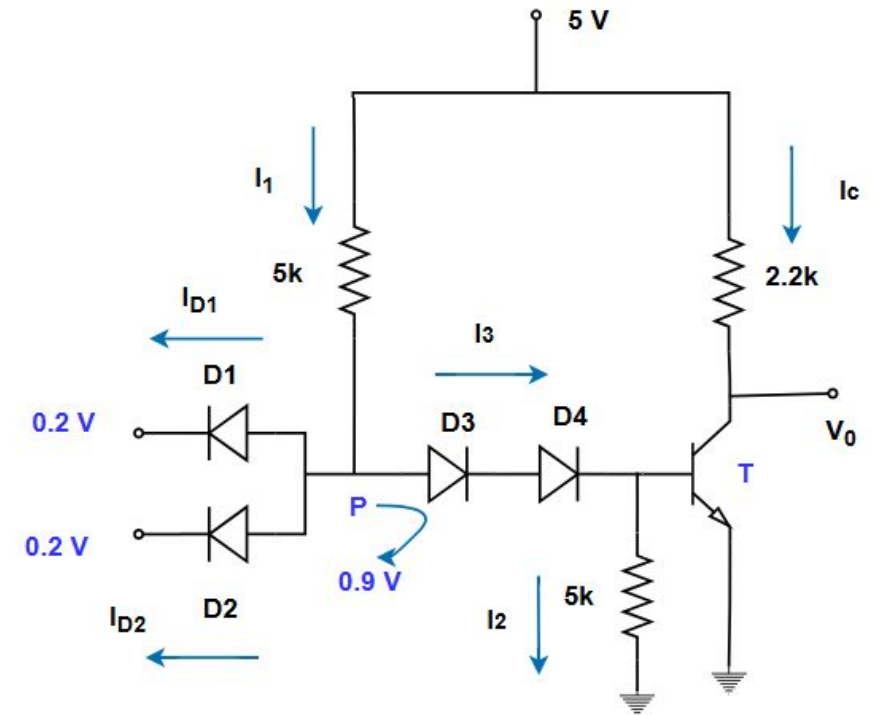
$$I_{D1} = \frac{I_1}{2} = 0.41 \text{ mA} = I_{D2}$$



# DTL NAND Gate

## Case 2:

$$V_A = 0.2 \text{ V}$$

$$V_B = 5 \text{ V}$$

Assume,  $D1$  is conducting and  $D2$  is off.

This implies,


$$V_p = 0.9 \text{ V}$$

# we need at least  $V_p < 1.7 \text{ V}$  to turn on  $T$  transistor. It again justifies our assumption.

$$I_c = I_B = I_3 = I_2 = 0 \text{ mA}, I_1 = 0.82 \text{ mA}$$

$$I_{D2} = 0 \text{ mA and } I_{D1} = 0.82 \text{ mA}$$

$$V_o = 5 \text{ V}$$

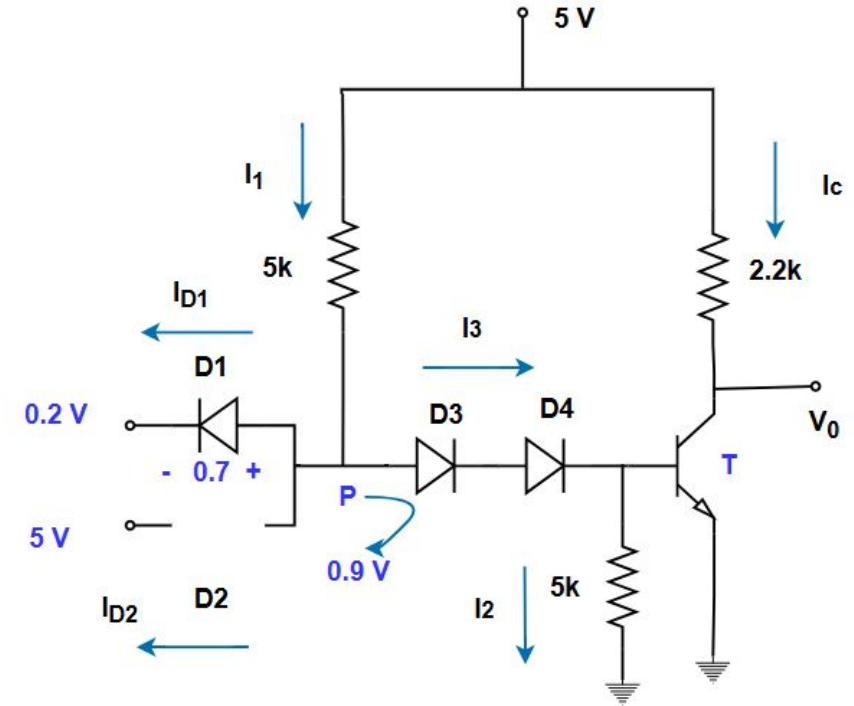

# DTL NAND Gate

## Case 3:

$$V_A = 5\text{ V}$$

$$V_B = 0.2\text{ V}$$

Assume,  $D2$  is conducting and  $D1$  is off.

This implies,


$$V_p = 0.9\text{ V}$$

# we need at least  $V_p < 1.7\text{ V}$  to turn on  $T$  transistor. It again justifies our assumption.

$$I_c = I_B = I_3 = I_2 = 0\text{ mA}, I_1 = 0.82\text{ mA}$$

$$I_{D1} = 0\text{ mA and } I_{D2} = 0.82\text{ mA}$$

$$V_o = 5\text{ V}$$

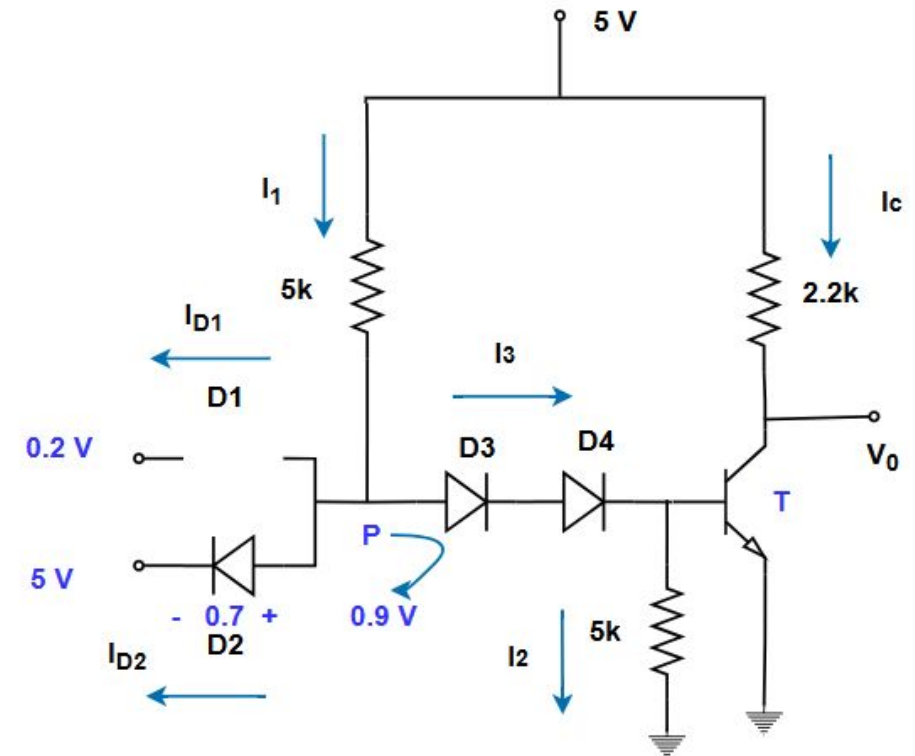

# DTL NAND Gate

## Case 4:

$$V_A = 5\text{ V}$$

$$V_B = 5\text{ V}$$

Assume,  $D1$  is off and  $D2$  is off.

$$I_{D1} = I_{D2} = 0\text{ mA}$$


Therefore,  $D3$ ,  $D4$ ,  $T$  must be ON.

Because it is a DTL circuit. The switching transistor must operate in saturation mode when it is turned on.

$$V_{CE} = 0.2\text{ V}, V_{BE} = 0.8\text{ V}$$

$$V_{D3} = V_{D4} = 0.7\text{ V}$$

[Conduction voltage of diode]

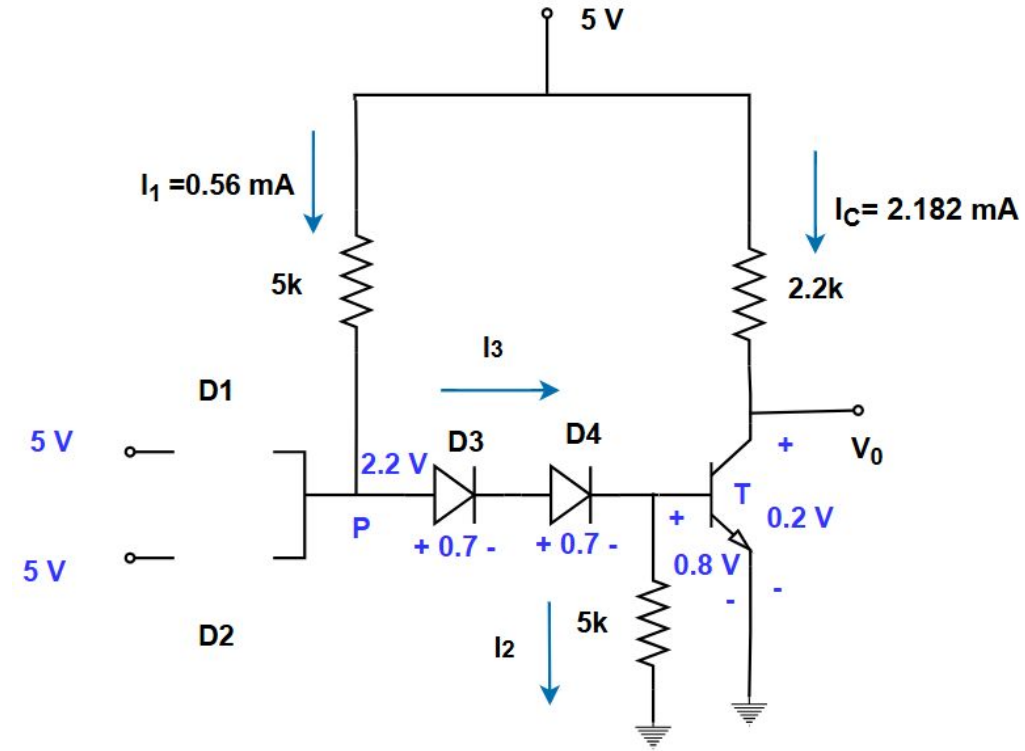

# DTL NAND

$$V_p = 0.7 + 0.7 + 0.8 = 2.2 \text{ V}$$

Finally we have anode voltage of D1 and D2 is smaller than cathode voltage. They justify our assumption.


# Current calculation

$$I_1 = \frac{5 - 2.2}{5k} = 0.56 \text{ mA}$$

$$I_2 = \frac{0.8 - 0}{5k} = 0.16 \text{ mA}$$

$$I_B = I_3 - I_2 = 0.4 \text{ mA}$$
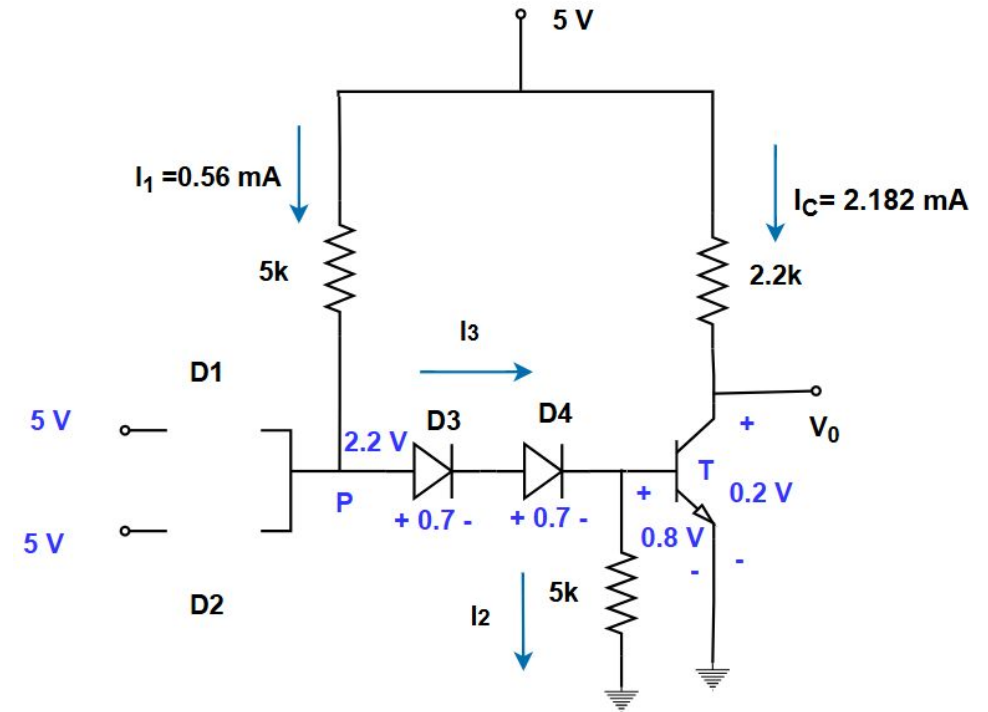
$$I_C = \frac{5 - 0.2}{2.2k} = 2.182 \text{ mA}$$



# DTL NAND

From the analysis we can get, the input output relationship. This indicates a NAND gate.

VA	VB	Vo
0.2	0.2	5
0.2	5	5
5	0.2	5
5	5	0.2

