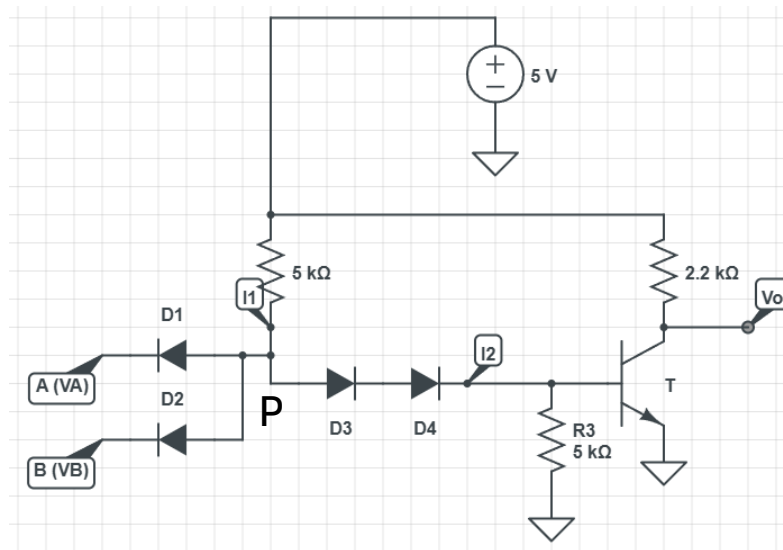


Basic Operation

Exercise 1



For the DTL NAND gate-

Find all the voltages & currents for all logic cases with verification of assumption.


Assume high input = 5 V, low input = 0.2 V

$$I_{D1} = I_{D2} = 0.41 \text{ mA}$$

$$I_{R3} = 0.82 \text{ mA}$$

$$V_o = 5 \text{ V}, 0.2 \text{ V}$$

Exercise 2

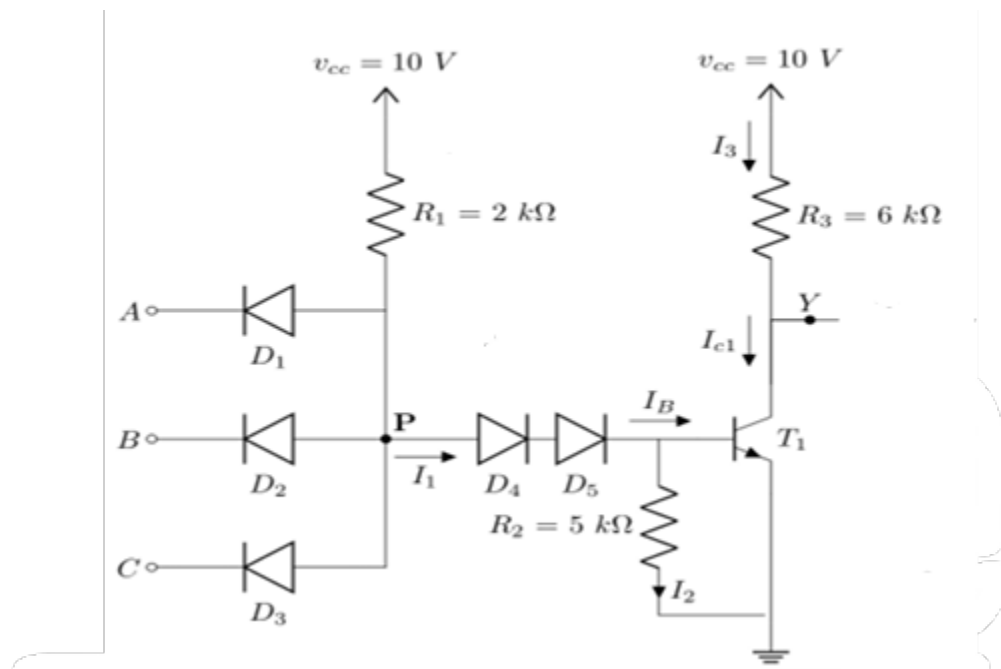

For the above circuit, $V_{OH} = 9.5 \text{ V}$, $V_{OL} = 0.1 \text{ V}$, $\beta_F = 30$

- Find the value of β_{min} when all inputs are high.
- If all the inputs are high, what is the magnitude of noise voltage at input A, that would cause the gate to malfunction?
- If at least one input is low, what is the magnitude of noise voltage at input A, that would cause the gate to malfunction?

Ans: a) 0.441
b) 8.4 V
c) 0.9 V


Practice Problem 1:

What is the current through D_B in the circuit of **Exercise 2**, for the logic case (1,0,0)?

Ans: 2.3 mA

Power Dissipation

Exercise 3

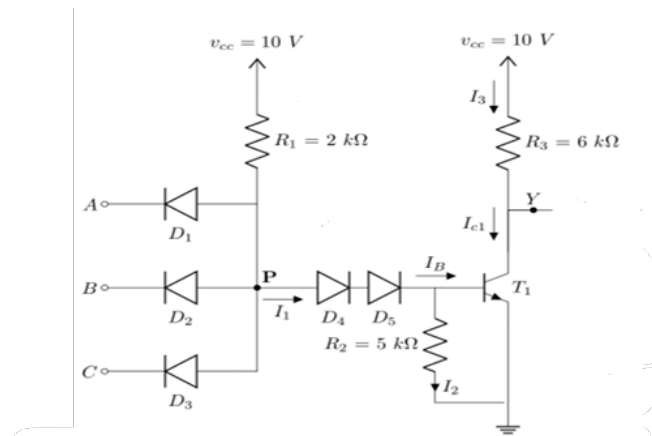

- Find power dissipation for all cases.
- Maximum & average power dissipation.

Ans: a) 45.54 mW, 55.5 mW
b) 55.5 mW, 46.785 mW


Practice Problem 2:

If the number of inputs to the DTL NAND gate in **Exercise 3**, is increased to 5, what will be the maximum & average power dissipation?

Ans: 55.5 mW, 45.85 mW

Fanout

Exercise 4

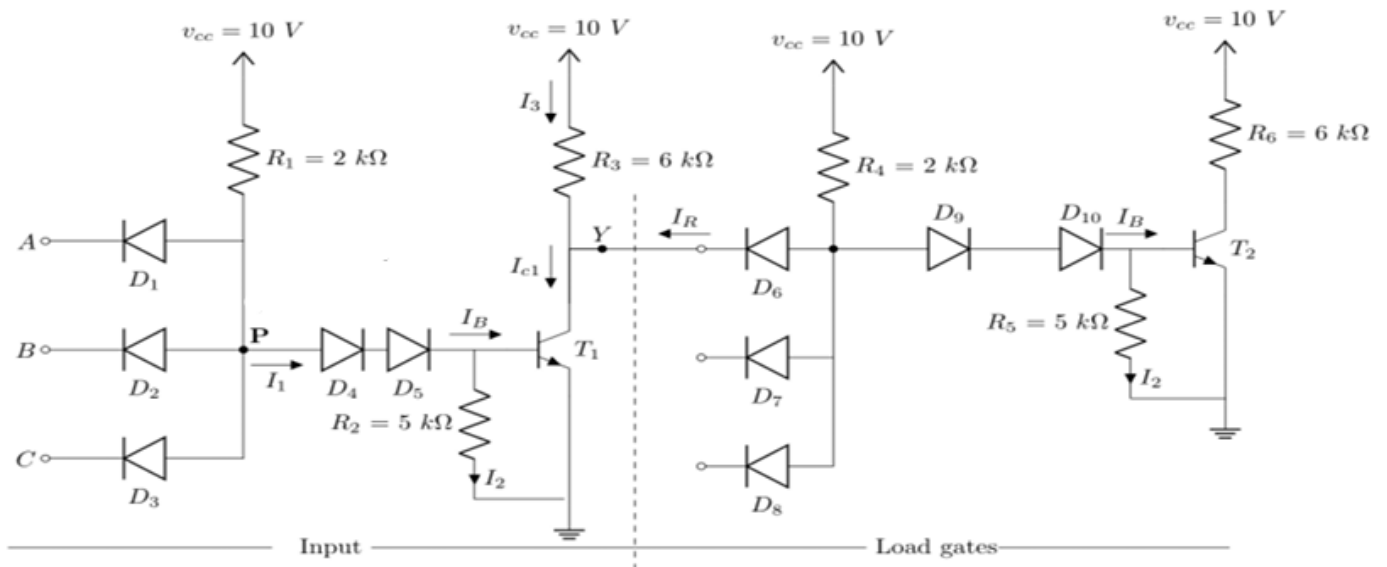

For the above circuit- $V_{OH} = 9.5\text{ V}$, $V_{OL} = 0.1\text{ V}$, $\beta_F = 30$

- Find the maximum fanout.
- Find the maximum power dissipation of the driver circuit, when N (maximum fanout) loads are connected.

Ans: a) 24
b) 66.54 mW

Practice Problem 3:

Find the value of R_3 that would reduce the maximum fanout found in **Exercise 4** to 20.

Ans: 490 Ω

Exercise 5


- Ans: a) 8.654
b) 35
c) 4.4387 mW, 73.82 mW
d) 10.4 V

Practice Problem 4:

If at least one input is low, what is the magnitude of the noise voltage at input A, that would cause the gate to malfunction in **Exercise 5**?

Ans: 0.8 V

Exercise 6

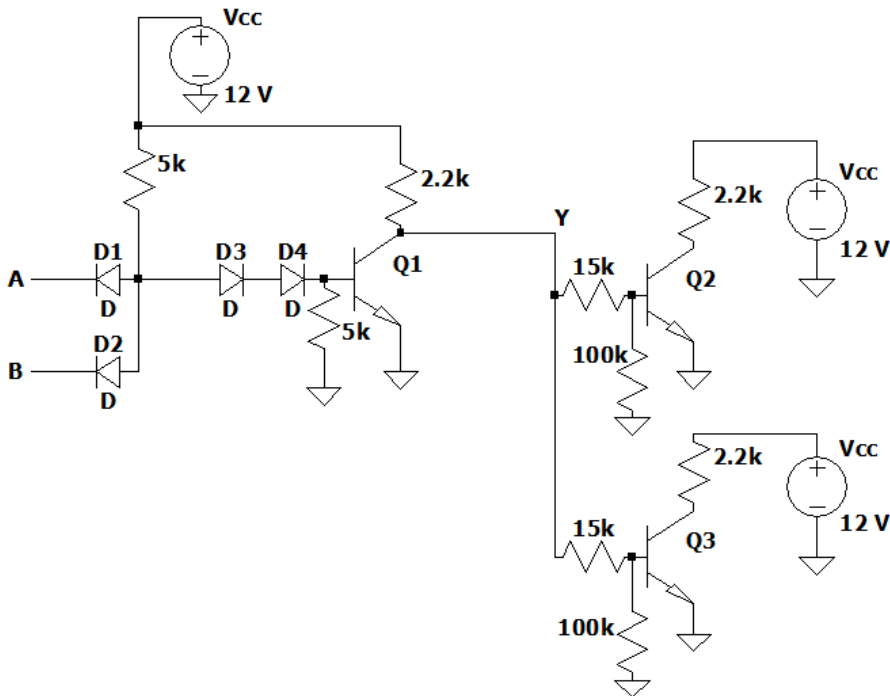

For the given circuit:

$V_{OH} = 10\text{ V}$, $V_{OL} = 0.2\text{ V}$, $\beta_F = 30$

- When $N=1$, what logic function do we get from the output of the load?
- Find the maximum fanout.
- For $N=\text{maximum fanout}$, find the maximum power dissipation in the loads.

Ans: a) $Y = \overline{AB}$
b) 1
c) 70.5 mW

Exercise 1

Solution:

For transistor T to be in saturation, at least 0.5 V must be between the base & emitter. For D_3 & D_4 both to be on, $0.6+0.6=1.4$ V is required. Thus, the required voltage for D_3, D_4 & T to be on, at P,


$$V_P = 0.6 \times 2 + 0.5 = 1.7 \text{ V}$$

Case (0,0):

Assuming D_1 & D_2 to be on (since low voltage 0.2 V at cathode), we get,

$$V_P = 0.2 + 0.7 = 0.9 \text{ V} < 1.7 \text{ V}$$

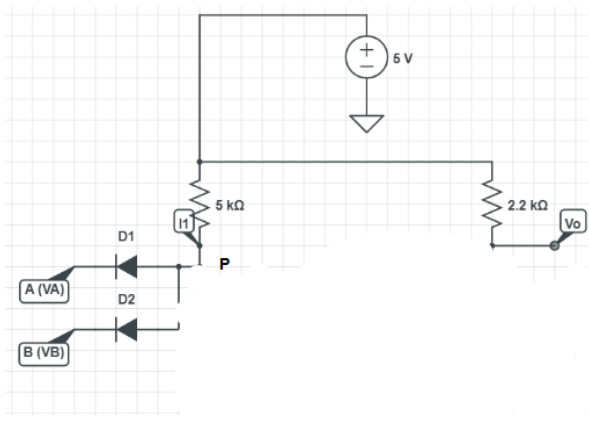Thus, D_3, D_4 & T will be off. This leads to an open circuit-



Thus, $V_o = 5 \text{ V}$

$$I_{5k\Omega} = \frac{5 - V_P}{5} = \frac{5 - 0.9}{5} = 0.82 \text{ mA}$$


$$I_{D_1} = I_{D_2} = \frac{I_{5k\Omega}}{2} = 0.41 \text{ mA}$$

Case (0,1):

Assuming D_1 on & D_2 off,

$$V_P = 0.2 + 0.7 = 0.9 < 1.7 \text{ V again.}$$

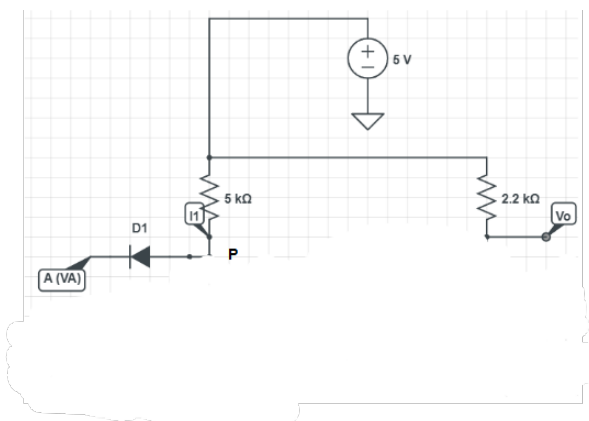Thus, D_3, D_4 & T will be off. This leads to an open circuit-



$V_o = 5 \text{ V}$

$$I_{5k\Omega} = \frac{5 - 0.9}{5} = 0.82 \text{ mA}$$

$$I_{D_1} = I_{5k\Omega} = 0.82 \text{ mA}$$


Case (1,0): Same as (0,1)

Case (1,1):

Assuming both D_1 & D_2 off, D_3 , D_4 & T can be assumed on, since there is no bound of V_P from the input diodes. Each diode will have 0.7 V & there will be 0.8 V between the base and emitter of T.

Thus, $V_P = 0.7 + 0.7 + 0.8 = 2.2 \text{ V}$

The circuit looks like:

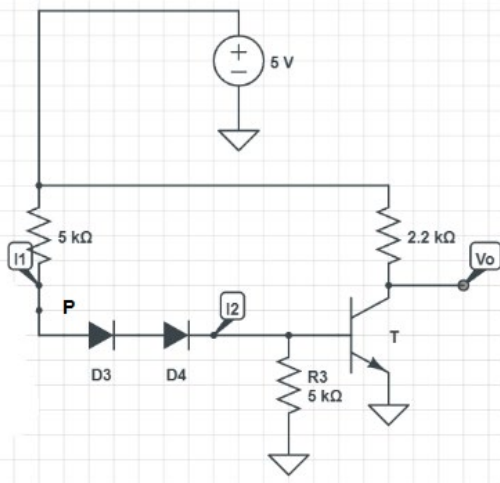

$$V_o = V_{CE_T} = 0.2 \text{ V}$$


$$I_{5V} = I_1 + I_{2.2k\Omega} = \frac{5-2.2}{5} + \frac{5-0.2}{2.2} = 2.74 \text{ mA}$$

$$I_{R_3} = \frac{0.8}{5} = 0.16 \text{ mA}$$

Exercise 2

Solution:

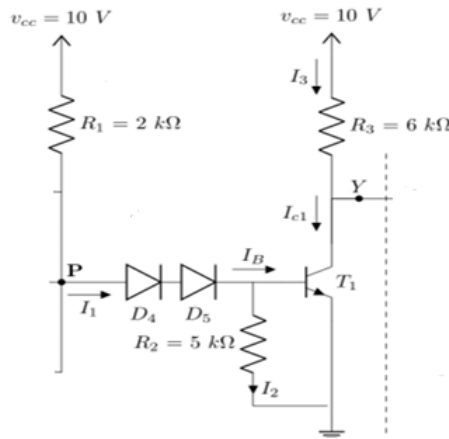a) D_1, D_2, D_3 all off. $V_P = 0.7 \times 2 + 0.8 = 2.2 \text{ V}$



$$I_{R_1} = \frac{10 - V_P}{2} = \frac{10 - 2.2}{2} = 3.9 \text{ mA}$$

$$I_2 = \frac{0.8}{5} = 0.16 \text{ mA}$$

$$\therefore I_B = I_{R_1} - I_2 = 3.9 - 0.16 = 3.74 \text{ mA}$$

$$I_C = I_{R_3} = \frac{10 - 0.1}{6} = 1.65 \text{ mA}$$

$$\therefore \beta_{min} = \frac{I_C}{I_B} = 0.441$$

This is the minimum value of β to keep T in saturation.

b) Let V_N be the noise voltage at A, that would cause the malfunction.

Thus, total voltage at input A = $10 + V_N$

It will malfunction if D_A turns on. The marginal voltage across the diode for this situation is the cut-in voltage (0.6 V) of the diode.

Thus, $V_{D_A} = 0.6 = V_P - (10 + V_N)$

Now, we found in (a), $V_P = 2.2 \text{ V}$ when all inputs are high.

So, $V_N = 2.2 - 0.6 - 10 = -8.4 \text{ V}$

Magnitude of $V_N = |-8.4| = 8.4 \text{ V}$

c) If at least one input is low, it will cause D_4, D_5 & T_1 to be off.

Thus, $V_P = 0.1 + 0.7 = 0.8 \text{ V}$ when no noise is present.

Let, V_N is the noise voltage.

Then, malfunction will happen when due to V_N , V_P will be high enough to turn D_4, D_5 & T_1 on.

$$V_{P_{malfunction}} = (V_{D_1})_{cut-in} + (V_{D_2})_{cut-in} + V_{T_{1Y}} = 0.6 \times 2 + 0.5 = 1.7 \text{ V}$$

$$V_P = V_N + 0.1 + 0.7 = V_N + 0.8$$

Considering marginal condition,

$$V_P = V_{P_{malfunction}} \rightarrow V_N + 0.8 = 1.7 \rightarrow V_N = 0.9$$

Exercise 3


Solution:

- a) Case (at least one input low) [(0,0,0), (0,0,1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1), (1, 1, 0)]:

As we found in **Exercise 2**,

$$V_P = 0.1 + 0.7 = 0.8 \text{ V}$$

D_4, D_5, T_1 all off

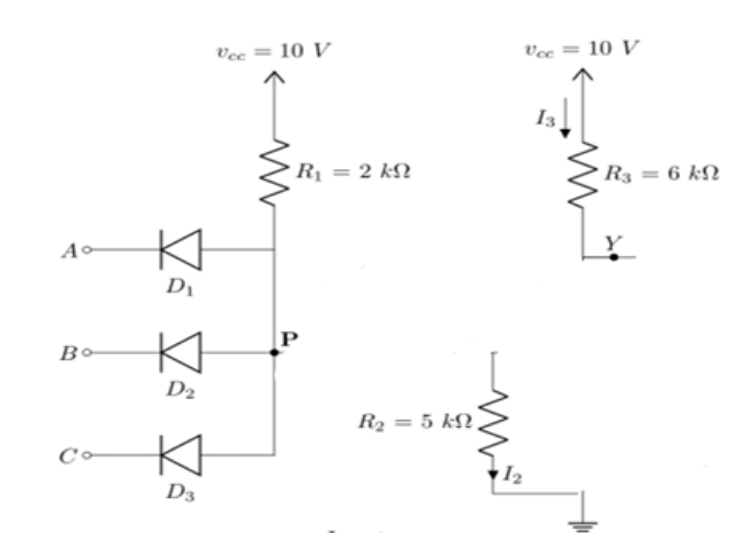


$$P = (10 - 0.1) \times I_{R_1} = 9.9 \times \frac{10 - 0.8}{2} = 45.54 \text{ mW}$$

Case (1,1,1):

From **Exercise 2**, we found that for this case, $V_P = 2.2\text{ V}$

D_4, D_5, T_1 all on

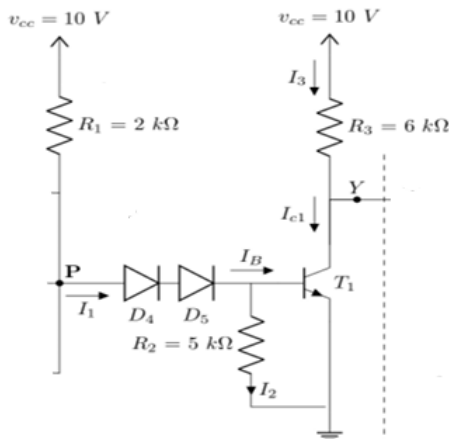

$$P = (10 - 0) \times I_{R_1} + (10 - 0) \times I_{R_3} \\ = 10 \times \frac{10-2.2}{2} + 10 \times \frac{10-0.1}{6} = 55.5\text{ mW}$$

b) $P_{max} = \max(55.5, 45.54) = 55.5\text{ mW}$

$$P_{avg} = \frac{7 \times 45.54 + 55.5}{8} = 46.785\text{ mW}$$

Exercise 4

Solution:

a) **Step 1:**

Current flows from loads toward the driver circuit. Thus, the condition for maximum fanout is the marginal case, when T_1 transitions from saturation to forward active.

Step 2:

Case (at least 1 input low at the driver):

Output V_Y is high, which turns D_6 of loads off. Thus, no current enters the driver circuit.

$$\therefore \text{Fanout} = \infty$$

Case (all inputs high):

Output V_Y is low, D_6 is on. KCL at Y,

$$I_{c1} = I_3 + I_R = \frac{10-0.1}{6} + \frac{10-0.8}{2} \times N = 1.65 + 4.6N$$

Here, we have considered the case (1,0,0) at all N loads connected. This is because maximum current will flow through D_6 in this situation, as all other diodes & T_2 will be off. The anode node voltage of D_6 will be 0.8 V for the same reasons described in previous examples (0.1+0.7).

$$I_B = I_1 - I_2 = \frac{10-2.2}{2} - \frac{0.8}{5} = 3.74 \text{ mA}$$

$$\text{Now, } \beta_{forced} = \frac{I_C}{I_B} = \beta_F = 30 \rightarrow \frac{1.65+4.6N}{3.74} = 30 \rightarrow N = \text{floor} \left(\frac{3.74 \times 30 - 1.65}{4.6} \right) = 24$$

Step 3:

$$\therefore \text{Maximum fanout} = \min(\infty, 24) = 24$$

b) We see, the difference in this case from the previous problem is that, the load currents will add to the collector current of T_1 . The load currents I_R will flow between V_Y & ground. Thus,

$$\begin{aligned} P_{max} &= (10 - 0) \times I_1 + (10 - 0) \times I_3 + (V_Y - 0) \times I_R \times N \\ &= 10 \times \frac{10-2.2}{2} + 10 \times \frac{10-0.1}{6} + (0.1 - 0) \times 24 \times \frac{10-0.8}{2} = 66.54 \text{ mW} \end{aligned}$$

Exercise 5

Solution:

a) When all inputs are high,

T_1 in forward active mode, D_2 on, T_2 in saturation mode, and load diodes are off. Hence, loads are disconnected.

$$\text{Thus, } I_{C_{T_2}} = I'_1 = \frac{12-0.1}{2.2} = 5.41 \text{ mA}$$

$$I_{B_{T_2}} = i_1 - \frac{0.8}{100} = (\beta_F + 1) \times I_{C_{T_1}} - 0.008 = (30 + 1) \times \frac{V_{C_{T_1}} - 2.2}{15} - 0.008$$

Now, KCL at $V_{C_{T_1}}$,

$$\frac{V_{C_{T_1}} - 2.2}{15} + 30 \times \frac{V_{C_{T_1}} - 2.2}{15} = \frac{(12 - V_{C_{T_1}})}{15} \rightarrow V_{C_{T_1}} = 2.51 \text{ V}$$

$$\text{Thus, } I_{B_{T_2}} = 0.625 \text{ mA}$$

$$\therefore \beta_{forced} = \frac{I_{C_{T_2}}}{I_{B_{T_2}}} = 8.654 < \beta_F(30)$$

b) Step 1:

The current flows from the loads toward the driver. Thus, the condition for maximum fanout is the marginal condition when T_2 transitions from saturation to forward active.

Step 2:

Cases with at least one low input:

T_1, D_2, T_2 all off

Output is high, and all load diodes will be off.

$$\therefore \text{Fanout} = \infty$$

Case (1,1,1):

T_1 in forward active mode, D_2 on, T_2 in saturation mode

$$I_{C_{T_2}} = I'_1 + N \times I_L = \frac{12-0.1}{2.2} + N \times \frac{12-0.1-0.7}{15+15} = 5.41 + 0.373N$$

$$I_{B_{T_2}} = 0.625 \text{ mA}$$

$$\therefore \frac{5.41+0.373N}{0.625} = 30 \rightarrow N = 35$$

$$\text{c) } P_{\text{at least one input is low cases}} = (12 - 0.1) \times I_1 = 11.9 \times \frac{12-0.7-0.1}{15+15} = 4.4387 \text{ mW}$$

$$P_{1,1,1} = (12 - 0) \times \frac{12-V_{C_{T_1}}}{15} + (0.1 - 0) \times N \times I_1 = 12 \times \frac{12-2.51}{15} + 0.1 \times 35 \times 0.373 = 73.82 \text{ mW}$$

$$\text{d) } V_A + V_{D_A} = V_P = 2.2 \rightarrow 12 + V_N + 0.6 = 2.2 \rightarrow V_N = -10.4 \text{ V}$$

$$\therefore |V_N| = 10.4 \text{ V}$$

Exercise 6**Solution:**

$$\text{a) } Y = \overline{AB}$$

b) Step 1:

Current flows from driver to loads. Hence, the condition for maximum fanout is supply-demand balance.

Step 2:

Case (1,1):

D_3, D_4, Q_1 on, $D_1 \& D_2$ off

Maximum supply current from the driver, $I_{2.2k} = \frac{12-0.2}{2.2} = 5.363 \text{ mA}$

Since the output of the driver is low, loads will be off. Thus, demand current = 0.

$$\therefore \text{Fanout} = \frac{5.363}{0} = \infty$$

Case (0,0)/(0,1)/(1,0):

D_3, D_4, Q_1 off, D_1 & D_2 on

Maximum supply current from the driver, $I_{2.2k} = \frac{12-10}{2.2} = 0.91 \text{ mA}$

Since the output of the driver is high, loads will be in saturation. Thus demand current,

$$I_L = \frac{10-0.8}{15} = 0.613 \text{ mA}$$

$$\therefore \text{Fanout} = \text{floor} \left(\frac{0.91}{0.613} \right) = 1$$

Step 3:

$$\therefore \text{Maximum fanout} = \min(1, \infty)$$

- c) N=1 load will be in saturation mode when driver output is high. Thus, maximum power dissipation in the single load,

$$P_{max} = (10 - 0) \times I_L + (12 - 0) \times I_{C_{load}} = 10 \times \frac{(10-0.8)}{15} + 12 \times \frac{12-0.2}{2.2} = 70.5 \text{ mW}$$