

CSE 350

Digital Electronics and Pulse Techniques

NMOS NOT and NOR without load
CMOS Logic Circuit Design

Course Instructor: Shomen Kundu (SDU)

Mail: shomen.kundu@bracu.ac.bd
Desk: 4N166



Inspiring Excellence

MOS Logic family



Unipolar logic family: current conduction is done by one type of charge carriers.

e.g. electron or hole




Basic Internal Structure

  
If some MOSFET is fabricated identically then source and body might be shorted.



Circuit Symbol

 

N-MOS

 

p-MOS



Basic Operation

If we apply voltage in the gate terminal.

Accumulation: If V_G is less than zero, holes inside p-type semiconductor might accumulate underneath the oxide layer.


Depletion: If $0 < V_G < V_{TN}$, then depletion layer forms beneath the oxide layer.

Inversion: If $V_G > V_{TN}$, then an inversion layer would emerge under the oxide layer.




Basic Operation

 Now if we apply $V_{GS} > V_{TN}$, a channel forms.




NMOS for small V_{DS}

 


NMOS for increased V_{DS}

Basic Operation

 Now if we apply $V_{GS} > V_{TN}$, a channel forms.



 Edge of Saturation, $V_{DS} = V_{GS} - V_{TN}$



Saturation, $V_{DS} > V_{GS} - V_{TN}$

Operating modes of MOSFET

Operating modes of n-MOSFET,

➤ Cut-off

$$V_{GS} < V_{TN}, I_D = 0$$

➤ Triode/Linear

$$V_{GS} > V_{TN} \text{ and } V_{DS} < V_{GS} - V_{TN}$$

$$I_D = K_n (2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2)$$

➤ Saturation

$$V_{GS} > V_{TN} \text{ and } V_{DS} > V_{GS} - V_{TN}$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

Note: $K_n = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$



N-MOS Logic


Pull up network: High resistance

Pull down network: n-MOS


Logic design techniques:

- Series n-MOS indicates AND
- Parallel n-MOS indicates OR
- Overall n-MOS logic is inverted


N-MOS Logic

 

NOT

 


NAND

 

NOR

N-MOS NOT gate/Inverter

 Find the output of the inverter for the input volta
5 V and 1.5 V. Given $V_{TN} = 0.5 \text{ V}$, $R = 20 \text{ k}$,
 $V_{DD} = 5 \text{ V}$, $K_n = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} = 0.3 \text{ mA/V}^2$



N-MOS NOT gate/Inverter

When $V_I = 5\text{ V}$

$$V_{GS} = 5\text{ V} > V_{TN},$$

MOSFET M1 is in Saturation / Triode region.


Assumption: Triode mode

$$I_D = K_n (2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2)$$

$$I_D = 0.3 (2 * (5 - 0.5)V_o - V_o^2)$$

$$= 0.3 (9V_o - V_o^2)$$

$$I_D = \frac{5 - V_o}{20}$$

 

N-MOS NOT gate/Inverter

$$I_D = 0.3 (9V_o - V_o^2)$$

$$I_D = \frac{5 - V_o}{20}$$

So, we can write,

$$0.3 (9V_o - V_o^2) = \frac{5 - V_o}{20}$$

Solving using calculator,


$$V_o = 9.074 \text{ V or } 0.092 \text{ V}$$

Acceptable value, $V_o = 0.092 \text{ V}$

Verification:

$$V_{DS} = 0.092 \text{ V and } V_{GS} - V_{TN} = 4.5 \text{ V}$$

 As $V_{DS} < V_{GS} - V_{TN}$, Assumption correct.



N-MOS NOT gate/Inverter

When $V_I = 1.5\text{ V}$


$$V_{GS} = 1.5\text{ V} > V_{TN},$$

MOSFET M1 is in Saturation / Triode region.

Assumption: Saturation mode

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$I_D = 0.3(1.5 - 0.5)^2$$

 

$$I_D = \frac{5 - V_O}{20}$$

N-MOS NOT gate/Inverter

So, we can write,

$$0.3 (1.5 - 0.5)^2 = \frac{5 - V_o}{20}$$

Solving using calculator,


$$V_o = -1 \text{ V}$$

Verification:

$$V_{DS} = -1 \text{ V and } V_{GS} - V_{TN} = 1 \text{ V}$$

As $V_{DS} < V_{GS} - V_{TN}$, Assumption not correct.

 We need to assume triode mode as saturation assumption is not correct.




N-MOS NOT gate/Inverter

$$\begin{aligned} I_D &= K_n (2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2) \\ I_D &= 0.3 (2 * (1.5 - 0.5)V_o - V_o^2) \\ &= 0.3 (2V_o - V_o^2) \\ I_D &= \frac{5 - V_o}{20} \end{aligned}$$

So, we can write,

$$\begin{aligned} 0.3 (2V_o - V_o^2) &= \frac{5 - V_o}{20} \\ \Rightarrow 12V_o - 6V_o^2 &= 5 - V_o \end{aligned}$$


Now Solve and verify

 

N-MOS NOT gate/Inverter

Find the transition voltage(Saturation to triode) of the inverter. Given
 
$$V_{TN} = 0.5 \text{ V}, R = 20 \text{ k}\Omega, K_n = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} = 0.3 \text{ mA/V}^2$$



N-MOS NOT gate/Inverter


$$\text{For transition, } V_{DS} = V_{GS} - V_{TN}$$
$$V_o = V_I - 0.5$$

$$\text{Now, } I_D = 0.3 (V_I - 0.5)^2 = \frac{5 - V_o}{20}$$

$$\Rightarrow I_D = 0.3 V_o^2 = \frac{5 - V_o}{20}$$

$$\text{Solving, } V_o = 0.5675 V$$

$$V_I = V_o + 0.5 = 1.0675 V$$

 


N-MOS NOR gate

Here, $V_{TN} = 0.8\text{ V}$ and $K_n = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} = 0.1\text{ mA/V}^2$

We can study this NOR gate, with four possible cases.

We need to find out I_1, I_2, I, V_o and power of the NOR gate

0	0	
0	5V	
5V	0	
5V	5V	

 

N-MOS NOR gate

Case 01: $V_1 = V_2 = 0V$

$$V_{GS1} = 0 < V_{TN},$$


$M1 \rightarrow \text{Cut off Mode}, I_{D1} = 0 \text{ mA}$

$$V_{GS2} = 0 < V_{TN}$$

$M2 \rightarrow \text{Cut off Mode}, I_{D2} = 0 \text{ mA}$

$$I = I_{D1} + I_{D2} = 0 \text{ mA}$$

$$V_o = 5 \text{ V}$$

 

N-MOS NOR gate

Case 02: $V_1 = 0V, V_2 = 5V$

$$V_{GS1} = 0 < V_{TN},$$

$M1 \rightarrow \text{Cut off Mode}, I_{D1} = 0 \text{ mA}$

$$V_{GS2} = 5 > V_{TN}$$

Assume M2 in Triode mode

$$I_{D2} = 0.1 (2(5 - 0.8)V_o - V_o^2)$$

$$I = I_{D1} + I_{D2}$$


$$\frac{5 - V_o}{20} = 0.1 (2(5 - 0.8)V_o - V_o^2)$$

Solving,

$$V_o = 8.6 \text{ V or } 0.29 \text{ V (8.6 V is not acceptable)}$$

Verification: $V_{DS} = 0.29 \text{ V}$ and $V_{GS} - V_{TN} = 4.2 \text{ V}$

 
As, $V_{DS} < V_{GS} - V_{TN}$, M2 is in Triode



N-MOS NOR gate

Case 03: $V_1 = 5\text{ V}$, $V_2 = 0\text{ V}$

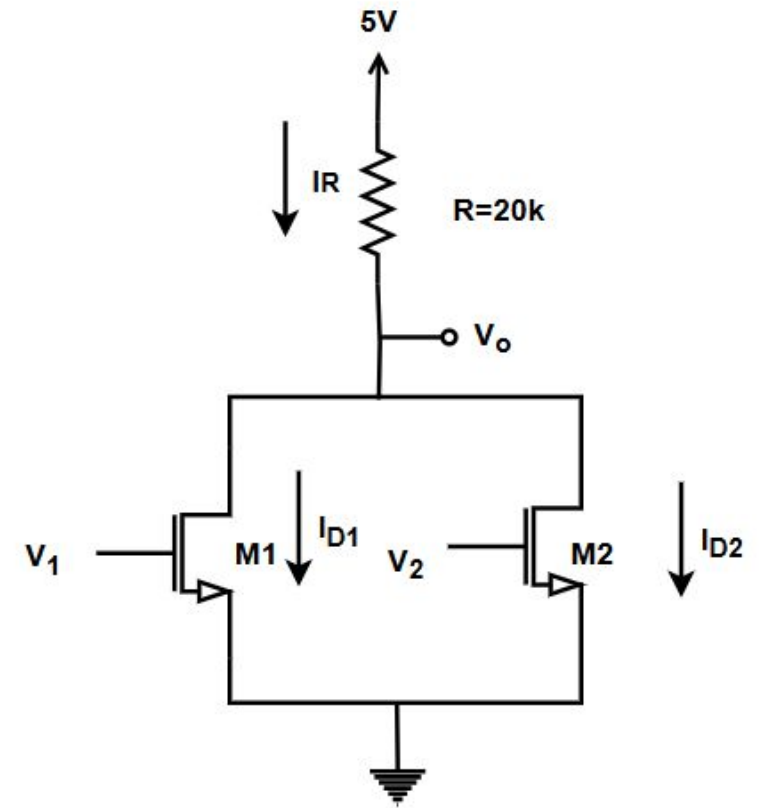Similar to case 2,
 $\Rightarrow V_o = 0.29\text{ V}$



N-MOS NOR gate

Case 04: $V_1 = V_2 = 5V$

$$V_{GS1} = 5 > V_{TN},$$

$M1 \rightarrow \text{Triode}$

$$V_{GS2} = 5 > V_{TN}$$


$M2 \rightarrow \text{Triode}$

$$I = I_{D1} + I_{D2}$$

$$\Rightarrow \frac{5 - V_o}{20} = 2 * 0.1 (2(5 - 0.8)V_o - V_o^2)$$

$$V_o = 0.149 V \text{ or } 4.17 V (4.17 V \text{ is not acceptable})$$


$$\Rightarrow V_o = 0.149 V$$

 

 Exercise:

For the Given NMOS find the power for all possible input cases. Also find it's average power.

Given: $K_n = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} = 100 \frac{\mu A}{V^2}$, $V_{TN} = 1V$. *Logic High* = 5V and *Logic Low* = 0V




CMOS

Complementary MOS circuit design

Features,

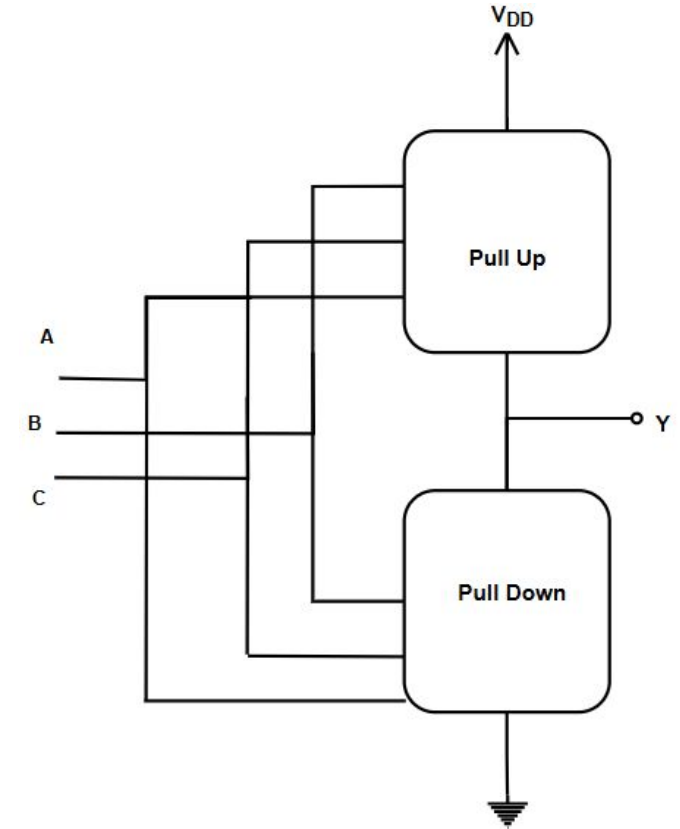
- I. In CMOS circuit there are two network, one is pull up and other is pull down.
- II. At a time either pull-up or pull-down network is on.
- III. Logic is high when pull up is on.
- IV. Logic is Low when pull down is on.
- V. Pull down consist of N-MOS, Pull up consist of P-MOS.



CMOS Pull Down Network Design

$\cdot \rightarrow$ AND can be implemented by series of two NMOS
 $+$ \rightarrow OR can be implemented by Parallel NMOS
lower part will be connected with GND
Upper part will be connected to the Output


Example: $Y = \overline{AB + C}$

 

CMOS Pull Up Network Design

- \rightarrow AND can be implemented by parallel of two PMOS
 - + \rightarrow OR can be implemented by Parallel NMseries of two NMOS
- Lower part will be connected to the Output
Upper part will be connected with V_{DD}


Example: $Y = \overline{AB} + C$

 

NOT Gate


•

$$Y = \bar{A}$$

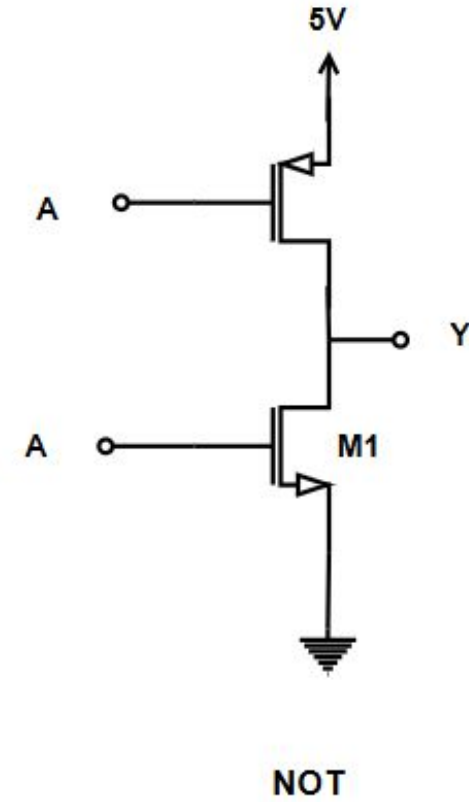

NAND Gate


$$Y = \overline{AB}$$

 

(a) Symbol

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


(b) Truth table

 

NOR Gate

•


$$Y = \overline{A + B}$$

 

(a) Symbol


A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

(b) Truth table

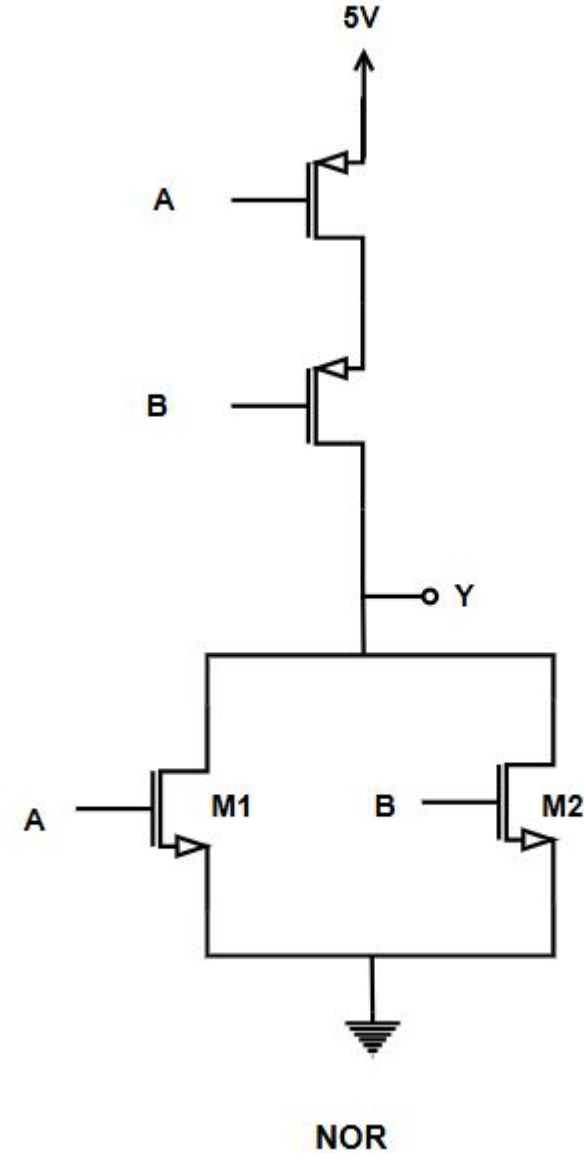

Example:

$$Y = \overline{AB + C}$$

 


(a) Logic circuit

A	B	C	f	
0	0	0	1	
0	0	1	0	← C=1
0	1	0	1	
0	1	1	0	← C=1
1	0	0	1	
1	0	1	0	← C=1
1	1	0	0	← A·B=1
1	1	1	0	← C=1

(b) Function table

Example:

$$Y = \overline{A(B + C)}$$

 

(a) Logic circuit


A	B	C	g
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

← $A \cdot C = 1$
 ← $A \cdot B = 1$
 ← $A \cdot (B + C) = 1$

(b) Function table


Example:

$$Y = \overline{A(B + C) + DE}$$

 

 Exercise:

Design a CMOS logic circuit to implement the given compound gate in Figure below. First derive the logical expression of output Y and then design the CMOS network.



Exercise:

Design a CMOS circuit that will follow the given truth table.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0



Exercise:

Design static CMOS circuit for the following expression,

$$Y = AB + C$$

$$Y = (A+B)C$$

$$Y = (A+B)(C+D)$$

$$Y = \overline{AB} + \overline{CD}$$

$$Y = \overline{AB + C}$$

$$Y = \overline{(A + B)C}$$

$$Y = \overline{(A + B)(C + D)}$$

$$Y = \overline{A} + \overline{B} + \overline{C}$$

