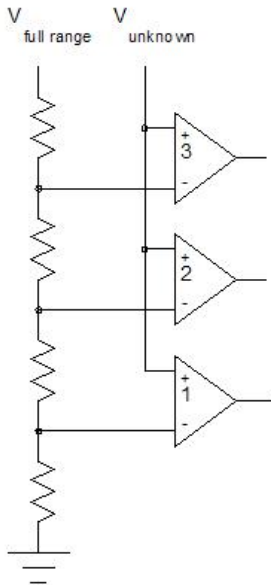


## ADC and DAC practice problem

1. An analog signal in the range of -5V to 5V is to be converted to a digital signal. Suppose a 2 bit quantization will be implemented.

- a. What is the step size of the ADC circuit?
- b. How many quantization levels are there ?
- c. Find the maximum value of the quantization error.
- d. Calculate the number of resistors and OP-AMP required for the Flash ADC circuit.
- e. Make a table with quantization range, quantization level and encoded binary value.
- f. At some instances the signal values of the ADC circuit are 3.35V, -2.67V and 1.14 V. Find corresponding encoded binary value.
- g. Explain the input and output relationship of the Encoder with a table.

2.



Here,

$R = 10\text{ k}$ ,  $V_{\text{fullrange}} = 10\text{ V}$ . ( Reference Voltage)

- a. What will be the output binary bits line for the above circuit?
- b. Draw the quantization level vs Input signal plot.
- c. If  $V_{\text{unknown}} = 3.5\text{ V}$ , what will be the quantization error for this case? ( Quantization error = Actual value - Quantized value)


3.  $x(t) = 5 + 5 \sin ( 2\pi \cdot f \cdot t )\text{ V}$

Where  $f = 2\text{ k Hz}$ .

Above signal will be converted to a digital signal through an ADC circuit.

- a. What will be the minimum required sampling frequency for this signal?
- b. Suppose, the sampling frequency is set at 10 kHz. Find the first 5 sampling values as well as their corresponding quantized value and encoded value.

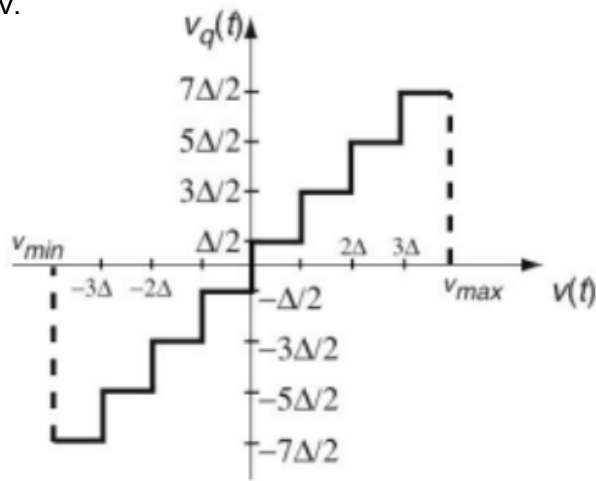
4. The following plot is the relationship between input and output of a midrise quantizer. Where the step size is 2V.



midrise quantizer


- What is the number of binary bits required to express the quantization levels?
  - Find the corresponding quantized value if the inputs of the quantizer are -5.6 V and 7.34 V.
  - What will be the maximum value of the quantization error?
  - Design a full ADC circuit consisting of maximum current of the circuit should not exceed 0.1 mA.
5. Design a 4 binary weighted DAC circuit with reference voltage of 5 V and maximum output voltage of 15V.

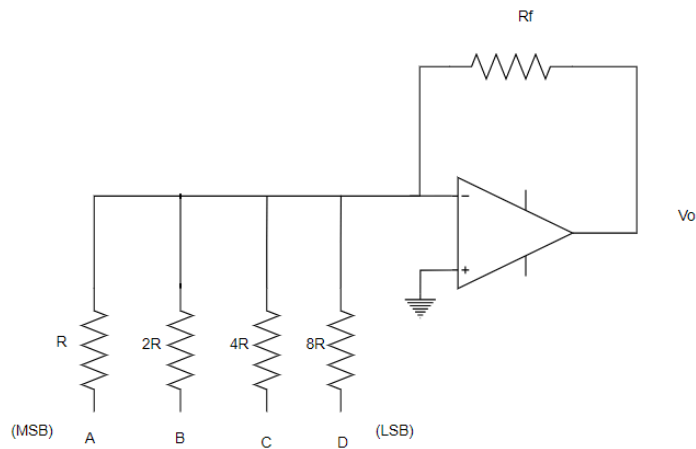6. Here  $R_f = 2\text{ k}\Omega$  and  $R = 4\text{ k}\Omega$ ,  $V_{ref} = -5\text{ V}$ .



- What will be the maximum and minimum output voltages?
- What is the step size of this DAC circuit?
- What is the resolution of this DAC scheme?
- Make a table for all the combinations of inputs and outputs.
- Find the output value for the binary inputs 1101, 0001 and 1110, 0001, 1000

7. Here  $V_{ref} = -2\text{ V}$

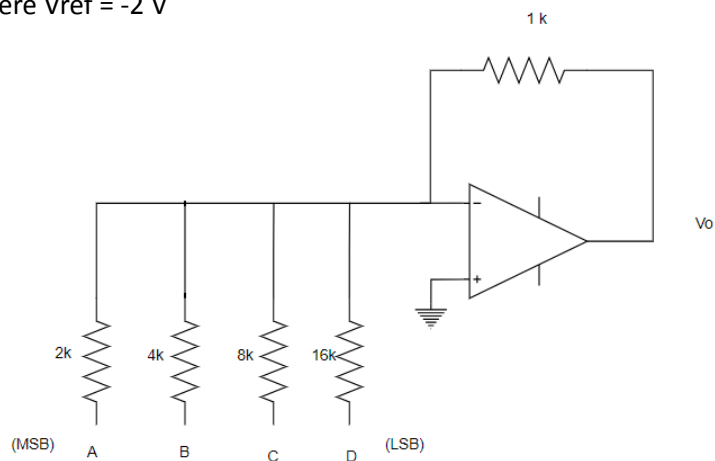

- Calculate the output value for 1111 and 1010 input value.
- What will be the resolution of this circuit?
- Redesign the circuit by changing the value of the feedback resistor so that maximum output voltage will be 7.5 V.

## Solution to ADC and DAC Practice Problem

$$1.a) \text{ Step size} = \frac{V_{\max} - V_{\min}}{2^n}$$

$$= \frac{5 + 5}{2^2}$$

$$= 2.5 \text{ V}$$

1.b) Number of quantization level

$$= 2^n$$

$$= 2^2$$

$$= 4$$

1.c) Maximum value of quantization error

$$= \frac{\Delta}{2}$$

$$= \frac{2.5}{2}$$

$$= 1.25 \text{ V}$$

$$1.d) \# \text{ of resistors} = 2^n = 2^2 = 4$$

$$\# \text{ of OP-AMP} = 2^n - 1 = 2^2 - 1 = 3$$



**ULKASEMI**

We are Integrating your Ideas

web: [www.ulkasemi.com](http://www.ulkasemi.com)  
e-mail: [info@ulkasemi.com](mailto:info@ulkasemi.com)

1.e) Here,  $\Delta = \frac{5 - (-5)}{2^4} = 1.25 \text{ V}$

Q. Range	Q. level	Encoded Value ( $b_2 b_1$ )
-5 — -2.5	-3.75	00
-2.5 — 0	-1.25	01
0 — 2.5	+1.25	10
2.5 — 5	+3.75	11


1.f) From previous table (1.e)

if,  $V_{sig} = 3.35 \text{ V}$ , encoded binary ( $b_2 b_1$ ) = 11

$V_{sig} = -2.67 \text{ V}$ , " " " = 00

$V_{sig} = 1.14 \text{ V}$ , " " " = 10

1.g) Encoder required,

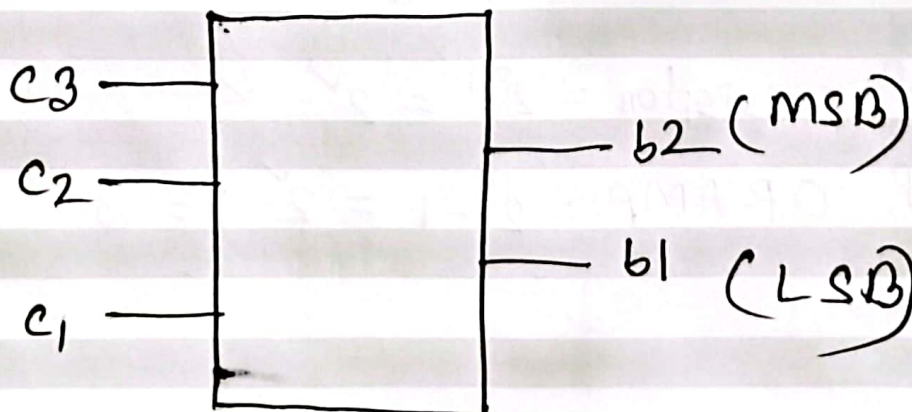



Input output relation table,

$c_3 c_2 c_1$	$b_2 b_1$
0 0 0	0 0
0 0 1	0 1
0 1 1	1 0
1 1 1	1 1

The block is a priority encoder with the priority sequence,  $c_3 > c_2 > c_1$


2.a) There are 4 resistors.

$$4 = 2^n$$

$$\Rightarrow n = 2$$

$\therefore$  Number of output bits line = 2

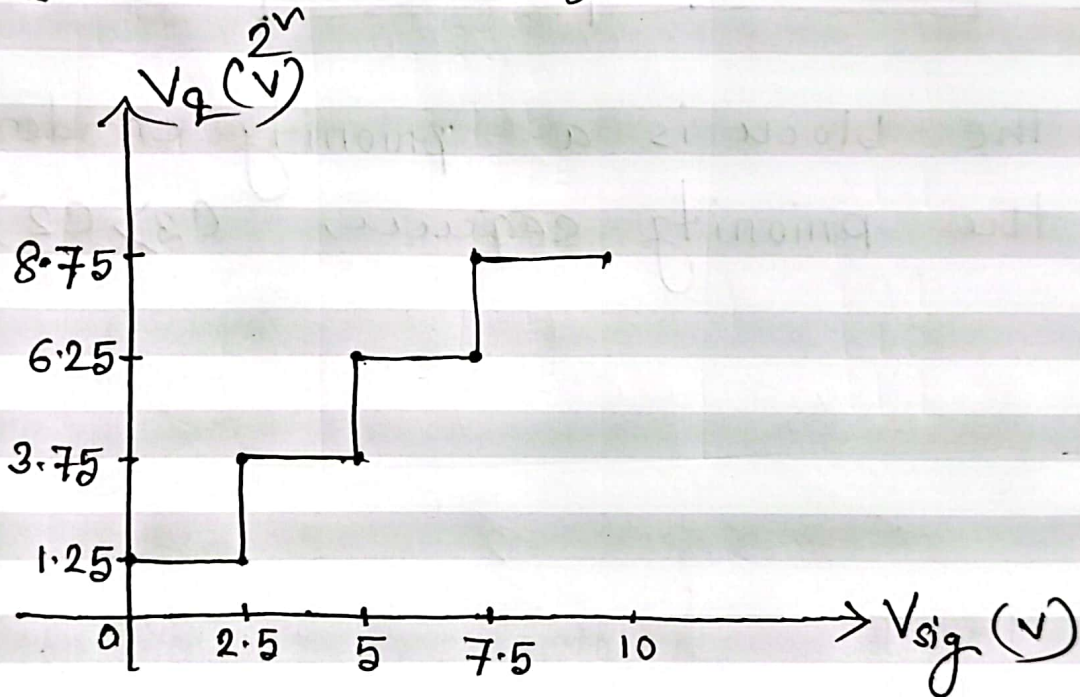2.b)  $\Delta = \frac{10 - 0}{2^2} = 2.5 \text{ V}$



2.c)  $V_{sig} = 3.5 \text{ V}$

This value is within the range 2.5 V to 5 V

$V_q = \frac{2.5 + 5}{2} = 3.75 \text{ V}$

Quantization Error =  $3.5 - 3.75 = -0.25 \text{ V}$



$$3. a) f_{\text{sampling}} \geq 2 \times f_{\text{sig}}$$

$$f_{\text{sampling}} \geq 2 \times 2 \text{ kHz}$$

$$f_{\text{sampling}} \geq 4 \text{ kHz}$$

∴ Minimum sampling freq. is 4 kHz

$$3. b) x(t) = 5 + 5 \sin(2\pi f t)$$

$$f = 2 \text{ kHz}, \quad f_s = 10 \text{ kHz}$$

$$\text{Sampling interval, } T_s = \frac{1}{f_s}$$

$$\therefore f \times T_s = \frac{f}{f_s} = \frac{2 \text{ k}}{10 \text{ k}} = \frac{1}{5}$$

$$t = 0, \quad x(0) = 5 + 0 = 5 \text{ V}$$

$$t = T_s, \quad x(T_s) = 5 + 5 \sin 2\pi f \times T_s = 5 + 5 \sin 2\pi \times \frac{1}{5} = 9.76 \text{ V}$$

$$t = 2T_s, \quad x(2T_s) = 5 + 5 \sin 2\pi \times \frac{2}{5} = 7.94 \text{ V}$$

$$t = 3T_s, \quad x(3T_s) = 5 + 5 \sin 2\pi \times \frac{3}{5} = 2.06 \text{ V}$$

$$t = 4T_s, \quad x(4T_s) = 5 + 5 \sin 2\pi \times \frac{4}{5} = 0.2447 \text{ V}$$



Table for ADC,

$$\Delta = \frac{V_{\max} - V_{\min}}{2^n} = \frac{10 - 0}{2^3} = 1.25$$

[connection: 3 bit binary system]

Q. Range	Q. level	Binary (b2 b1 b0)
0 - 1.25	0.625	000
1.25 - 2.5	1.875	001
2.5 - 3.75	3.125	010
3.75 - 5	4.375	011
5 - 6.25	5.625	100
6.25 - 7.5	6.875	101
7.5 - 8.75	8.125	110
8.75 - 10	9.375	111

taking the lower range

From the Table	$V_x(t)$	$V_q$	b2 b1 b0
$t = 0$	5	4.375	011
$t = T_s$	9.76	9.375	111
$t = 2T_s$	7.94	8.125	110
$t = 3T_s$	2.06	1.875	001
$t = 4T_s$	0.2447	0.625	000



4.a) There are 8 quantization level in  $y$  axis

$$2^n = 8$$

$$n = 3$$

4.b) Given,  $\Delta = 2V$  ;

$$V(t) = -5.6V$$

This value will ~~be~~ fall in the range,

$-3\Delta$  to  $-2\Delta$  or  $-6V$  to  $-4V$  range

$$V_q = -2.5\Delta = -2.5 \times 2 = -5V$$

$$V(t) = 7.34$$

This value will ~~be~~ fall in the range,

$3\Delta$  to  $4\Delta$  or  $6V$  to  $8V$  range.

$$V_q = \frac{7}{2}\Delta = 3.5 \times 2 = 7V$$

$$4.c) \text{ Max error} = \frac{\Delta}{2} = \frac{2}{2} = 1V$$


$$4.d) \# \text{ bits} = 3$$





$$\text{resistor} = 2^3 = 8$$


$$\text{OP-AMP} = 2^3 - 1 = 7$$

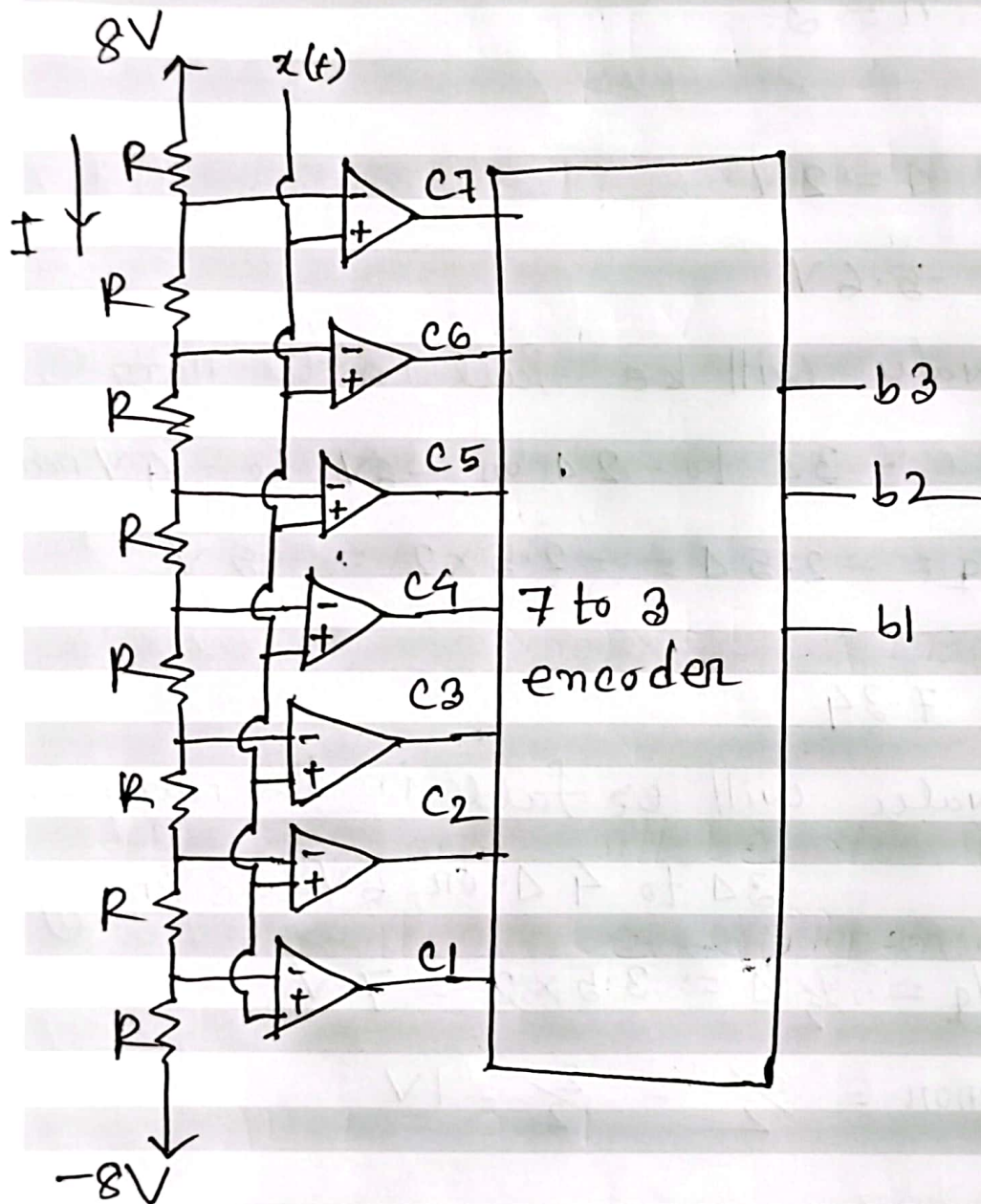

Given,  $I = 0.1 \text{ mA}$ , and,  $I = \frac{8 - (-8)}{8R} = \frac{2}{R}$   
 $\therefore \frac{2}{R} = 0.1 \text{ m} \Rightarrow R = 20 \text{ k}\Omega$



5. 4 bit binary weighted DAC,

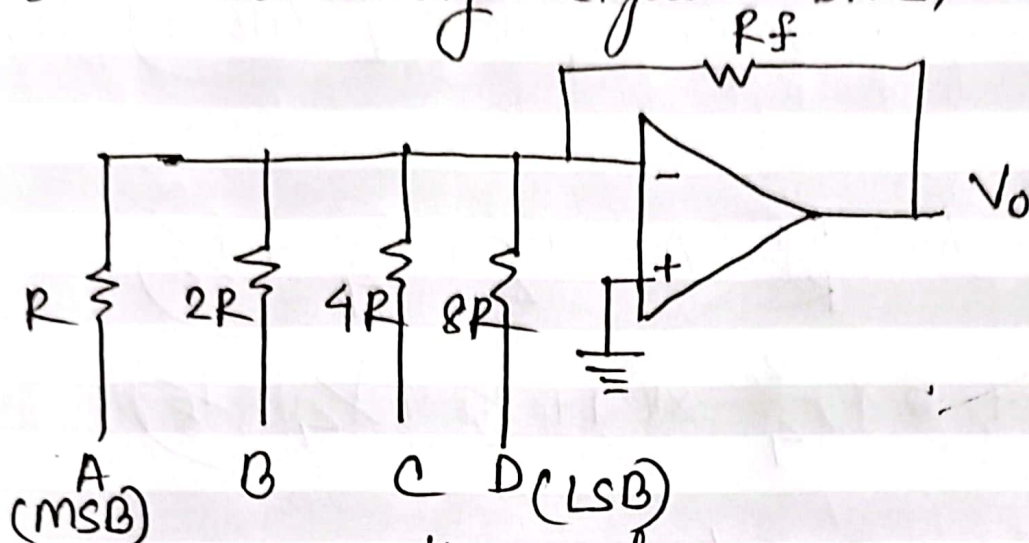

We can either choose  $R$  or  $R_f$ .

Let's choose,  $R = 1k\Omega$

$$V_o = - \frac{V_{ref} R_f}{R} \left( A + \frac{B}{2} + \frac{C}{4} + \frac{D}{8} \right)$$

$V_o$  will be maximum by value, when input bits 1111

$$V_o = - \frac{5 \times R_f}{R} \left( 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right)$$

Taking modulus value,

~~Neglecting (-) value~~, and assigning  $V_o = 1.5$

$$1.5 = \frac{5 \times R_f}{R} \left( \frac{15}{8} \right)$$

$$\frac{R}{R_f} = \frac{5}{8}$$

$$R_f = \frac{8}{5} \times 1k\Omega = 1.6k\Omega$$



6. a) For max output, Input seq (ABCD) = 1111

$$\begin{aligned}V_o &= -V_{ref} \frac{R_f}{R} \left( A + \frac{B}{2} + \frac{C}{4} + \frac{D}{8} \right) \\&= +5 \times \frac{2}{4} \times \left( 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) \\&= 4.6875 \text{ V}\end{aligned}$$

For min output, Input seq (ABCD) = 0000

$$\begin{aligned}V_o &= -V_{ref} \times \frac{R_f}{R} \left( A + \frac{B}{2} + \frac{C}{4} + \frac{D}{8} \right) \\&= 0 \text{ V}\end{aligned}$$

6. b) Step size will be  $V_o$  for 0001 seq.  
or it can be difference between  
two consecutive input sequence.

$$ABCD = 0001$$

$$\begin{aligned}\text{Step size} = V_o &= -V_{ref} \frac{R_f}{R} \left( A + \frac{B}{2} + \frac{C}{4} + \frac{D}{8} \right) \\&= 5 \times \frac{2}{4} \times \left( 0 + 0 + 0 + \frac{1}{8} \right) \\&= 0.3125 \text{ V}\end{aligned}$$



6.c) Resolution = Step size =  $0.3125\text{V}$

6.d)

Input				$V_0$
A	B	C	D	
0	0	0	0	0
0	0	0	1	$\Delta$
0	0	1	0	$2\Delta$
0	0	1	1	$3\Delta$
0	1	0	0	$4\Delta$
0	1	0	1	$5\Delta$
0	1	1	0	$6\Delta$
0	1	1	1	$7\Delta$
1	0	0	0	$8\Delta$
1	0	0	1	$9\Delta$
1	0	1	0	$10\Delta$
1	0	1	1	$11\Delta$
1	1	0	0	$12\Delta$
1	1	0	1	$13\Delta$
1	1	1	0	$14\Delta$
1	1	1	1	$15\Delta$

where,  $\Delta = 0.3125\text{V}$

6.e) From the above table,

$$1101 \longrightarrow V_0 = 13\Delta = 13 \times 0.3125\text{V}$$

Rest are similar/ use formula



7. a)

$$V_o = -V_{ref} \times R_f \left( \frac{A}{R_A} + \frac{B}{R_B} + \frac{C}{R_C} + \frac{D}{R_D} \right)$$

For, ABCD = 1111

$$V_o = 2 \times 1k \left( \frac{1}{2k} + \frac{1}{4k} + \frac{1}{8k} + \frac{1}{16k} \right) \\ = 1.875V$$

7. b) Resolution will be the value for LSB,

$$V_o = 2 \times 1k \left( 0 + 0 + 0 + \frac{1}{16k} \right)$$

$$\text{Resolution} = \frac{1}{8} V \text{ (Ans.)}$$

7. c) For  $V_o \rightarrow \text{Max}$

ABCD = 1111

$$V_o = 7.5 = 2 \times R_f \left( \frac{1}{2k} + \frac{1}{4k} + \frac{1}{8k} + \frac{1}{16k} \right)$$

$$R_f = 4k\Omega$$



**ULKASEMI**

We are Integrating your Ideas

web: [www.ulkasemi.com](http://www.ulkasemi.com)  
e-mail: [info@ulkasemi.com](mailto:info@ulkasemi.com)