

BRAC UNIVERSITY

CSE 350

Quiz-1, Section 8

Fall 2024


Marks: 20

Name: _____

ID: _____


1. According to the circuit, answer the following questions. Here logic high and logic low level are indicated by accordingly 5 V and 0 V.

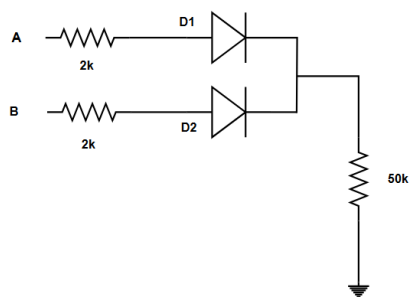- a. Identify the logic gate. [2]
- b. What will be the value of V_{OH} for this logic gate? [8]



2. According to the circuit, answer the following questions. Here logic high and logic low level are indicated by accordingly 5 V and 0 V.

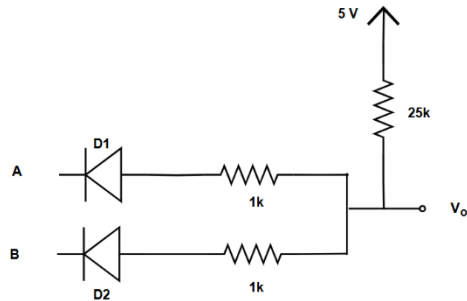- a. Find out the value of V_o for the input, $A = 0$ and $B = 1$. [6]
- b. Implement $Y = AB + C$ with Diode Logic. [4]




Quiz-1 Section 8

1. a) OR gate

1. b) We will find V_{OH} for 01 on 10 case.


Case (0, 1)

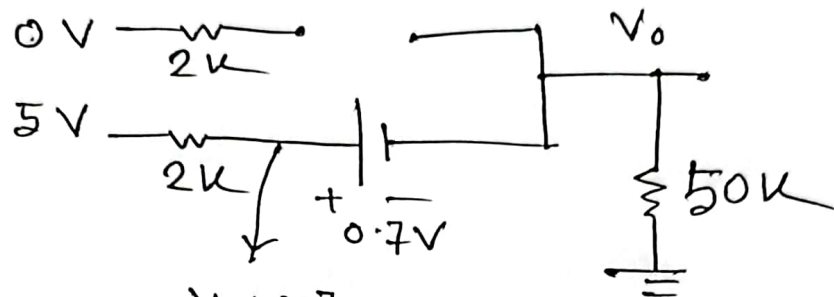

$$\frac{V_O - 0}{50k} + \frac{V_O + 0.7 - 5}{2k} = 0 \Rightarrow V_O = 4.135V$$

$$\therefore V_{OH} = 4.135V$$


2. a)

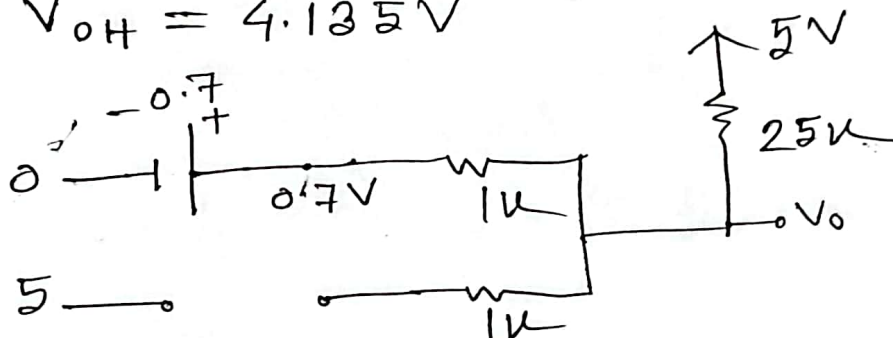

$$\frac{V_O - 5}{25k} + \frac{V_O - 0.7}{1k} = 0$$

$$V_O = 0.865V$$

2. b)

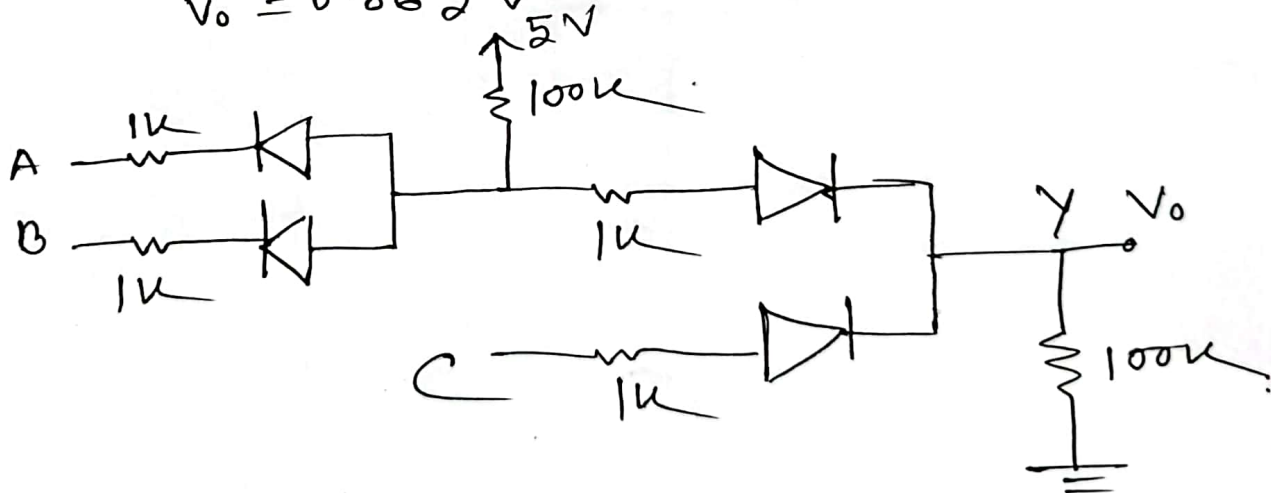

BRAC UNIVERSITY

CSE 350

Quiz-1, Section 13

Fall 2024


Marks: 20

Name: _____

ID: _____

1. According to the circuit, answer the following questions. Here logic high and logic low level are indicated by accordingly 5 V and 0 V.

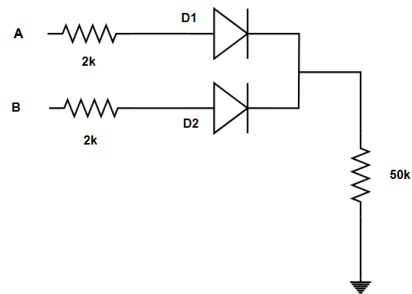
- a. Identify the logic gate. [2]
- b. What will be maximum power and minimum power for this logic circuit? [8]



2. According to the circuit, answer the following questions. Here logic high and logic low level are indicated by accordingly 5 V and 0 V.

a. Find out the value of V_o for the input, $A = 0$ and $B = 1$. [6]

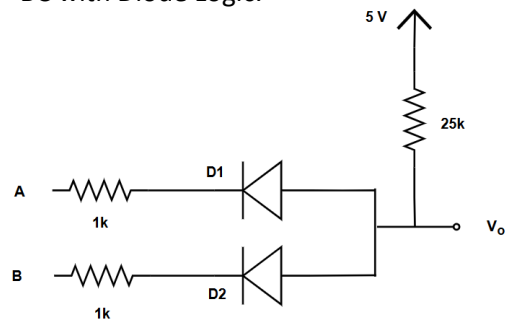
b. Implement $Y = A + BC$ with Diode Logic. [4]



Quiz-12 Section-13

1. a) OR Gate


1. b) Maximum power (1,1)

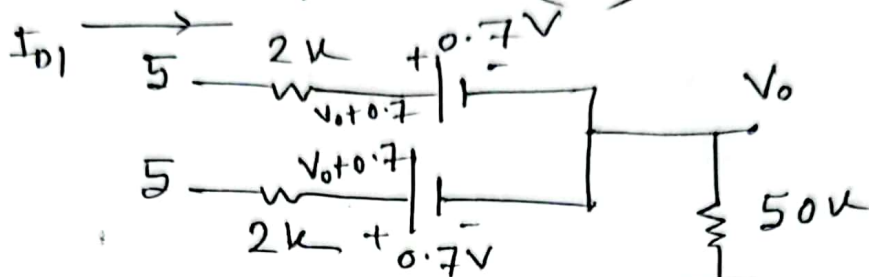

$$\frac{V_o - 0}{50k} + \frac{V_o + 0.7 - 5}{2k} + \frac{V_o + 0.7 - 5}{2k} = 0$$


$$\Rightarrow V_o = 4.216V$$
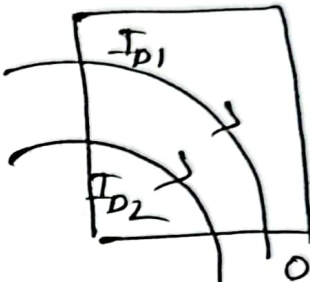
$$I_{D1} = I_{D2} = \frac{1}{2} \times \left(\frac{V_o}{50k} \right) \text{ or } \frac{5 - (V_o + 0.7)}{2k} = 0.04216 \text{ mA}$$




$$P_{\max} = (5 - 0) \times 0.04216 + (5 - 0) \times 0.04216 = 0.4216 \text{ mW}$$


Minimum power

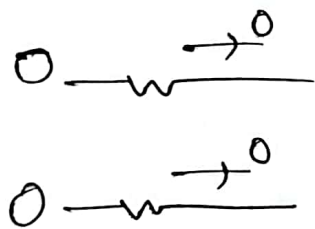

$$P_{\min} = 0$$

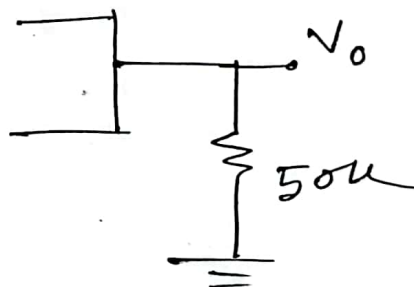


2. a)

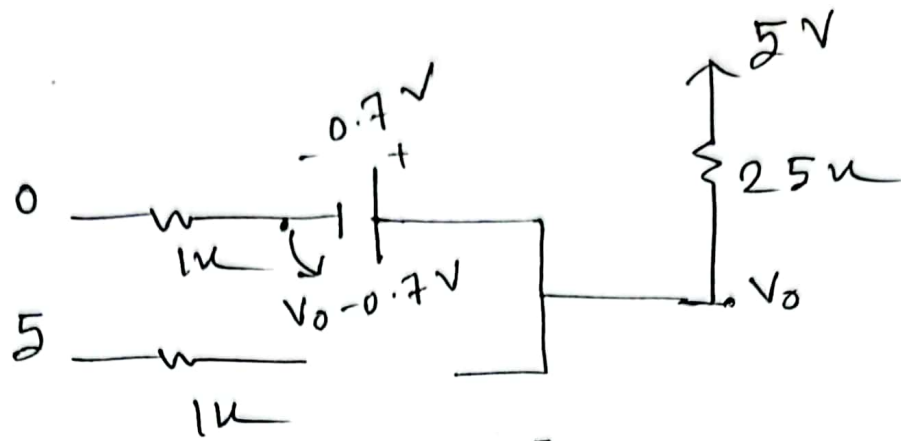

$$\frac{V_o - 5}{25\mu} + \frac{V_o - 0.7 - 0}{1\mu} = 0$$

$$V_o = 0.865V$$

2. b)

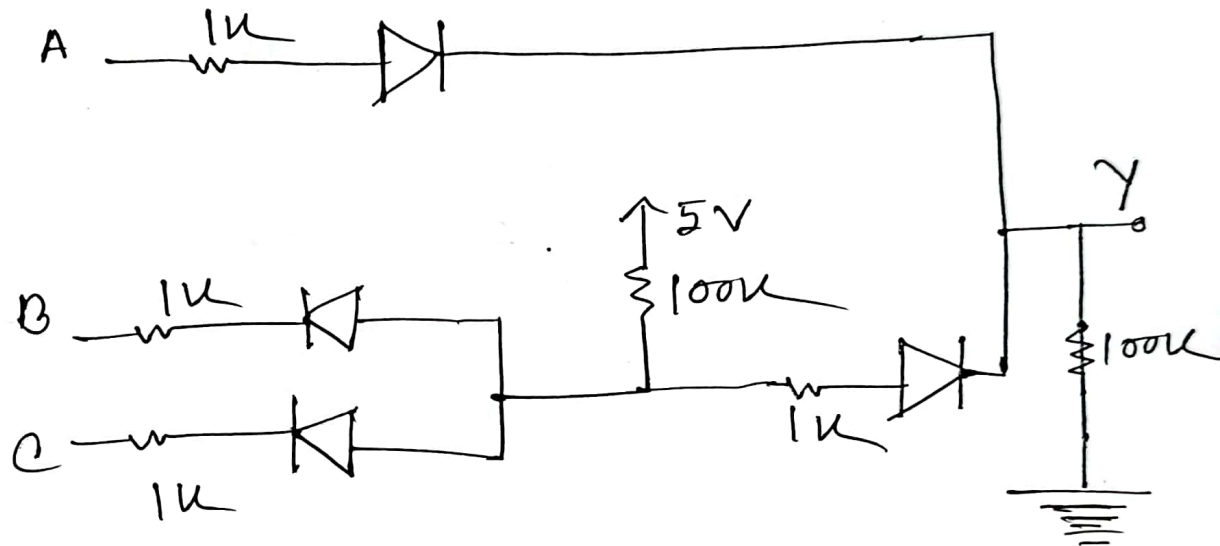

BRAC UNIVERSITY

CSE 350

Quiz-2, Section 8

Fall 2024

Marks: 20


Name: _____

ID: _____

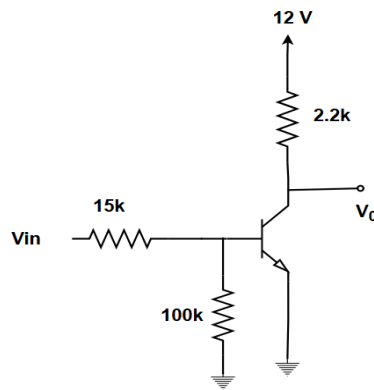1. Answer the following questions considering the given circuit.

[Logic High = 12 V, Logic Low = 0.2 V, $V_{CE}(SAT) = 0.2\text{ V}$ and $V_{BE}(SAT) = 0.8\text{ V}$, $\beta_F = 50$]


- What will be the maximum allowable fanout for this RTL inverter? [5]
- Find the value of I_E of the transistor when the input of the circuit is high. [5]



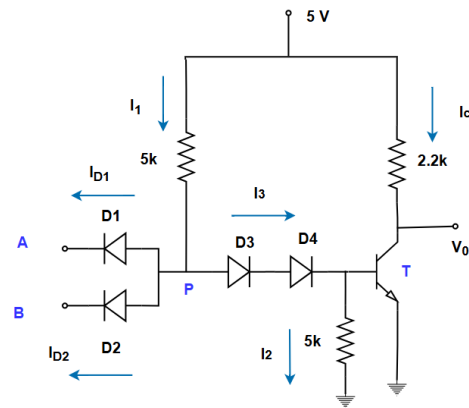2. Answer the following questions from the given circuit.


[Logic high = 5 V, Logic low = 0.2 V, $V_{CE}(SAT) = 0.2$ V and $V_{BE}(SAT) = 0.8$ V, $\beta_F = 30$]

- Make a truth table for the given logic circuit. [2]
- Find the value of base current of the transistor when both inputs are high. [8]



Quiz-2 Section-8

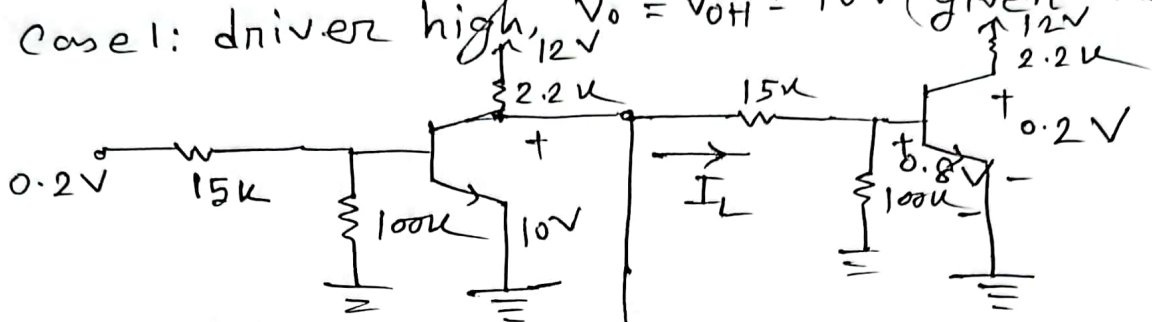1.a) case 1: driver high, $V_0 = V_{OH} = 10V$ (given in Question)




$$I_{\text{supply}} = \frac{12 - 10}{2.2k} = 0.909 \text{ mA}$$

$$I_L = \frac{10 - 0.8}{15k} = 0.613 \text{ mA}$$

$$N = \frac{0.909}{0.613} = \lfloor 1.48 \rfloor = 1$$

$$FO = 1$$

case 2: driver low, $V_0 = 0.2$

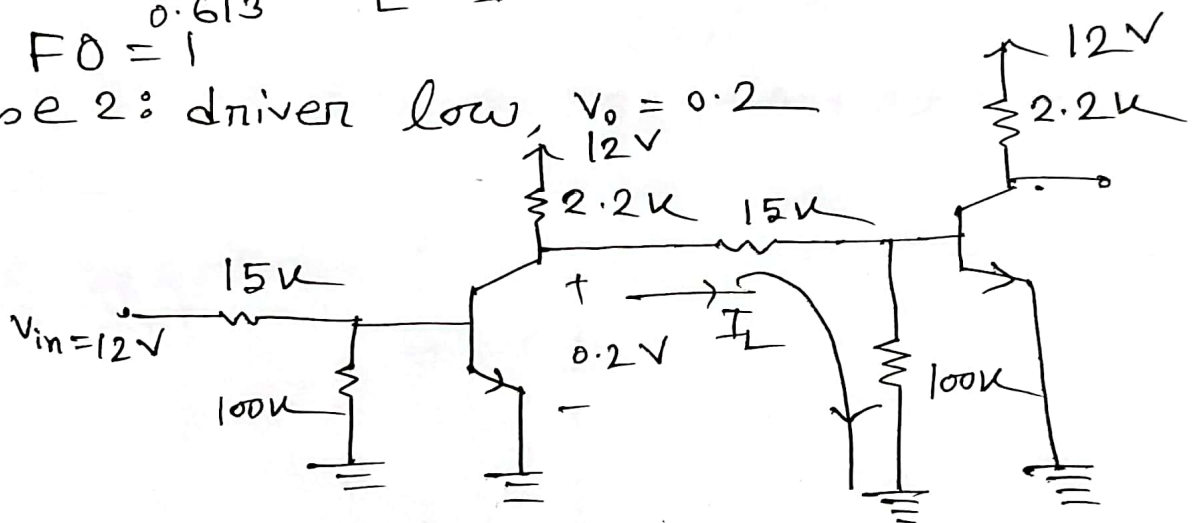


$$I_{\text{supply}} = \frac{12 - 0.2}{2.2k} = 5.364 \text{ mA}$$

$$I_L = \frac{0.2 - 0}{115k} = 1.74 \times 10^{-3} \text{ mA}$$

$$FO = \frac{5.364}{1.74 \times 10^{-3}} = 3084$$

$$FO = \text{Min}(3084, 1) = 1$$

1.b)

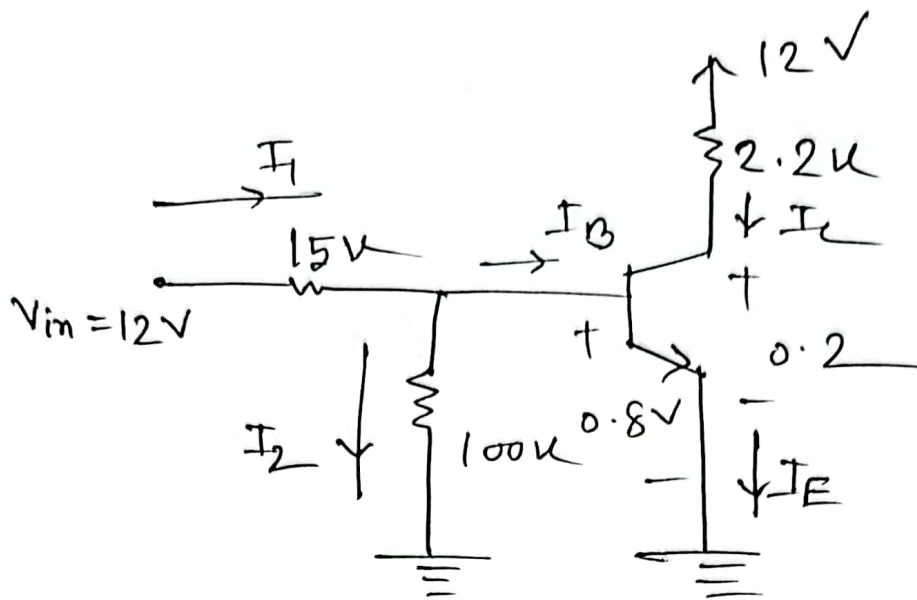

$$I_1 = \frac{12 - 0.8}{15k}, \quad I_2 = \frac{0.8 - 0}{100k}$$

$$I_B = I_1 - I_2 = \frac{12 - 0.8}{15k} - \frac{0.8}{100k} = 0.739 \text{ mA}$$


$$I_C = \frac{12 - 0.2}{2.2k} = 5.364 \text{ mA}$$

$$I_E = I_C + I_B = 5.364 + 0.739 = 6.103 \text{ mA}$$

2.a) NAND gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

2.b)

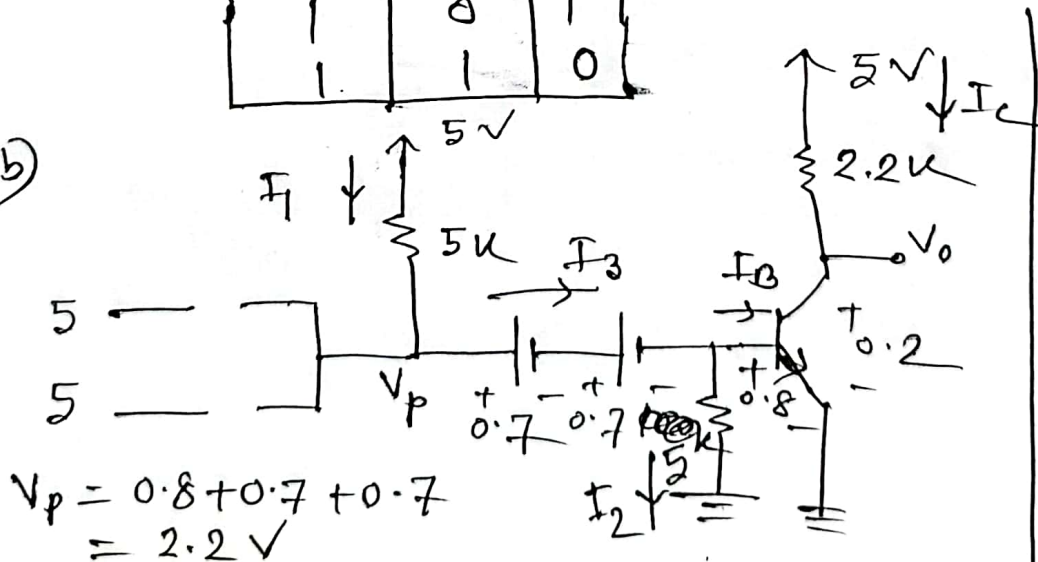

$$V_p = 0.8 + 0.7 + 0.7 = 2.2 \text{ V}$$

$$I_3 = I_1 = \frac{5 - 2.2}{5k} = 0.56 \text{ mA}$$

$$I_2 = \frac{0.8 - 0}{5k} = 0.16 \text{ mA}$$

$$I_0 = I_3 - I_2 = 0.4 \text{ mA}$$

BRAC UNIVERSITY

CSE 350

Quiz-2, Section 13

Fall 2024

Marks: 20


Name: _____

ID: _____

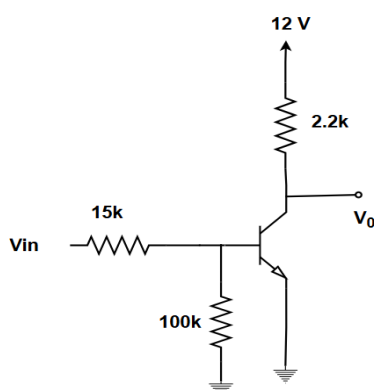1. Answer the following questions considering the given circuit.

[Logic High = 12 V, Logic Low = 0.2 V, $V_{CE}(SAT) = 0.2\text{ V}$ and $V_{BE}(SAT) = 0.8\text{ V}$]


- Make a truth table of the logic circuit. [2]
- Find the average power for the given logic circuit. [8]



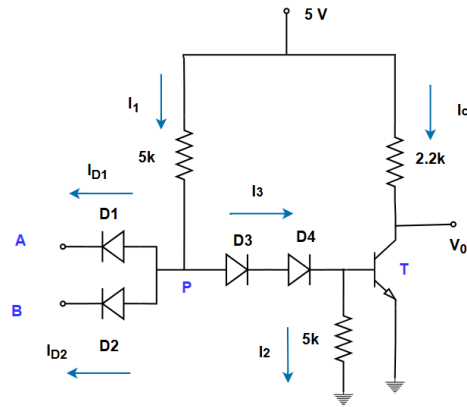2. Answer the following questions from the given circuit.

[Logic high = 5 V, Logic low = 0.2 V, $V_{CE}(SAT) = 0.2$ V and $V_{BE}(SAT) = 0.8$ V, $\beta_F = 30$]

- Find the V_o for the case when both inputs are high. [4]
- For which input combination the BJT will be in Saturation mode? Find the value of β_{forced} for this BJT in that particular case. [2+4]



Quiz-2 Section-13

1. a) This is a RTL inverter

A	Y
0	1
1	0

1. b) Case 1.

$$V_{in} = 0.2V$$

$$I_1 = \frac{0.2 - 0}{115k}$$

$$= \frac{1}{575} mA$$

$$P_1 = (0.2 - 0) \times \frac{1}{575} = 3.47 \times 10^{-4} mW$$




Case 2: $V_{in} = 12V$

$$I_1 = \frac{12 - 0.8}{15k}$$

$$= 0.747 mA$$

$$I_c = \frac{12 - 0.2}{2.2k}$$

$$= 5.364 mA$$

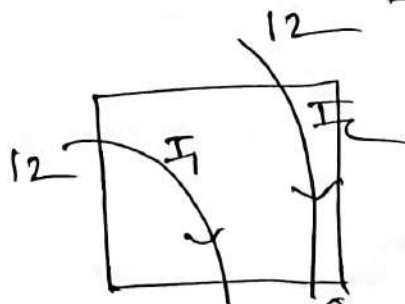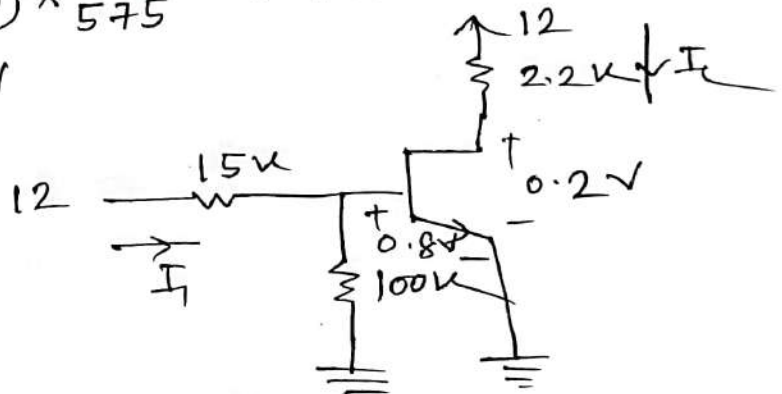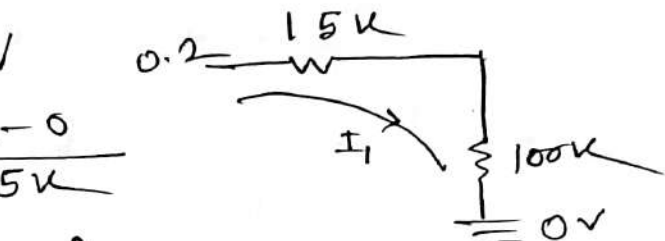


$$P_2 = (12 - 0) \times 0.747 mW + (12 - 0) \times 5.364 mW$$

$$= 73.33 mW$$

$$P_{av} = \frac{P_1 + P_2}{2} = 36.67 mW$$

2.a) $V_A = V_B = 5V$

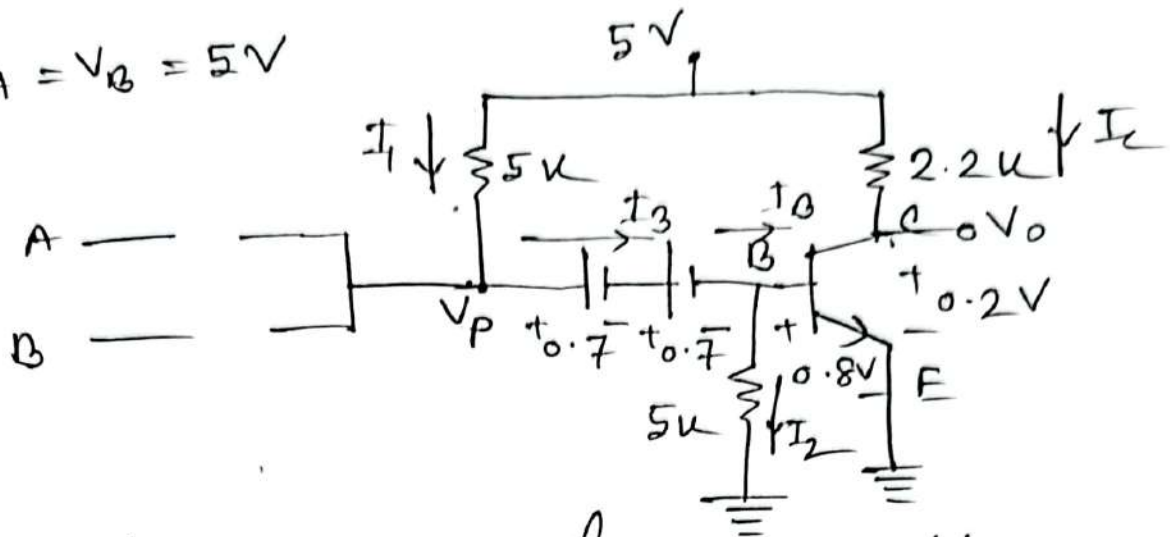

D1 and D2 are in ~~cut~~ reverse bias

$$V_P = 0.7 + 0.7 + 0.8 = 2.2V$$

$$V_{CE} = V_C - V_E = 0.2$$

$$\Rightarrow V_0 - 0 = 0.2 \quad \left[\begin{array}{l} V_E = 0V, \\ V_C = V_0 \end{array} \right]$$

$$\therefore V_0 = 0.2V$$

2.b) For both inputs logic high value,
BJT will be in saturation mode.

$$I_1 = I_3 = \frac{5 - 2.2}{5k}$$

$$I_2 = \frac{0.8}{5k}$$

$$I_B = I_1 - I_2 = 0.4mA$$

$$I_C = \frac{5 - 0.2}{2.2k} = 2.18mA$$

$$\beta_{Forward} = \frac{I_C}{I_B} = \frac{2.18mA}{0.4mA} = 5.45 < 30$$