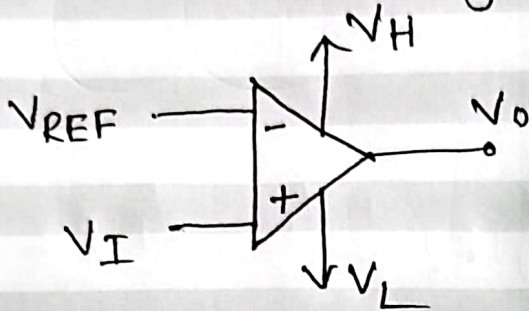


Comparators:

(a) Non inverting



Here, $V_+ = V_I$, $V_- = V_{REF}$

For $V_O = V_H$,

$$V_+ > V_-$$


$$\Rightarrow V_I > V_{REF}$$

For $V_O = V_L$,

$$V_+ < V_-$$

$$\Rightarrow V_I < V_{REF}$$

V_O vs V_I plot,

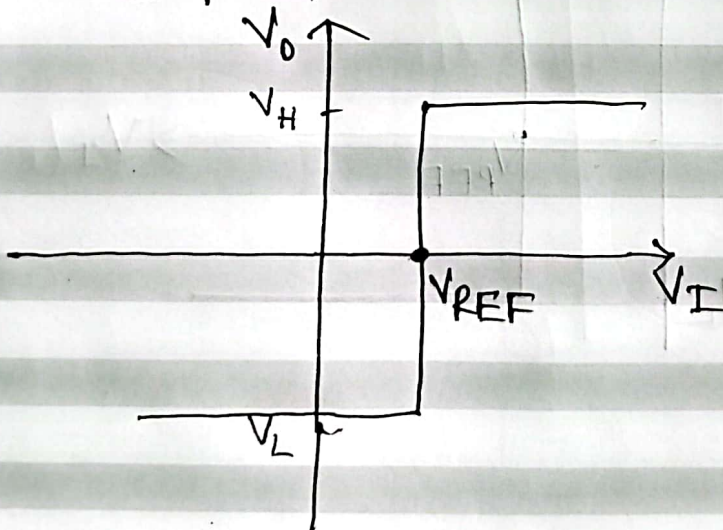


ULKASEMI

We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

(b) Inverting

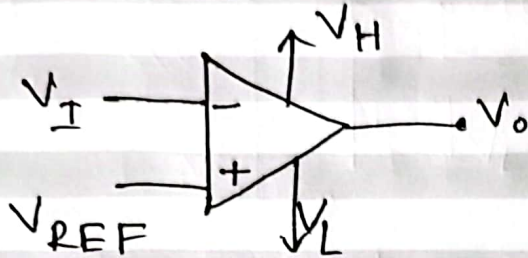

Here, $V_+ = V_{REF}$, $V_- = V_I$

For $V_O = V_H$

$$V_+ > V_-$$

$$\Rightarrow V_{REF} > V_I$$


$$\Rightarrow V_I < V_{REF}$$

For, $V_O = V_L$


$$V_+ < V_-$$

$$\Rightarrow V_{REF} < V_I$$

$$\Rightarrow V_I > V_{REF}$$

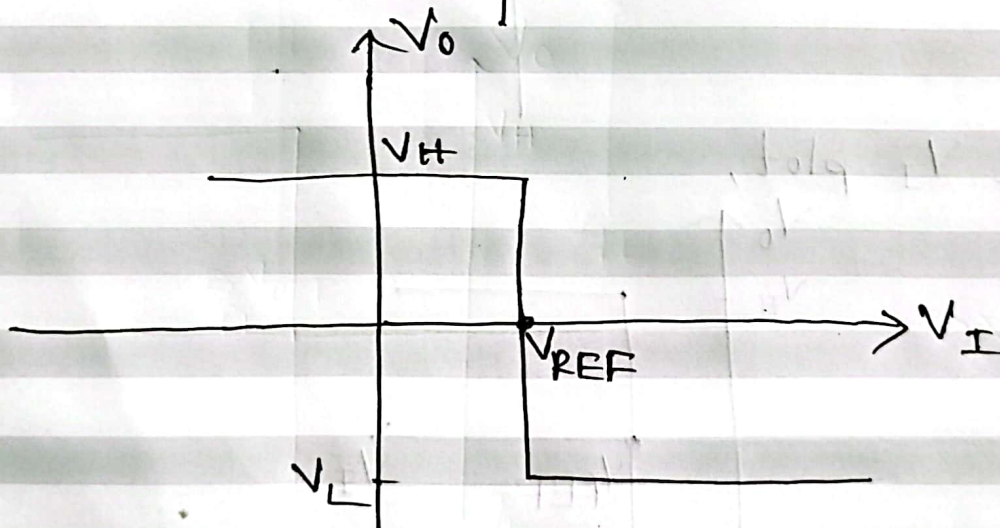

© Non inverting (voltage division)

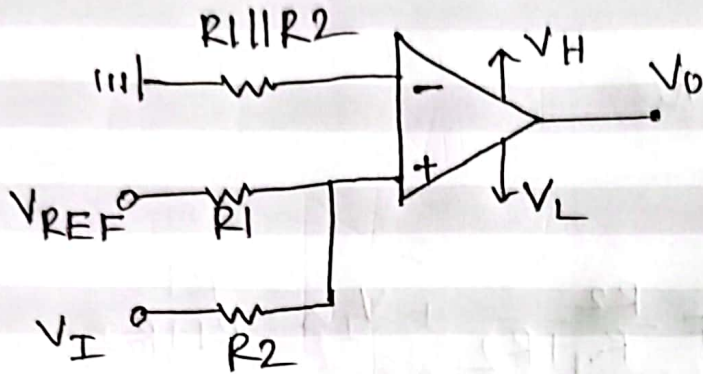

Here, $V_- = 0$

$$V_+ = V_{REF} \frac{R_2}{R_1 + R_2} + V_I \times \frac{R_1}{R_1 + R_2}$$


For, $V_o = V_H$

$$V_+ > V_-$$

$$\Rightarrow V_{REF} \frac{R_2}{R_1 + R_2} + V_I \times \frac{R_1}{R_1 + R_2} > 0$$

$$V_I > -\frac{R_2}{R_1} V_{REF}$$

$$V_I < -\frac{R_2}{R_1} V_{REF}$$

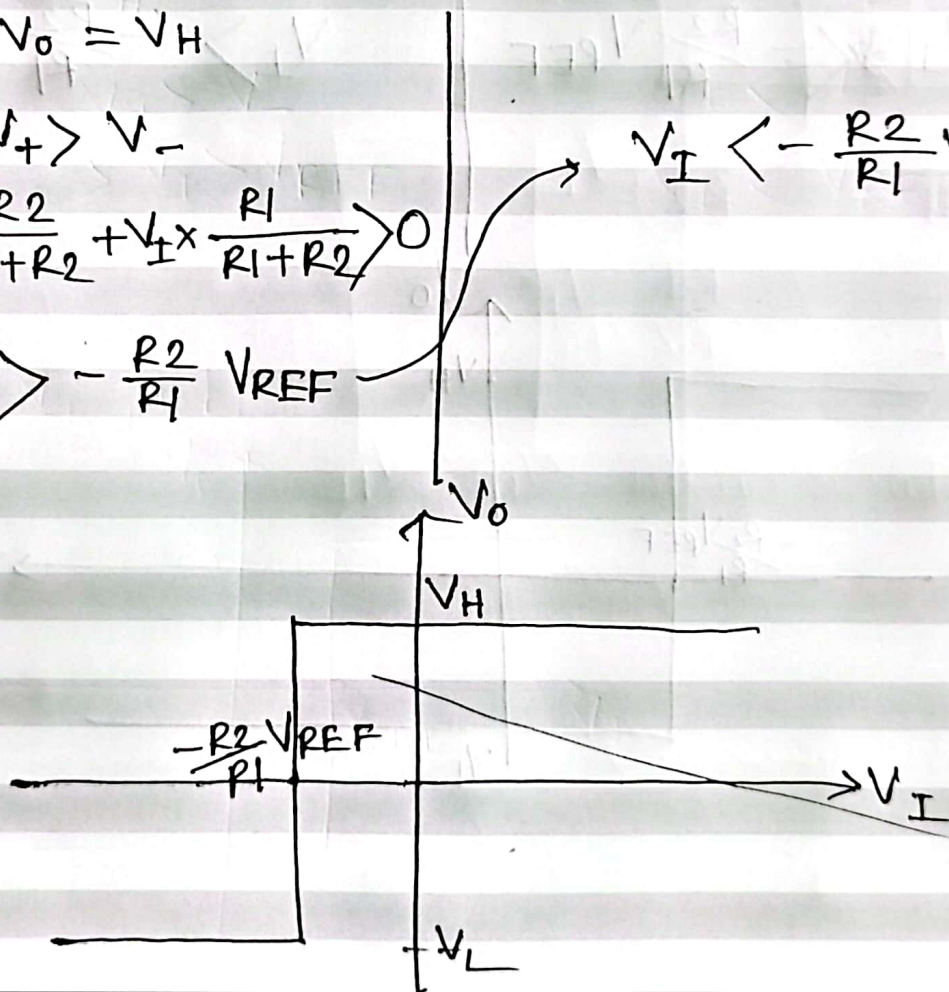


ULKASEMI

We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

(d) Inverting (voltage divider)

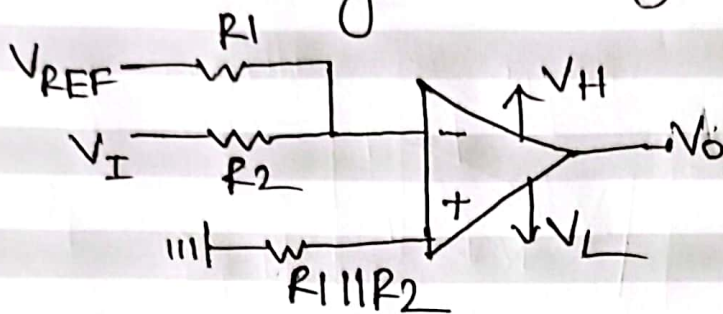

Here, $V_+ = 0$, $V_- = V_{REF} \frac{R_2}{R_1 + R_2} + V_I \times \frac{R_1}{R_1 + R_2}$

For, $V_O = V_H$


$V_+ > V_-$

$V_I < -\frac{R_2}{R_1} V_{REF}$

For $V_O = V_L$


$V_+ < V_-$

$V_I > -\frac{R_2}{R_1} V_{REF}$

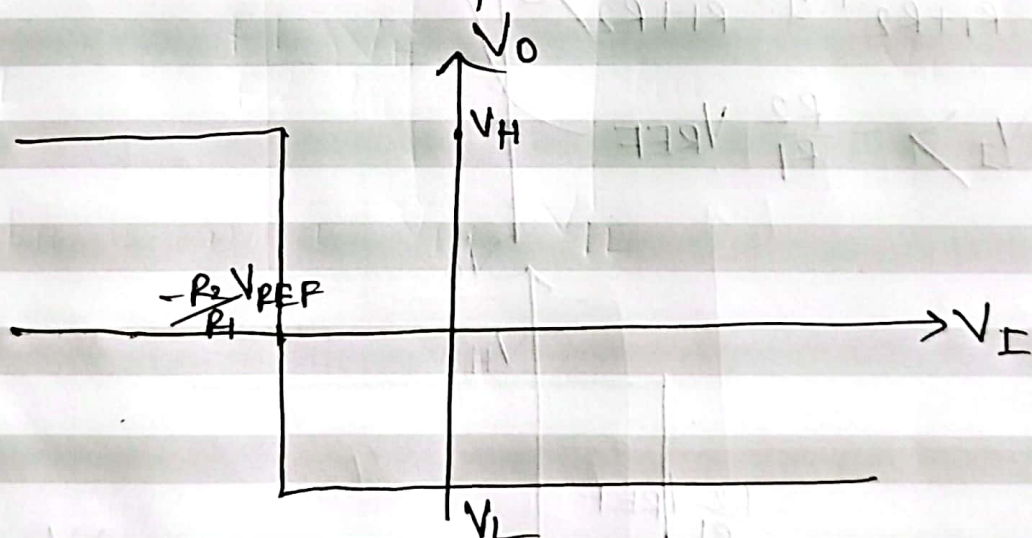

Schmitt Trigger

⊗ Inverting ST

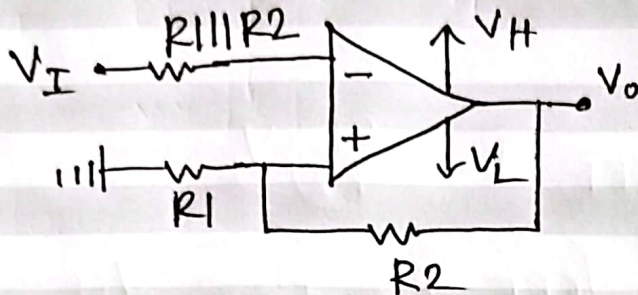

Here, $V_- = V_I$, $V_+ = V_O \frac{R_1}{R_1 + R_2}$.

Case 1: V_I large positive

$$V_O = V_L \text{ as } V_- > V_+$$

Now, $V_- = V_I$

$$V_+ = V_L \frac{R_1}{R_1 + R_2}$$

For sustaining, $V_O = V_L$,

$$\begin{aligned} V_- &> V_+ \\ V_I &> V_L \frac{R_1}{R_1 + R_2} \end{aligned}$$

$$\therefore V_{TL} = V_L \frac{R_1}{R_1 + R_2}$$

Case 2: V_I large Negative

$$V_O = V_H \text{ as } V_+ > V_-$$

$$V_- = V_I, V_+ = V_H \frac{R_1}{R_1 + R_2}$$


For sustaining, $V_O = V_H$

$$V_+ > V_-$$

$$V_I < V_H \frac{R_1}{R_1 + R_2}$$

$$V_{TH} = V_H \frac{R_1}{R_1 + R_2}$$


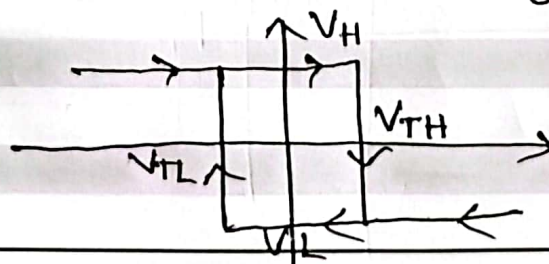
$$\text{Hysteresis width} = V_{TH} - V_{TL}$$



ULKASEMI
We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

(b) Noninverting ST

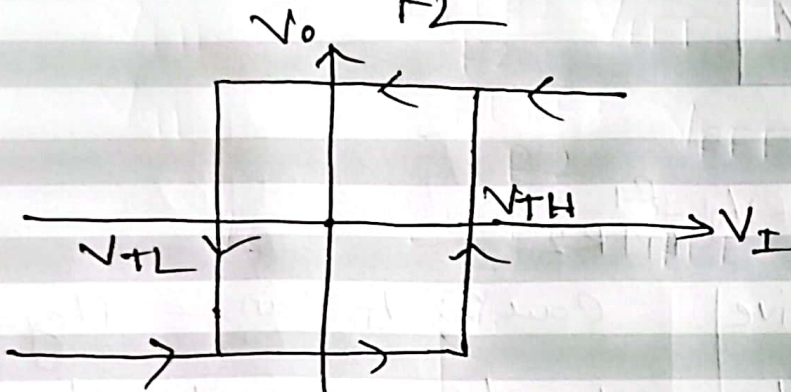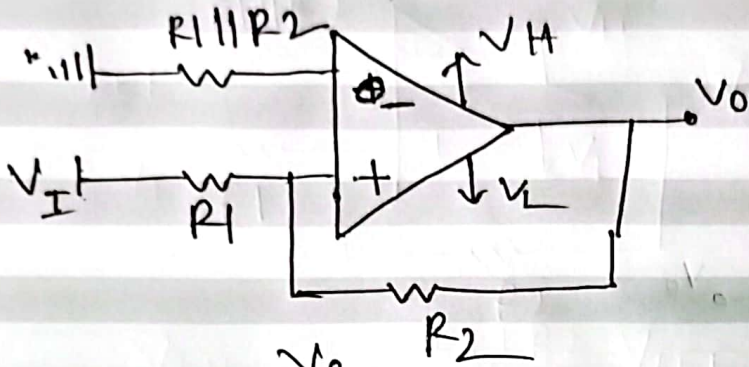


$$V_{TH} = \left(-\frac{R_1}{R_2} \right) V_L$$

$$V_{TL} = \left(-\frac{R_1}{R_2} \right) V_H$$

$$\text{Hysteresis width} = V_{TH} - V_{TL}$$




(c) Inverting ST with V_{REF}

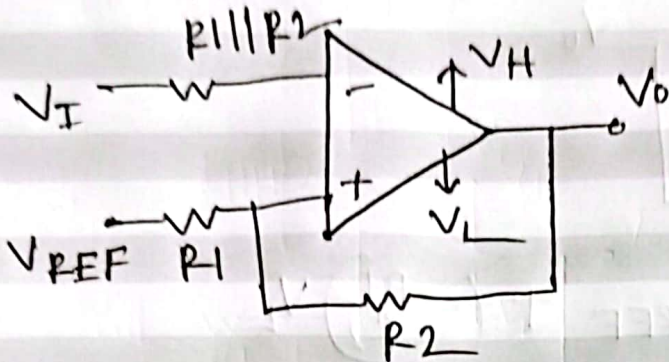


$$V_{TH} = V_{REF} \frac{R_2}{R_1 + R_2} + V_H \frac{R_1}{R_1 + R_2}$$

$$V_{TL} = V_{REF} \frac{R_2}{R_1 + R_2} + V_L \frac{R_1}{R_1 + R_2}$$
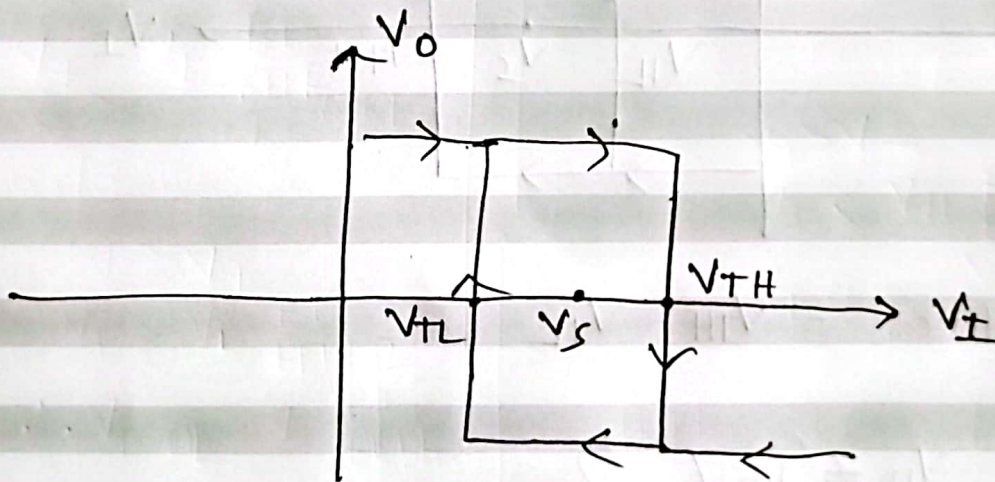
$$V_S = \frac{V_{TH} + V_{TL}}{2} = V_{REF} \frac{R_2}{R_1 + R_2}$$




(d) Non Inverting ST with V_{REF}

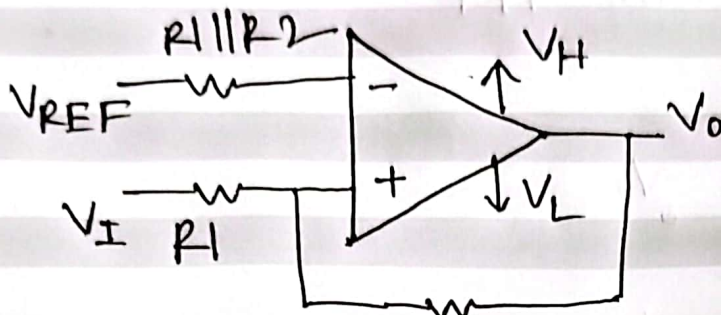

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{REF} + \left(-\frac{R_1}{R_2} \right) V_L$$

$$V_{TL} = \frac{R_1 + R_2}{R_2} V_{REF} + \left(-\frac{R_1}{R_2} \right) V_H$$

$$V_S = \frac{R_1 + R_2}{R_2} V_{REF}$$

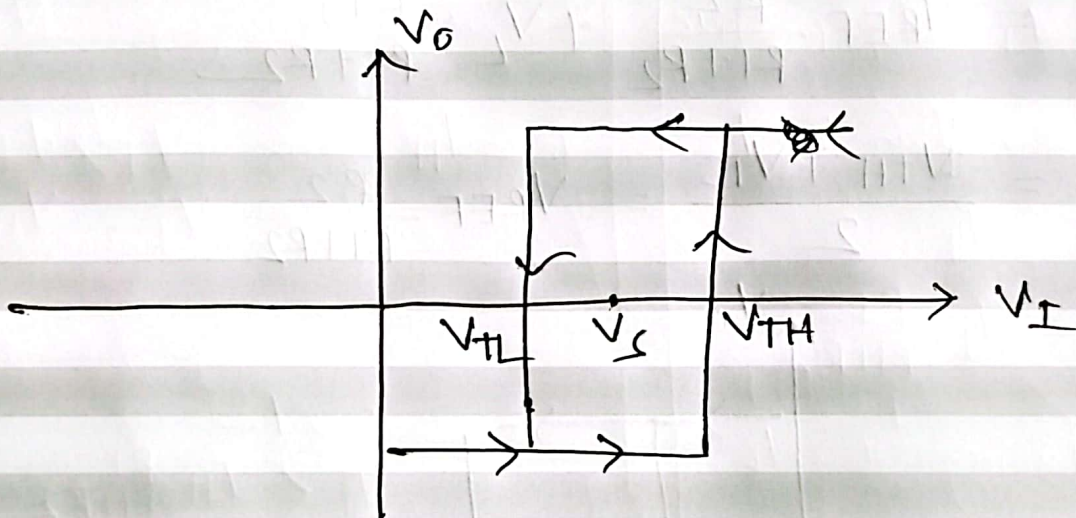

$$V_{Hysteresis} = V_{TH} - V_{TL}$$

Note: $V_H = 15V$

$V_L = -15V$

can be assumed, if data are missing