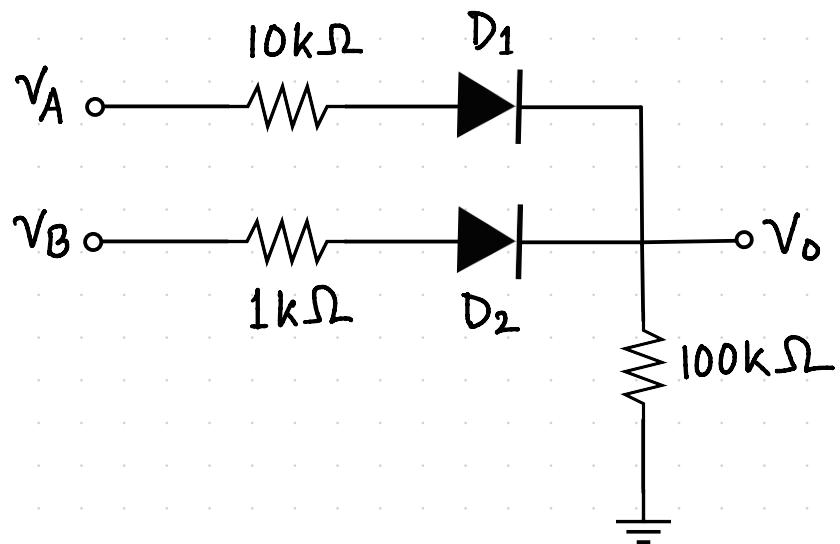


Week 1

Diode Logic


Question 1



Solve the circuit to find the output voltage for each of the input combinations.

Calculate the average power dissipation.

Solution:

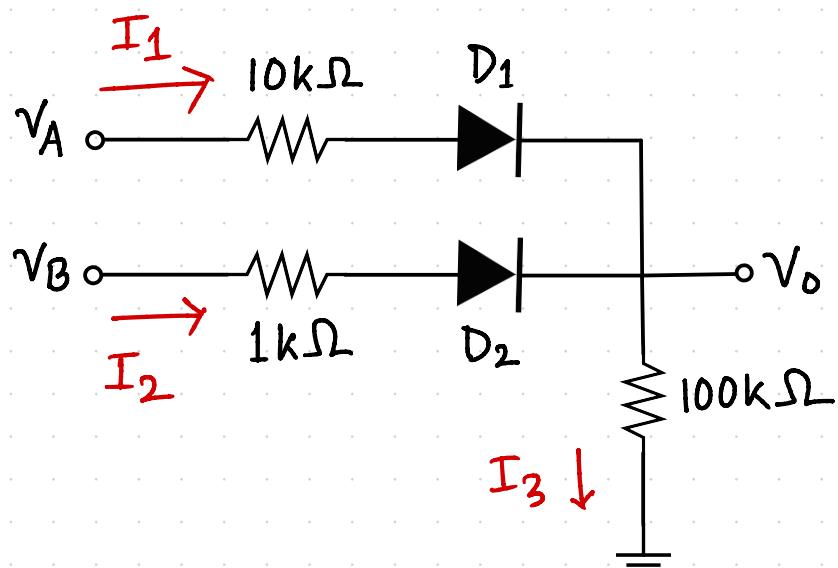

Case 1 :

$$A = B = 0V$$

Both diodes D_1 and D_2 are OFF

$$V_o = 0V$$

Case 2 : $A = 5V, B = 0V$

Diode D_1 will be ON, D_2 will be OFF

Nodal Analysis \Rightarrow

$$I_1 + I_2 = I_3$$

$$\Rightarrow \frac{5 - (V_o + 0.7)}{10k} + 0 = \frac{V_o - 0}{100k}$$

$$\Rightarrow V_o = 3.91V$$

Case 3: $A = 0 \text{ V}$, $B = 5 \text{ V}$

Diode D_1 will be OFF, D_2 will be ON

Nodal Analysis \Rightarrow)

$$I_1 + I_2 = I_3$$

$$\Rightarrow 0 + \frac{5 - (V_o + 0.7)}{1k} = \frac{V_o - 0}{100k}$$

$$\Rightarrow V_o = 4.25 \text{ V}$$

Case 4: $A = 5 \text{ V}$, $B = 5 \text{ V}$

Both diode D_1 and D_2 will be OFF

Nodal Analysis \Rightarrow)

$$I_1 + I_2 = I_3$$

$$\Rightarrow \frac{5 - (V_o + 0.7)}{10k} + \frac{5 - (V_o + 0.7)}{1k} = \frac{V_o - 0}{100k}$$

$$\Rightarrow V_o = 4.26 \text{ V}$$


Power Dissipation

Case 1 :

$$P = \sum \Delta V I$$

$$= (0-0) \times 0$$

$$= 0 \text{ W}$$

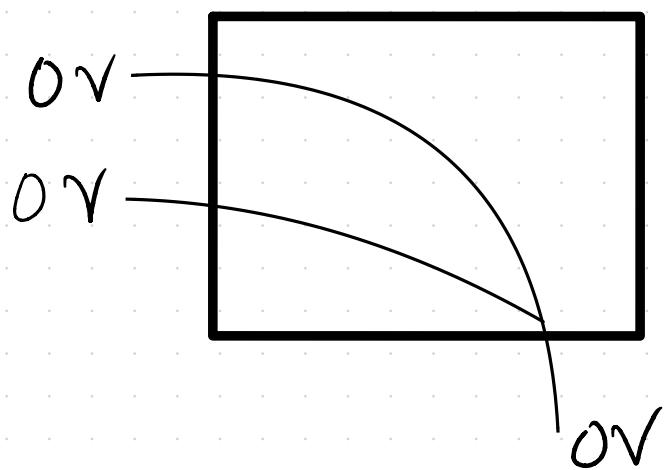


Case 2 :

$$P = \sum \Delta V I$$

$$= (5-0) \times \frac{3.91}{100k}$$

$$= 0.195 \text{ mW}$$

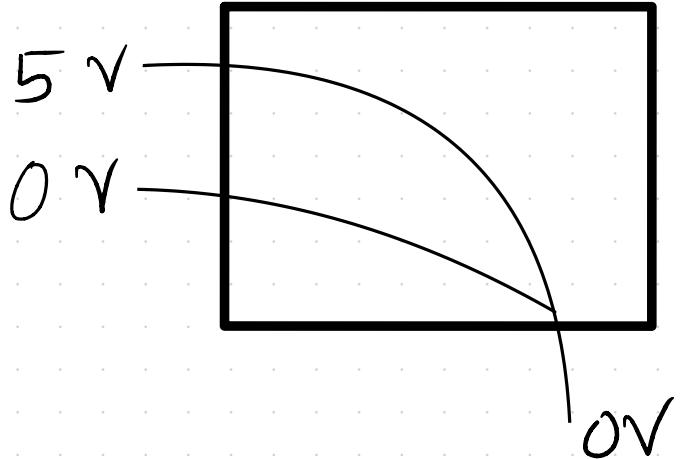


Case 3 :

$$P = \sum \Delta V I$$


$$= (5-0) \times \frac{4.25}{100k}$$

$$= 0.2125 \text{ mW}$$

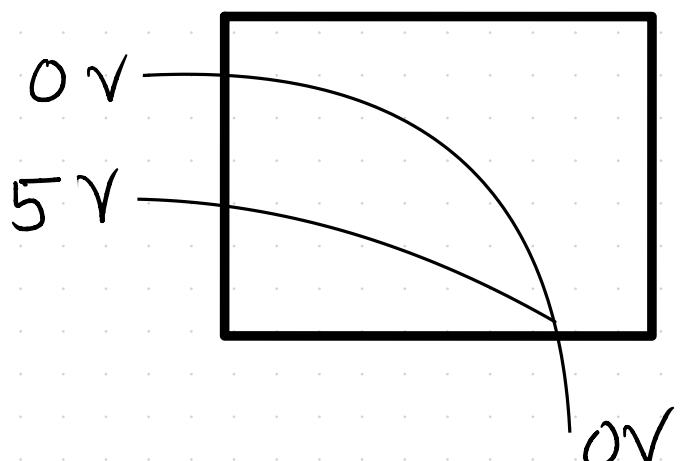

Case 4 :
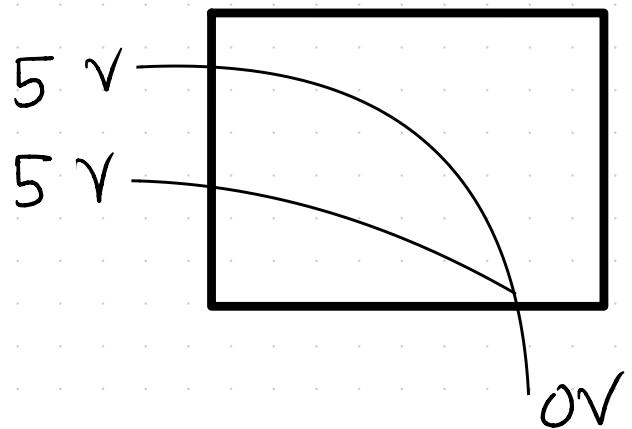
$$\begin{aligned}
 P &= \sum \Delta V I \\
 &= (5-0) \times \frac{4.26}{100k} \\
 &= 0.213 \text{ mW}
 \end{aligned}$$



Alternate approach


$$\begin{aligned}
 P &= \sum \Delta V I \\
 &= (5-0) \times \frac{5-(4.26+0.7)}{10k} + (5-0) \times \frac{5-(4.26+0.7)}{1k} \\
 &= 0.213 \text{ mW}
 \end{aligned}$$

i.e. Average power dissipation

$$= \frac{0+0.195+0.2125+0.213}{4}$$

$$= 0.155 \text{ mW}$$


Question 2

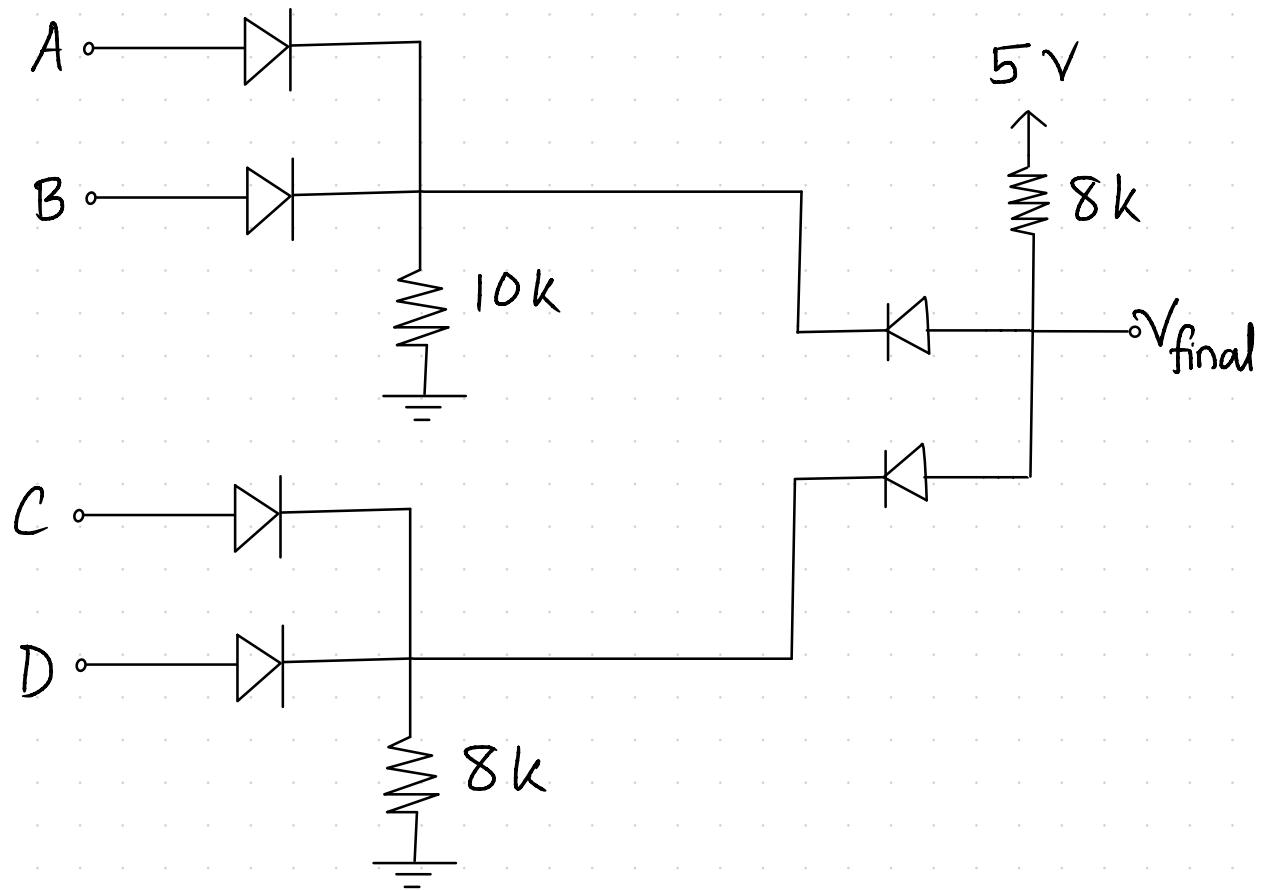

Determine the boolean expression of V_{final} in terms of input A, B, C, D

Solution: $V_{final} = (A+B).(C+D)$

Question 3

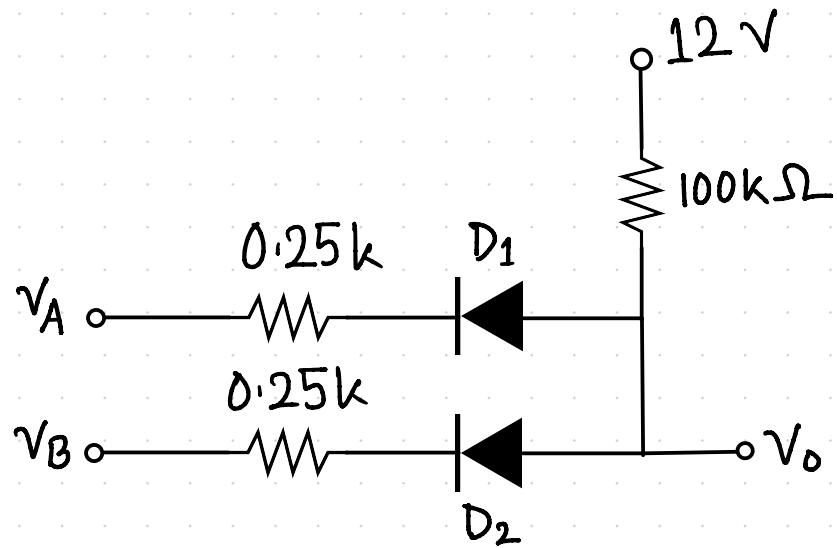

Find out the output voltage levels for all input combinations.

Calculate the maximum power dissipation.

Solution:

Case 1: For $V_A = 0 \text{ V}$, $V_B = 0 \text{ V}$


Both diodes D_1 and D_2 will conduct.

$$\therefore I_3 = I_1 + I_2$$

$$\Rightarrow \frac{12 - V_0}{100k} = \frac{(V_0 - 0.7) - 0}{0.25k} \times 2$$

$$\Rightarrow V_0 = 0.714 \text{ V}$$

Case 2 and 3
are identical

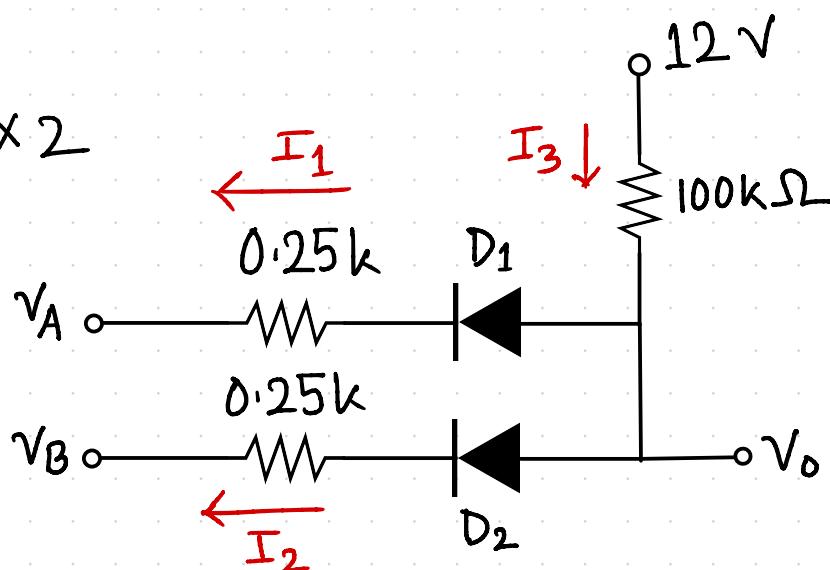

When any one input V_A or V_B is 0 V ,

Any one diode will conduct.

$$\therefore I_3 = I_1 + I_2$$

$$\Rightarrow \frac{12 - V_0}{100k} = \frac{(V_0 - 0.7) - 0}{0.25k}$$

$$\Rightarrow V_0 = 0.728 \text{ V}$$

Case 4: For $V_A = 12 \text{ V}$ and $V_B = 12 \text{ V}$

Both diodes will be OFF.

$$\therefore I_3 = 0, I_2 = 0, I_1 = 0$$

$$\therefore V_o = 12 \text{ V}$$

Maximum power dissipation happens when current is maximum i.e. case 1

$$P = \Delta V I$$

$$= (12 - 0) \times \frac{12 - 0.714}{100k}$$

$$= 1.354 \text{ mW}$$

