 


BRAC UNIVERSITY
Department of Computer Science & Engineering
Practice Problem sheet - ADC DAC
CSE 350: Digital Electronics and Pulse Technique

Question 1 - Flash ADC

Design a 3 bit flash ADC with a reference voltage of $V_{REF}=10V$. The quantized levels for this ADC should be **uniform (Equal step size)**.


(a)	Calculate total number of resistors and comparators required to fabricate a 3-bit flash A/D converter.
(b)	Calculate the 1LSB value or each step size (quantization range) for this 3 bit ADC. What would be the resolution for this ADC?
(c)	Calculate each quantization level and plot the Vin vs Dout graph.
(d)	If the input voltage Vin= 7 V , i) Comment on the quantization range in which the input lies. ii) Find the digital output for the given input.
(e)	If the 3-bit output is 110 What is the maximum and minimum value of v_A that produces this output?(Hint:find the quantization range).
(f)	If 1 bit was increased from this 3 bit Flash ADC, how many resistors and comparators are required? comment on the hardware changes for this 1 bit of increment.



a) $N = 3$; Resistor required $= 2^N = 2^3 = 8$
 Comparator required $= 2^3 - 1 = 7$

Solution:

 b) 1 LSB = resolution or step size = $\frac{V_{max} - V_{min}}{2^N} = \frac{10 - 0}{2^3} = 1.25V$




$$I = \frac{10V}{\frac{3R}{2} + 6R + \frac{R}{2}} = \frac{10V}{R \left(\frac{3}{2} + \frac{12}{2} + \frac{1}{2} \right)} = \frac{10V}{R \cdot \frac{16}{2}}$$

(same as previous example)

$$\therefore I = \frac{10}{8R} = \frac{1.25}{R}$$

$V_0 = 0V$
 $V_1 = \frac{1.25}{R} \cdot \frac{R}{2} = 0.625V \left(\frac{1}{2} \text{ LSB} \right)$
 $V_2 = \frac{1.25}{R} \cdot \left(R + \frac{R}{2} \right) = \frac{1.25}{R} \times \frac{3R}{2} = 1.875V \left(1\frac{1}{2} \text{ LSB} \right)$
 $V_3 = \frac{1.25}{R} \cdot \left(\frac{5R}{2} \right) = 3.125V$
 $V_4 = \frac{1.25}{R} \cdot \frac{7R}{2} = 4.375V$
 $V_5 = \frac{1.25}{R} \cdot \frac{9R}{2} = 5.625V$
 $V_6 = \frac{1.25}{R} \cdot \frac{11R}{2} = 6.875V$
 $V_7 = \frac{1.25}{R} \cdot \frac{13R}{2} = 8.125V$ } $\leftarrow$ input 7
 $V_{ref} = \frac{1.25}{R} \cdot \left(\frac{13R}{2} + \frac{3R}{2} \right) = 10V$

Digital output code, D

 

Input V_{in} vs Digital output code, D

As all the step size is uniform or equal to 1LSB; this distribution is a uniform distribution. from (V₁ - V₇)

d) if input = 7V ; it will be in between the quantization range of $V_6 - V_7$ or $6.875V - 8.125V$.

Quantization Range	Quantized value	Digital o/p ($b_2 b_1 b_0$)
$6.875V - 8.125V$	6	110

e) If digital output = 110 = 6 (quantized value)

Maximum value of $V_A = 8.125V$

Minimum value of $V_A = 6.875V$

f) If 1 bit was increased $\rightarrow N = 3 + 1 = 4$ bit



No. of R = $2^N = 2^4 = 16$

No. of Comparator = $2^4 - 1 = 15$

Encoder = 15 lines to 4 lines

1 bit of increment doubles the hardware needed.



Question 2 - Flash ADC

  


(a)	Design a 3-bit Flash ADC circuit for the given input-output characteristics.
(b)	An unknown signal is passed to the ADC as input. The ADC takes samples at a rate of 1kHz. In the graph, the input signal is shown where the x-axis represents time, and the y-axis represents the voltage at any specific time. The sampling instances are given in the figure. Find the encoded output that represents the analog signal inside the given time frame.

Solution

Encoding

  

 ① 3 bit ADC - $2^3 - 1 = 7$
Op amps and 8 resistors required.




②

Sampling instance	Level	Encoding
0	3	011
1	4	100
2	5	101
3	6	110
4	6	110
5	5	101
6	3	011
7	2	010
8	0	000
9	0	000
10	0	000

 Question 3 - Dual Slope

Dual - Slope A/D Converter

- A dual slope A/D converter has $V_{ref} = 5V$, and a 8 bit counter that outputs an 8-bit representation of the input signal. A 1 MHz clock is used for the clock and counter circuits



- ① Determine the input voltage range, number of steps and step size (resolution) of the A/D converter.
- ② For a specific input voltage, the ADC outputs a count of $m=100$. Determine the input voltage.
- ③ Determine the total time required to get the reading in ②
- ④ Calculate the maximum sampling rate of the ADC.
- ⑤ A person wishes to get a sampling rate 4 times that of the current circuit. Determine how many bits should be used for the counter without changing any other system parameters.

Solution:

① Input voltage range : $5V$ ($0 - V_{ref}$)
number of steps $= 2^n = 2^8 = 256$
step size $= \frac{\text{voltage range}}{\text{number of steps}} = 0.0195 V$

② We know, $V_{in} = \frac{m}{2^n} V_{ref} = \frac{100}{256} \times 5V = 1.95V$

③ For a single conversion, the integrator

Ⓐ integrates $-V_{in}$ for t_1 duration as counter counts from $0 - 2^n$

$$t_1 = \frac{2^n}{\text{clock rate}} = \frac{256}{1 \times 10^6} = 2.56 \times 10^{-4} s$$

Ⓑ integrates V_{ref} for t_2 duration as counter counts from $0 - m$

$$t_2 = \frac{m}{\text{clock rate}} = \frac{100}{1 \times 10^6} = 1 \times 10^{-4} s$$

$$\text{total conversion time} = t_1 + t_2 = 3.56 \times 10^{-4} s$$

④ Maximum sampling rate is limited by the time required for worst case conversion of input $= 5V$

$$\text{In that case, } t_1 = t_2 = 2.56 \times 10^{-4} s$$

$$\text{thus, worst case conversion duration} = t_1 + t_2 = 5.12 \times 10^{-4} s$$

$$\text{Max sampling rate} = \frac{1}{5.12 \times 10^{-4} s} = 1953.125 \text{ Hz}$$


⑤ Sampling duration $\propto 2^n$ // Sampling rate $\propto \frac{1}{2^n}$

$$\text{For 4 times sampling rate, counter bit} = (8 - 2) = 6$$

 vi) Determine the output binary code when input analog voltage is 3V

$$vi) \frac{D}{2^N} = \frac{V_A'}{V_{REF}} \Rightarrow D = \frac{V_A' \times 2^N}{V_{REF}} = \frac{3}{5} \times 2^8 = 153.6 \approx 153$$

Digital o/p (binary value of 153) = 10011001



Given, number of bits $n = 6$
Clock period = $6 \mu s$
 $v_A' = 2 V$

(a)	Find the value of v_{O1} at $t=T_1$, suppose $R=25k\Omega$ and $C=2\mu F$.
(b)	If $R=50k\Omega$ and we $C=2\mu F$, calculate the new value of V_{O1} at $t=T_1$, compare it with (a) and comment on the changes between two output voltages.

$$a) \text{ slope} = \frac{\Delta Y}{\Delta x} = \tan \theta = \frac{OB}{AB}$$


$$\text{As, } \tan \theta = \frac{V_A'}{RC}; \text{ so } \frac{OB}{AB} = \frac{V_A'}{RC}$$

$$\Rightarrow v_{O1} = OB = \frac{V_A'}{RC} \times AB$$

$$\Rightarrow v_{O1} = \frac{V_A'}{RC} \times T_1$$

$$\Rightarrow v_{O1} = \frac{2}{25k \times 2\mu F} \times 2^6 \times 6\mu s$$

$$v_{O1} = 0.01536 V$$

 

$$T_1 = 2^N \cdot 1 \text{ clock period} \\ = 2^N \cdot T = 2^6 \cdot 6\mu s$$

$$b) v_{O1} = \frac{2}{50k\Omega \times 2\mu F} \times 2^6 \times 6\mu s$$


$$v_{O1} = 0.00768 V$$

Comment:

As, resistance increases by 2, it decreases the output by half.

Question 4 - Binary Weighted DAC

(a)	Determine the output voltage, v_O in V of the 4-bit weighted-resistor D/A in the following figure for input = 1010 and input = 1100? Assume $R_F = 5\text{ k}\Omega$.
(b)	Identify the maximum allowed tolerance ($\pm$ percent) in the value of R_1 so that the maximum error in the output is limited to $\pm \frac{1}{2}$ LSB quantized voltage value? (hint: Do two separate calculations for output error being $+\frac{1}{2}$ LSB and $-\frac{1}{2}$ LSB Then, calculate the percentage change in R_1 in these two cases.)

 

a) Input = 1010; $R_F = 5\text{ k}\Omega$

$$v_O = 5 \times \frac{5}{20} + 5 \times \frac{5}{80} = \boxed{1.5625\text{ V}}$$

Input = 1100; $R_F = 5\text{ k}\Omega$

$$v_O = 5 \times \frac{5}{20} + 5 \times \frac{5}{40} = \boxed{1.875\text{ V}}$$

b) $1\text{ LSB} = 5 \times \frac{5}{160} = 0.15625\text{ V}$

$\Rightarrow \frac{1}{2}\text{ LSB} = 0.078125\text{ V}$

$1\text{ MSB} = 1.25\text{ V} \rightarrow$

$$v_O = 1.25 \pm 0.078125\text{ V}$$

$$= 1.328125\text{ V} \text{ or } 1.171875\text{ V}$$

$$-5 \times \frac{5}{R_1} = 1.328125\text{ V}$$

$$\text{or}$$

$$-5 \times \frac{5}{R_1} = 1.171875\text{ V}$$


$\Rightarrow$

$R_1 = 18.823\text{ k}\Omega \rightarrow \%\text{ change in } R_1 = \frac{20 - 18.823}{20} \times 100 = \boxed{5.88\%}$
 or $21.33\text{ k}\Omega \rightarrow \%\text{ change in } R_1 = \frac{21.33 - 20}{20} \times 100 = 6.67\%$

$\boxed{\text{Max tolerance} \rightarrow 5.88\%}$

$$\left[\begin{array}{l} v_O = 1\text{ MSB} + \frac{1}{2}\text{ LSB} \\ v_O = 1\text{ MSB} \text{ or } - \frac{1}{2}\text{ LSB} \end{array} \right] \text{ Output error}$$

Question 5 - R-2R DAC

 

The N -bit D/A converter with an R - $2R$ ladder network in the above figure is to be designed as a 6-bit D/A device. Suppose $V_{REF} = -5V$ and $R_F = R = 5k\Omega$.

(a)	Find currents $I_1, I_2, I_3, I_4, I_5, I_6$.
(b)	What is the output voltage if the input is 010011?
(c)	What is the change in output voltage if the input changes from 101010 to 010101?

a) $I_1 = \frac{V_{REF}}{2R} = \frac{-5}{10} \Rightarrow I_1 = -0.50mA$

$$I_2 = \frac{I_1}{2} = -0.25mA$$

$$I_3 = \frac{I_2}{2} = -0.125mA$$

$$I_4 = \frac{I_3}{2} = -0.0625mA$$

$$I_5 = \frac{I_4}{2} = -0.03125mA$$

$$I_6 = \frac{I_5}{2} = -0.015625mA$$

b) Input = 010011

$$v_o = -[I_2 + I_5 + I_6] R_F = [0.25 + 0.03125 + 0.015625]mA \times 5k\Omega = 1.484375V$$

c) Input = 101010


$$v_o = -[I_1 + I_3 + I_5] R_F = [0.50 + 0.125 + 0.03125]mA \times 5k\Omega = 3.28125V$$

Input = 010101

$$v_o = -[I_2 + I_4 + I_6] R_F = [0.25 + 0.0625 + 0.015625]mA \times 5k\Omega = 1.640625V$$


$$\Delta v_o = 1.640625V$$

Question 6 - ADC+DAC

 


ADC Input Voltage	Encoding	DAC Output Voltage
0-1	000	0.5
1-2	001	1.5
2-3	010	2.5
3-4	011	3.5
4-5	100	4.5
5-6	101	5.5
6-7	110	6.5
7-8	111	7.5

- | | |
|-----|---|
| (a) | For the following input waveshape, draw the reconstructed output by the DAC. The sampling instances are marked on the input waveshape. |
| (b) | Comment on the quality of the reconstructed signal and how the quality would be affected if additional bits were used for both the ADC and DAC. |

 


Solution:

①

 

ADC Input Voltage	Encoding	DAC Output Voltage
0-1	000	0.5
1-2	001	1.5
2-3	010	2.5
3-4	011	3.5
4-5	100	4.5
5-6	101	5.5
6-7	110	6.5
7-8	111	7.5

 

② Reconstructed signal roughly estimates the original input, and the quality is not very good.

Using higher number of bits for both the ADC and DAC will give a better voltage resolution. The reconstructed voltage levels would be closer to that of the originally sampled value.