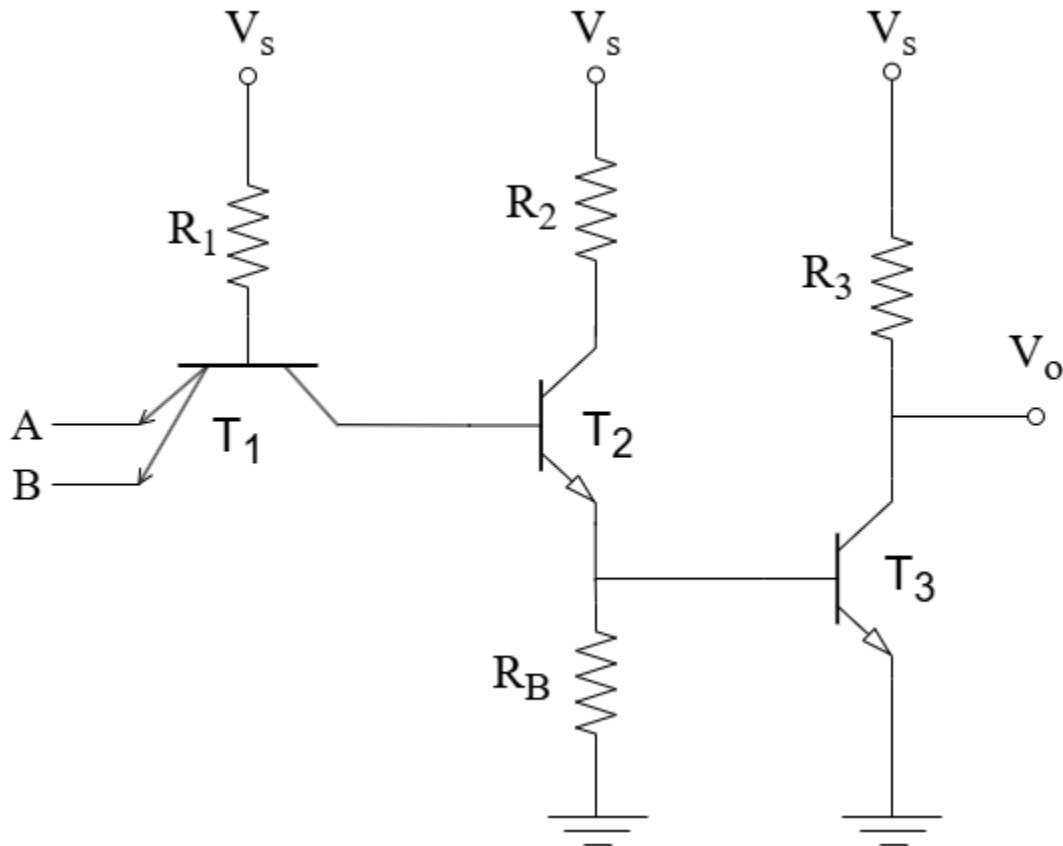


Assignment 2:

Use $V_{\gamma}(\text{diode}) = 0.6 \text{ V}$, $V_D(\text{conducting voltage of diode}) = 0.7 \text{ V}$, $V_{\gamma}(\text{transistor}) = 0.5 \text{ V}$, $V_{BE}(\text{forward active}) = 0.7 \text{ V}$, $V_{BE}(\text{saturation}) = 0.8 \text{ V}$, $V_{CE}(\text{saturation}) = 0.2 \text{ V}$, $\beta_F = 30$, $\beta_R = 0.1$, $V_{BC}(\text{reverse active}) = 0.7 \text{ V}$ for all the questions unless otherwise stated.



Given, $V_S = 9 \text{ V}$, $R_2 = 2 \text{ k}$, $R_3 = 4.4 \text{ k}$, $R_B = 4.4 \text{ k}$

Question 1: Determine the power dissipation of this TTL circuit when both inputs are HIGH. You must show your calculation. Assume $R_1 = 6.7 \text{ k}$ for this question only

Question 2: Suppose you are selling this TTL logic gate to a customer and he states a strict criteria of keeping the power dissipation below 1.23 mW when both inputs are LOW (0 V). Determine the maximum value of R_1 you can use to satisfy this criteria.